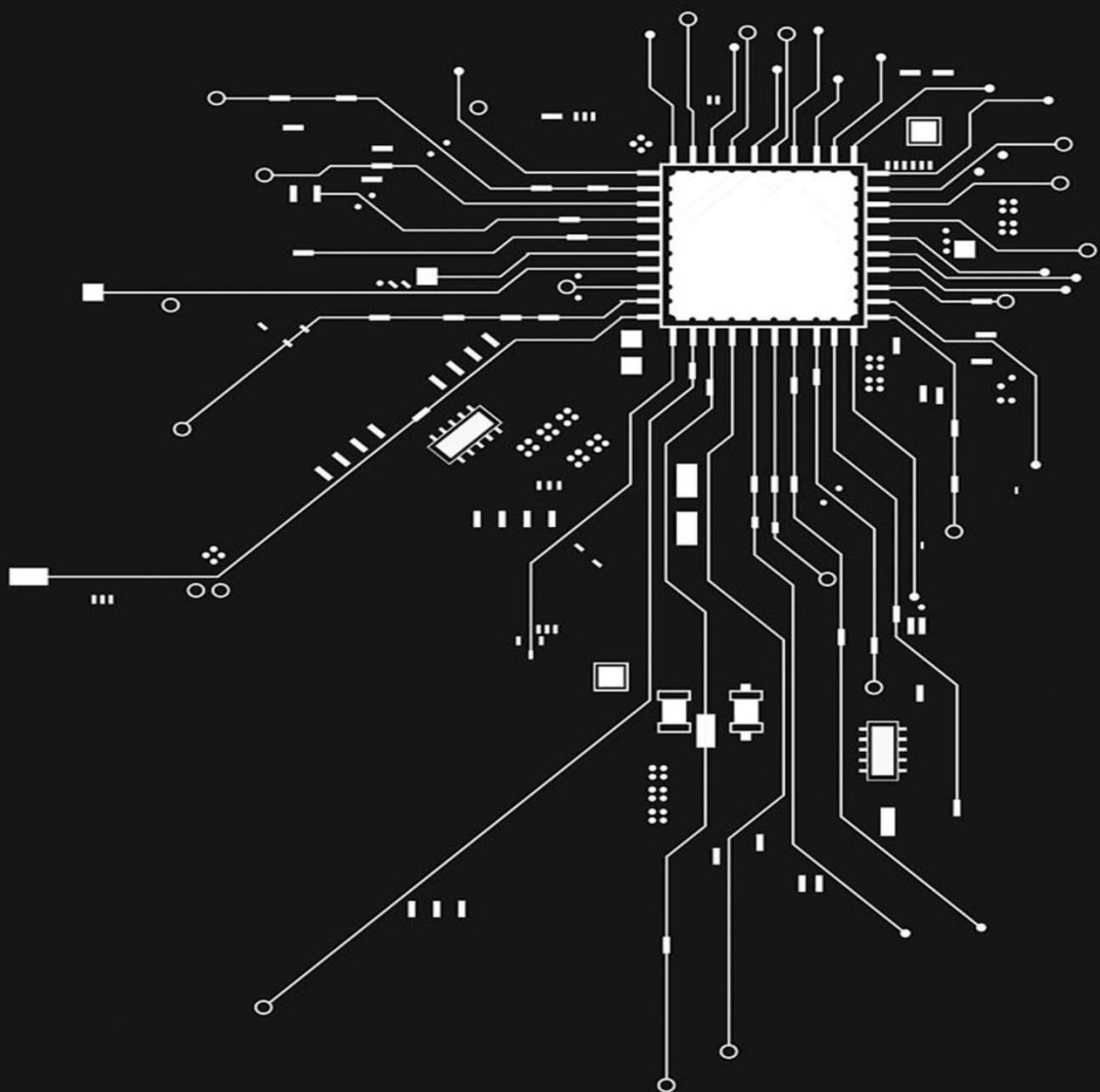


Nas- U4



-Shriya Arunkumar

Unit - 4

- Causality
- Stability

- Hurwitz Polynomials
 - ↳ Properties
 - ↳ Conditions to check

- Positive real function
 - ↳ Conditions

Elementary Synthesis Procedure

LC Impedance functions

RC and RL functions


- Foster form
 - ↳ Form I
 - ↳ Form II
- Cauer form
 - ↳ Form I
 - ↳ Form II

$$\rightarrow \text{transfer functions} \rightarrow H(s) = \frac{a_n s^n + a_{n-1} s^{n-1} + a_{n-2} s^{n-2} + \dots + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_0} \xrightarrow{\text{Response}} R(s) \rightarrow \text{response}$$

$$\xrightarrow{\text{Excitation}} E(s) \rightarrow \text{Excitation}$$

Synthesis is feasible only for **Causality** and **Stability**.

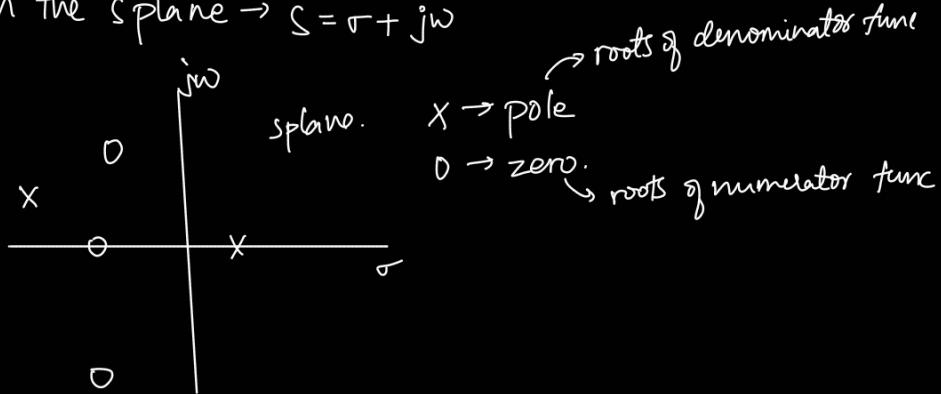→ On the s-plane $\rightarrow s = \sigma + j\omega$



Causality

- ↳ right sided signal
- ↳ no output without being excited
- ↳ response should be zero for $t \leq 0$

$$h(t) = u(n) = \text{causal} \leftarrow e^{-at} u(t)$$

$$u(-n-1) \rightarrow \text{non causal} \leftarrow e^{-at|t|}$$

→ Non causal responses can be modified to become causal by shifting the function (using delay)

→ modified signals are called realisable impulse response

Conditions to be realisable

1) $h(t)$ must have Fourier Transform

2) $\int_{-\infty}^{\infty} |H(j\omega)|^2 d\omega < \infty$ should be integrable

3) Amplitude function must satisfy.

$$\int_{-\infty}^{\infty} \frac{|\log|H(j\omega)||}{1+\omega^2} d\omega < \infty \quad \left. \begin{array}{l} \text{Paley Wiener} \\ \text{criterion} \end{array} \right\}$$

↳ exception $|H(j\omega)| = e^{-\omega^2}$

$$|\log(H(j\omega))| = \omega^2$$

$$\int_{-\infty}^{\infty} \frac{\log(H(j\omega))}{1+\omega^2} d\omega = \int_{-\infty}^{\infty} \frac{\omega^2}{1+\omega^2} d\omega \rightarrow \text{not finite}$$

↳ low pass filter

→ ex of funct satisfying Paley Wiener condition

$$|H(j\omega)| = \frac{1}{\sqrt{1+\omega^2}}$$

Stability

↳ BIBO stable \Rightarrow Bounded input provides a bounded output

↳ denominator of a stable function must be a Hurwitz polynomial

→ Conditions for Stability

① $H(s)$ can't have poles in right half of Splane

② $H(s)$ can't have multiple poles on $(j\omega)$ axis

③ Degree of num \leq degree of denonmt

④ final value theorem must hold good.

Properties of Hurwitz Polynomial

- all roots are real
- all intermediate powers of 's' should be present
 - ↪ special cond → only even powers or odd powers
- all roots should be on the left side of s-plane (left side)
- roots on (jω) axis are simple → shouldn't repeat
- complex roots should be in pairs $1 \pm 2j$

Procedure to check if $P(s)$ is Hurwitz

$$\rightarrow P(s) = b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0 \rightarrow \text{denominator}$$

1) Decompose $P(s)$ to $M(s)$ → even polynomial
and $N(s)$ → odd polynomial

2) Synthetic division → $\frac{M(s)}{N(s)}$ or $\frac{N(s)}{M(s)}$

* If Quotient is +ve → $P(s)$ is Hurwitz

* If $P(s)$ is odd or even, → generate $P'(s)$ and get even & odd part for $P'(s)$

Example

1) $F(s) = s^4 + 3s^3 + 5s^2 + 3s + 4 \rightarrow$ check if Hurwitz

$$f(-s) = s^4 - 3s^3 + 5s^2 - 3s + 4$$

$$M(s) = \frac{F(s) + f(-s)}{2} = s^4 + 5s^2 + 4$$

$$N(s) = 3s^3 + 3s$$

$$\Psi(s) = \frac{M(s)}{N(s)} = \frac{3s^3 + 3s}{s^4 + 5s^2 + 4} \quad \begin{array}{c} \cancel{s^4 + 5s^2 + 4} \\ \cancel{s^3 + 3s} \\ \hline 2s^2 + 4 \end{array} \quad \begin{array}{c} s^3 + 3s \\ \cancel{s^2 + 2s} \\ \hline s \end{array} \quad \begin{array}{c} 2s^2 + 4 \\ \cancel{2s^2 + 4} \\ \hline s \end{array} \quad \begin{array}{c} 4 \\ \cancel{4} \\ \hline 0 \end{array} \quad \rightarrow \text{CFE}$$

$\Psi(s) = \frac{m(s)}{n(s)} = s + \frac{1}{s^2 + \frac{1}{2s + \frac{1}{s/4}}}$

all quotients are +ve ∴ $F(s)$ is Hurwitz

continued factor expression

$$2) G(s) = s^3 + 2s^2 + 3s + 6$$

$$m(s) = 2s^2 + 6 \quad n(s) = s^3 + 3s$$

$$\begin{array}{r} 2s^2 + 6 \\ \overline{-} s^3 + 3s \\ \hline 0 \end{array} \quad \text{common factor b/w } m(s) \text{ & } n(s)$$

$$\Psi(s) = \left(\frac{s}{2} \right) \quad G(s) = W(s) \times P(s)$$

$$3) F(s) = s^4 + s^3 + 2s^2 + 3s + 2$$

$$m(s) = s^4 + 2s^2 + 2 \quad n(s) = s^3 + 3s$$

$$\begin{array}{r} s^3 + 3s \\ \overline{-} s^4 - 3s^2 \\ \hline -s^2 + 2 \end{array} \quad \begin{array}{r} s^3 + 3s \\ \overline{-} s^3 - 2s \\ \hline +s \end{array}$$

$$\begin{array}{r} -s^2 + 2 \\ \overline{-} s^3 - 2s \\ \hline +s \end{array} \quad \begin{array}{r} (-s^2 + 2) \\ \overline{-} (-s^3 - 2s) \\ \hline 2 \end{array} \quad \begin{array}{r} (-s^2 + 2) \\ \overline{-} (-s^3 - 2s) \\ \hline 2 \end{array}$$

$$\Psi(s) = s + \frac{1}{\frac{-s^2 + 1}{2}} \quad \frac{-s^2 + 1}{2} = \frac{1}{\frac{s^2}{2}}$$

→ negative quotient \therefore Not Hurwitz

$$\text{try } f(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$$

$$G(s) = 6s^4 + 2s^2 \rightarrow \text{express as CFE}$$

Positive Real Function

→ Used to represent impedance or admittance

Conditions for Positive, Real function

(1) $F(s)$ is real for real s
i.e. $s = \sigma$

(2) $\operatorname{Re}\{F(s)\} \geq 0$

(3) $F(s) \in \text{Rational}$

$$\left. \begin{array}{l} F(s) = Ls \quad L > 0 \\ F(s) = R \\ F(s) = \frac{1}{sC} \quad C > 0 \\ Y(s) = \frac{K}{s} \\ Y(s) = K \\ Y(s) = KS \end{array} \right\} \begin{array}{l} \text{Impedance} \\ \text{admittance} \end{array}$$

Properties of PR function.

- ↪ Reciprocal of PR func = PR func
- ↪ $y(s) \& z(s)$ are in R
- ↪ Sum of PR = PR
- ↪ Difference of PR ≠ PR
- ↪ PR should be Hurwitz but Hurwitz need not be PR
- ↪ $\frac{a_1 s^m + a_2 s^{m-1} + \dots + a_m}{b_1 s^n + b_2 s^{n-1} + \dots + b_n}$ $m-n=1$ } highest degree difference ≤ 1
lowest degree difference ≤ 1

Conditions for checking Hurwitz is PR

Hurwitz can be PR if

- ① $F(s) \rightarrow$ no poles on right half of s-plane
- ② $F(s) \rightarrow$ simple poles on $(j\omega)$ axis with real & +ve Residues.

$$\text{③ } \operatorname{Re}\{F(j\omega)\} \geq 0 \quad \omega \geq 0 \quad \rightarrow \text{even poly}$$

$$F(s) = \frac{P(s)}{Q(s)} = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)} \rightarrow \text{odd}$$

$$F(s) = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)} \times \frac{M_2(s) - N_2(s)}{M_2(s) + N_2(s)}$$

$$\operatorname{Re}\{F(s)\} = \frac{M_1(s)M_2(s) - N_1(s)N_2(s)}{M_2^2(s) - N_2^2(s)} \quad s=j\omega$$

$$\operatorname{Re}\{F(j\omega)\} = M_1(j\omega)M_2(j\omega) - N_1(j\omega)N_2(j\omega)$$

$$F(s) = \frac{s+a}{s^2+bs+c} \rightarrow (b \geq a, a, b, c \geq 0) \rightarrow \text{should be satisfied}$$

$$F(s) = \frac{s^2+a_1s+a_0}{s^2+b_1s+b_0} \rightarrow a_1, b_1 \geq (\sqrt{a_0} - \sqrt{b_0})^2$$

ex(1) check if $f_1(s) = \frac{s+2}{s^2+3s+2}$ is PR

$$F(s) = \frac{s+a}{s^2+bs+c} \rightarrow b \geq a, a, b, c \geq 0$$

$a=1, b=3, c=2$ $3 > 2 \therefore$ Is PR

~~$F_2(s) = \frac{s+1}{s^2+2}$~~

$a=1, b=0, c=2$
 $0 < 1 \therefore$ Not PR
 $b < a$

* first check if roots are on left side of plane

$$\text{ex3 } F_3(s) = \frac{s+4}{s^2+2s+1}$$

$a=4 \quad b=2 \quad c=1$ Not PR

$$\text{ex4 } F(s) = \frac{s^2+2s+25}{s^2+5s+16}$$

$a_1=1 \quad a_0=25 \quad 10 \geq (5-4)^2$
 $b_1=5 \quad b_0=16 \quad 10 \geq 1$
 $\therefore \text{is PR}$

$$M_1(s) = 2s^2 + 2 \quad N_1(s) = 2s^3 + 3s$$

$$\begin{aligned} & 2s^2 + 2 \quad | 2s^3 + 3s \\ & -2s^3 - 2s \\ & \hline s) 2s^2 + 2 \quad (2s \\ & -7s^2 \\ & \hline 2) s (s/2 \\ & -s \\ & \hline \end{aligned}$$

$\Psi(s)$ is Hurwitz

Elementary Synthesis Procedure

↪ impedance function which is PR can be decompose to elements $Z_i(s)$ and those are basically \rightarrow RLC circuits
 \rightarrow can be done for admittance parameters also

Analysis

$$Z(s) = \frac{P(s)}{Q(s)} = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}$$

CITERION-1
 \hookrightarrow when $b_0 = 0 \Rightarrow$ there is a pole at $s=0$.

$$\begin{aligned} Z(s) &= Z_1(s) + Z_2(s) \\ &= \frac{K}{s} + Z_2(s) \} \text{Partial fraction} \end{aligned}$$

then you synthesize a circuit for it

CITERION-2

$\hookrightarrow n-m=1 \Rightarrow$ pole at $s=\infty$

$$Z(s) = Z_1(s) + Z_2(s) = Ls + Z_2(s)$$

Remove pole by synthetic division $\Rightarrow \frac{P(s)}{Q(s)} = Ks + \frac{1}{1 + }$

CRITERION 3

$\hookrightarrow z(s) \rightarrow$ poles are complex conjugates

$$z(s) = \frac{2s}{s^2 + w_1^2} + z_2(s)$$

CRITERION 4

$\hookrightarrow \min(\operatorname{Re}\{z(jw)\}) =$

$$\text{ex1 } \frac{7s+2}{2s+4} = \frac{2(4) - 7s(2s)}{16 - (2s)^2} = \left(\frac{8 - 14s^2}{16 - 4s^2} \right) = \frac{7s^2 - 4}{2s^2 - 8}$$

$$\text{ex2 } \frac{(3s^2 + 1)(0) - (6s^3 + 3s)(6s^3 + 3s)}{s^2 - (6s^2 + 3s)^2} = 1$$

ex1

$$z(s) = \frac{s^2 + 2s + 6}{s(s+3)}$$

criteria 1 (pole at $s=0$)

$$\frac{s^2 + 2s + 6}{s(s+3)} = \frac{A}{s} + \frac{B}{s+3}$$


$$A = 2$$

$$B = -3$$

$$\begin{aligned} z_2(s) &= z(s) - \frac{2}{s} \\ &= \frac{s^2 + 2s + 6}{s(s+3)} - \frac{2(s+3)}{s(s+3)} \\ z_2(s) &= \frac{s^2 + 2s + 6 - 2s^2 - 6s}{s(s+3)} = \frac{-s^2 + 2s + 6}{s(s+3)} \end{aligned}$$

$$z(s) = \frac{2}{s} + \frac{1}{s+3}$$
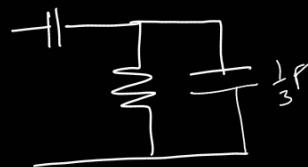
$$= \frac{2}{s} + \frac{1}{1 + \left(\frac{3}{s}\right)}$$



$$\text{ex2 } z(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s}$$

(CR 4)

$$z(s) = \min(\operatorname{Re}\{F(s)\}) + z_2(s)$$

$$\min(\operatorname{Re}\{F(s)\}) = \frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2} = \frac{6s^2 + 1(0) - (6s^3 + 3s)(6s^3 + 3s)}{s^2 - (6s^3 + 3s)^2} = 1$$

$$z(s) = 1 + z_2(s)$$

$$z_2(s) = \frac{6s^3 + 3s^2 + 3s + 1 - (6s^3 + 3s)}{6s^3 + 3s}$$

$$\therefore \frac{3s^2 + 1}{6s^3 + 3s} = \frac{1}{Y(s)}$$

$$Y_2(s) = \frac{6s^3 + 3s}{3s^2 + 1} \quad n-m=1 \Rightarrow s=\infty \text{ (pole)} \\ \therefore \text{ criteria 2}$$

$$\frac{3s^2 + 1}{6s^3 + 3s} \xrightarrow[s]{\cancel{6s^3 - 2s}} \frac{2s}{s} \Rightarrow Y_2(s) = 2s + \frac{1}{3s^2 + 1}$$

$$Z(s) = 1 + \frac{1}{2s + \frac{1}{3s + 1}} \rightarrow \begin{array}{c} 1 \\ \text{---} \\ M \\ | \\ 2n \\ | \\ 3H \\ | \\ 1P \end{array}$$

Network Synthesis

LC immittance admittance
or
impedance

→ LC one port N/W → dissipation less

→ LC N/W aka → reactive networks

$$z(s) = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)}$$

$$P_{avg} = \frac{1}{2} \operatorname{Re} [z(j\omega)] |I|^2$$

for reactive N/W → P=0

$$\operatorname{Re} [z(j\omega)] = 0 = E \vee [z(j\omega)] \\ \text{where } E \vee [z(s)] = \frac{M_1(s) \cdot M_2(s) - N_1(s) N_2(s)}{M_2^2(s) - N_2^2(s)} = 0$$

$$\Rightarrow M_1(j\omega) \cdot M_2(j\omega) - N_1(j\omega) \cdot N_2(j\omega) = 0$$

case 1 ① $M_1 = 0 = N_2 \Rightarrow z(s) = \frac{N_1(s)}{M_2(s)}$

② $M_2 = 0 = N_1 \Rightarrow z(s) = \frac{M_1(s)}{N_2(s)}$

∴ we can conclude \rightarrow LC immittance \rightarrow ratio of odd to even polynomials
or even to odd polynomials

$\rightarrow E$, odd \rightarrow Both are Hurwitz \Rightarrow poles, zeros all on Im axis

Properties

- ① ratio of odd or even polynomials
- ② poles & zero \rightarrow on $\text{Im}(j\omega)$ axis and are simple
- ③ all ω -coefficients in the function must be real and positive
- ④ highest and lowest powers of numerator & denominator must differ by 1
- ⑤ If polynomial is even \rightarrow all even powers; if odd \rightarrow all odd powers
- ⑥ $\text{Re}[Z(j\omega)] = 0$ for $\omega \geq 0$
- ⑦ as all poles are imaginary, \Rightarrow residues should be real & +ve
- ⑧ LC impedance / admittance can be given by

$$Z(s) = \frac{k(s^2 + \omega_1^2)(s^2 + \omega_2^2)}{s(s^2 + \omega_3^2)(s^2 + \omega_4^2)} \dots \quad \begin{matrix} \text{complex conjugates} \\ \text{partial fractions} \end{matrix}$$

$$Z(s) = \frac{k_0}{s} + \frac{2k_2 s}{s^2 + \omega_2^2} + \frac{2k_4 s}{s^2 + \omega_4^2} + \dots + k_\infty s$$

all poles are on Im axis

$$\Rightarrow s = j\omega, \text{Re}\{F(j\omega)\} = 0$$

$$Z(j\omega) = j \left[-\frac{k_0}{\omega} - \frac{2k_2 \omega}{\omega_2^2 - \omega^2} + \frac{2k_4 \omega}{\omega_4^2 - \omega^2} + \dots + k_\infty \omega \right]$$


$$= j X(\omega) \quad \begin{matrix} \text{pure reactance} \end{matrix}$$

since residues are real $\Rightarrow \frac{dX(\omega)}{d\omega} \geq 0$

$$⑨ Z(s) = \frac{k_s (s^2 + \omega_3^2)}{(s^2 + \omega_2^2)(s^2 + \omega_4^2)} \dots \quad \begin{matrix} s = j\omega \end{matrix}$$

$$Z(j\omega) = j X(\omega) = j \frac{k\omega (-\omega^2 + \omega_3^2)}{(-\omega^2 + \omega_2^2)(-\omega^2 + \omega_4^2)}$$

$X(\omega)$ can be plotted as

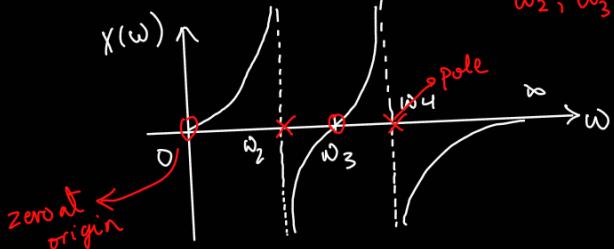

$0, \infty \rightarrow$ external critical frequencies
 $\omega_2, \omega_3, \omega_4 \rightarrow$ internal critical frequencies

* poles and zeros alternate


Numerical

1) State if these are driving point immittances of LC networks

$$Z(s) = \frac{5s(s^2+4)}{(s^2+1)(s^2+3)}$$

$$\text{poles} = \pm 1, \pm \sqrt{3}$$

$$\text{zeros} = \pm 2, 0$$

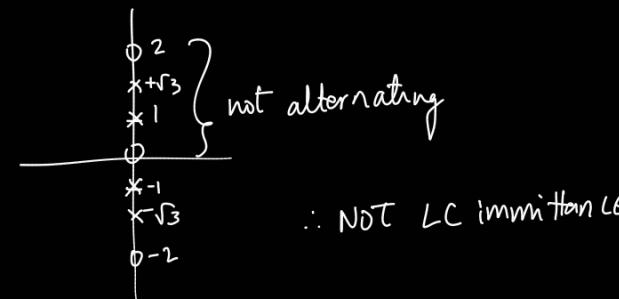


$$2) Z(s) = \frac{2(s^2+1)(s^2+9)}{s(s^2+2)}$$

$$\text{zeros} = \pm 1, \pm 3$$

$$\text{poles} = 0, \pm \sqrt{2} = 1.414$$

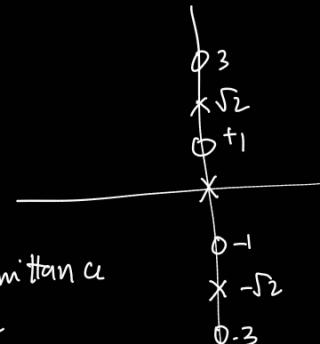alternating, on Im axis \Rightarrow LC imittance func



Synthesis of LC imittance

→ Foster form (Partial Fraction Expansion)

→ Cauer form (Continuous Fraction Expansion)

Foster Realisation

↪ advantage → all poles can be removed simultaneously

$$F(s) = \frac{H(s^2+\omega_1^2)(s^2+\omega_3^2)}{s(s^2+\omega_2^2)(s^2+\omega_4^2)}$$

by PFE

$$F(s) = \frac{K_0}{s} + \frac{K_2}{s+j\omega_2} + \frac{K_2^*}{s-j\omega_2} + \dots + K_\infty s$$

$$F(s) = \frac{K_0}{s} + \frac{2K_2}{s^2+\omega_2^2} + \dots + K_\infty s \quad \left. \begin{array}{l} \text{on combining these two take } K = K^* \\ \{ K_0, K_1, K_2, \dots, K_i, K_\infty \text{ are residues of } f(s) \text{ at } 0, 1, 2, \dots, j\omega_i \text{ and } \infty \text{ respectively} \end{array} \right\}$$

$$\text{Residues are } \rightarrow K_0 = \lim_{s \rightarrow 0} s F(s)$$

$$K_i = \left. \frac{(s^2+\omega_i^2)F(s)}{2s} \right|_{s^2 = -\omega_i^2}$$


$$K_\infty = \lim_{s \rightarrow \infty} F(s)$$

Foster I form \rightarrow impedance func
II form \rightarrow Admittance func

forster I form

$$* F(s) = Z(s) - \frac{K_0}{s} + \frac{2K_2 s}{s^2 + \omega_2^2} + \dots + K_\infty s \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{When summed up} \rightarrow \text{series connection}$$

$$= Z_1(s) + Z_2(s) + \dots + Z_n(s)$$

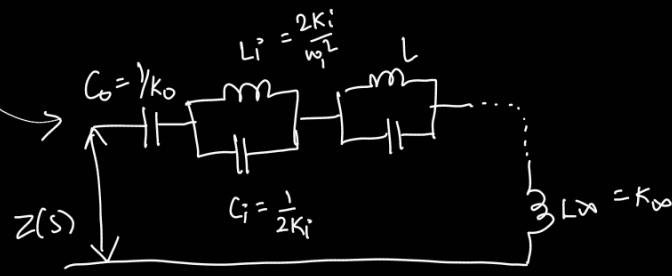

* Pole at origin $\rightarrow C_0$

* pole at $\infty \rightarrow L_\infty$

$$\frac{K_0}{s} \rightarrow \text{capacitor of } \frac{1}{K_0} F \quad \rightarrow \text{---} \quad \frac{1}{K_0} = C_0$$

$$K_\infty s \rightarrow \text{inductor of } K_\infty H \quad \rightarrow \text{---} \quad K_\infty = L_\infty$$

$$\frac{2K_i s}{s^2 + \omega_i^2} \rightarrow L \parallel C \Rightarrow \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} \quad \rightarrow \frac{\left(\frac{1}{C_i}\right)s}{s^2 + \frac{1}{L_i C_i}}$$

$$\frac{2K_i}{\omega_i^2} \rightarrow \frac{1}{2K_i} \quad \rightarrow \frac{2K_i}{\omega_i^2} = C_i$$

forster II form


$$F(s) = Y(s) = \frac{K_0}{s} + \frac{2K_2 s}{s^2 + \omega_2^2} + \dots + K_\infty s \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{each term represents impedance}$$

$$= Y_1(s) + Y_2(s) + \dots + Y_n(s) \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{when added} \rightarrow \text{gives parallel connection of each term}$$

$$\frac{K_0}{s} \rightarrow \text{---} \quad \frac{1}{K_0} H$$

$$K_\infty \rightarrow \text{---} \quad \frac{1}{K_\infty} F$$
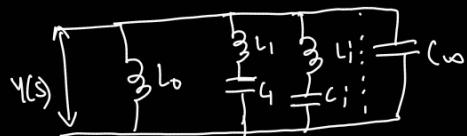
$$\frac{2K_i s}{s^2 + \omega_i^2} \rightarrow \text{---} \quad \parallel \quad \text{(series)} \quad L_i = \frac{1}{2K_i} \quad \frac{2K_i}{\omega_i^2} = C_i$$



Cauer form I

↪ successive removal of pole/zero at $s=\infty$

↪ first you have $Z(s) \rightarrow \text{impedance func.}$

by removing a pole at ∞ ,

$$Z_2(s) = Z(s) - L_1 s \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{criterion 2}$$

after removing the pole at ∞ , $Z_2(s)$ has a zero at $s=\infty$.

Now invert $Z_2(s)$ to get $Y_2(s)$; $Y_2(s)$ has a pole at ∞ .


$$Y_3(s) = Y_2(s) - C_2 s \quad \left. \begin{array}{l} \text{criterion 2} \\ \text{for removing pole at } \infty \end{array} \right\}$$

$Y_3(s) \rightarrow \text{zero at } s=\infty$.

$$\hookrightarrow \frac{1}{Y_3(s)} = Z_3(s) \rightarrow \text{pole at } s=\infty$$


for impedance func like $Z_2(s)$, $Z_4(s) \rightarrow$ when pole is removed its replaced by inductor
for admittance func $\rightarrow Y_3(s) \rightarrow$ when is removed \rightarrow put capacitor
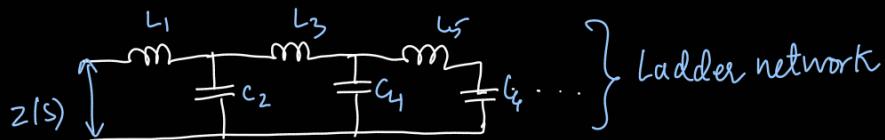
$$Z(s) = L_1 s + \frac{1}{C_2 s + \frac{1}{L_3 s + \frac{1}{C_4 s + \dots}}} \quad \text{Represented in diagram}$$



* If $Z(s) = \frac{P(s)}{Q(s)} \rightarrow$ if degree of numm - deg of den = 1 \Rightarrow zero at ∞
 \hookrightarrow when this is satisfied invert $Z(s)$ and continue with $Y(s)$

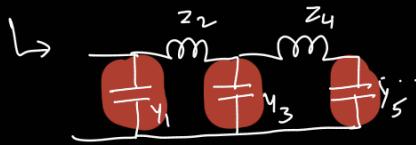\hookrightarrow when this is given first element is a capacitor \hookrightarrow it is removed in admittance func.



Cauer form II

\hookrightarrow removal of pole origin.

\hookrightarrow the lowest deg of Num - lowest deg of denominator = 1

$\hookrightarrow \frac{s(s+i)}{s^2+2s+4} \rightarrow \text{zero at } s=0$

\hookrightarrow so invert it $\frac{s^2+2s+4}{s(s+i)} \Rightarrow$ pole at $s=0$

\downarrow
remove the pole by division method.


\downarrow
keep repeating.

$$z(s) = \frac{1}{C_1 s} + \frac{1}{\frac{1}{L_2 s} + \frac{1}{\frac{1}{C_3 s} + \frac{1}{\dots}}}$$



* if $Z(s)$ has zero at origin \rightarrow then first element is inductor and the cap. -

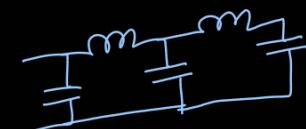* if $Z(s)$ has pole at origin \rightarrow first element is capacitor



ex ① Realise the foster & Cauer forms $\rightarrow Z(s) = \frac{4(s^2+1)(s^2+4)}{s(s^2+4)}$

\hookrightarrow it is an LC impedance func \rightarrow poles or zero at $0, \pm j, \pm j\sqrt{3}$

$$Z(s) = \frac{4(s^2+1)(s^2+9)}{s(s^2+4)}$$

* Numerator degree is greater than deno.
 \therefore do division first

$$= 4(s^4 + 10s^2 + 9) / s^3 + 4s$$

$$= \frac{4s^4 + 40s^2 + 36}{s^3 + 4s}$$

FOSTER form I

$$\begin{array}{r} s^3 + 4s \\ \overline{-} 4s^4 - 16s^2 \\ \hline 24s^2 + 36 \end{array}$$

$$= 4s + \frac{24s^2 + 36}{s^3 + 4s} = 4s + \frac{24s^2 + 36}{s(s^2 + 4)} \quad * \text{ Now apply PFE}$$

$$= 4s + \frac{k_0}{s} + \frac{k_1}{s+j2} + \frac{k_1^*}{s-j2}$$

$$= 4s + \frac{k_0}{s} + \frac{2k_1 s}{(s^2 + 4)}$$

$$k_0 = s Z(s) \Big|_{s=0} = \frac{4(s^2+1)(s^2+9)}{s(s^2+4)} = \frac{4(1)(9)}{4} = 9$$

$$k_1 = \frac{(s^2+4)Z(s)}{2s} \Big|_{s^2=-4} = \frac{(s^2+4)(4)(s^2+1)(s^2+9)}{s(s^2+4)(2s)} = \cancel{\frac{(-3)(5)}{2}} = \frac{15}{2}$$

$$Z(s) = 4s + \frac{9}{s} + \frac{15s}{(s^2+4)}$$



$$\frac{1}{2k_1} = C \quad \frac{2k_1}{\omega_1^2} =$$

$$s(s^2+4) =$$

$$\cancel{4(s^2+1)(s^2+9)}$$


$$\text{ex } Y(s) = \frac{s(s^2+4)}{4(s^2+1)(s^2+9)} \quad \text{FOSTER form II}$$

By PFE

$$Y(s) = \frac{2k_1 s}{s^2 + 1} + \frac{2k_2 s}{s^2 + 9}$$

$$k_1 = \frac{(s^2+1)Y(s)}{2s} \Big|_{s^2=-1} = \frac{(s^2+1)}{2s} \cdot \cancel{\frac{s(s^2+4)}{4(s^2+1)(s^2+9)}} = \frac{1}{8} \left(\frac{3}{8}\right) = \frac{3}{64} \quad \left. \right\}$$

$$k_2 = \frac{(s^2+9)Y(s)}{2s} \Big|_{s^2=-9} = \frac{(s^2+9)}{2s} \cdot \cancel{\frac{s(s^2+4)}{4(s^2+1)(s^2+9)}} = \frac{1}{8} \left(\frac{-5}{8}\right) = \frac{5}{64} \quad \left. \right\}$$

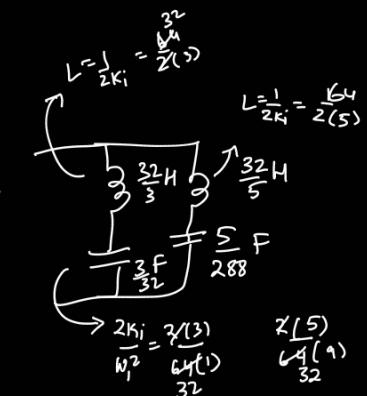

$$\text{ex3 } Z(s) = \frac{4s^4 + 40s^2 + 36}{s^3 + 4s}$$

* deg of Num > deg dem by 1 \Rightarrow pole at ∞

Do CFE

CAUER form I

$$\begin{aligned}
 & s^3 + 4s \overbrace{4s^4 + 40s^2 + 36}^{(4s)^4} \leftarrow Z(s) \\
 & -4s^4 \overbrace{-16s^2}^{24s^2 + 26} \overbrace{s^3 + 4s}^{s^3 - \frac{3}{2}s} \leftarrow Y(s) \\
 & -\cancel{s^3} - \frac{3}{2}s \overbrace{24s^2 + 36}^{24s^2} \leftarrow \frac{48s}{s} \\
 & -24s^2 \overbrace{36}^{s_1 s} \leftarrow \frac{\frac{ss}{72}}{s} \\
 & -\frac{\frac{ss}{72}}{s} \overbrace{0}^{0} \\
 & \text{Circuit: } \frac{m}{4n} \parallel \frac{1}{\frac{1}{24}f} \parallel \frac{m}{\frac{ss}{72} f}
 \end{aligned}$$

$$\text{ex4 } Z(s) = \frac{4s^4 + 40s^2 + 36}{s^3 + 4s}$$


* Arrange numerator & denominator in ascending order of power.

CAUER-form II

$$Z(s) = \frac{36 + 40s^2 + 4s^4}{4s + s^3}$$

* Do CFE
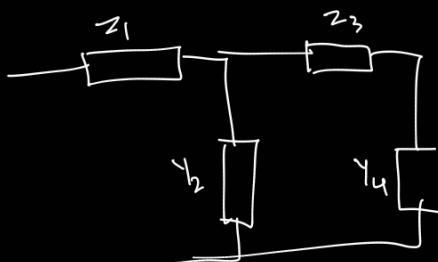
$$\begin{aligned}
 & 4s + s^3 \overbrace{36 + 40s^2 + 4s^4}^{(s)^4} \leftarrow \frac{1}{Z(s)} \\
 & -36 \quad -9s^2 \quad \frac{48}{31s^2} \quad \times \\
 & \overbrace{31s^2 + 4s^4}^{4s^4 + s^3} \leftarrow Y_2(s) \quad \frac{31 - 16}{31} = \frac{15}{31}
 \end{aligned}$$



$$\begin{aligned}
 Z(s) &\rightarrow ks \rightarrow L \\
 \frac{1}{ks} &\rightarrow k \rightarrow C \\
 Y(s) &\rightarrow ks \rightarrow c \\
 \rightarrow \frac{1}{ks} &\rightarrow L = k
 \end{aligned}$$

$$\begin{aligned}
 & \frac{15}{31}s^3 \overbrace{31s^2 + 4s^4}^{(961/15)s^2} \leftarrow \frac{31s^2(31)}{15s^2} \\
 & -31s^2 \overbrace{4s^4}^{15s^3} \leftarrow Z_3 \quad \frac{15s^3}{45s^4} \\
 & -\frac{15s^3}{31} \overbrace{0}^{0} \leftarrow Y_4
 \end{aligned}$$

RC Driving Point Impedances

→ Replace all inductances by resistances in the foster form I

$$Z(s) = \frac{k_0}{s} + k_{00} + \frac{k_1}{s + \tau_1} + \frac{k_2}{s + \tau_2} + \dots$$

$$C_0 = \frac{1}{K_0} \quad \left(\frac{1}{CS} = \frac{K_0}{S} \right) \quad R_{\infty} = K_{\infty} \quad \left(\frac{1}{\frac{S}{K_1} + \frac{\sigma_1}{K}} \right) \quad C_1 = \frac{1}{K_1} \quad R_1 = \frac{K_1}{\sigma_1}$$

$$Z(s) = \frac{Y_C}{s + \frac{1}{R_C}}$$

$$Y(s) = \frac{Y_L}{s + \frac{R}{L}}$$


$$C_2 = \frac{1}{K_2} \quad R_2 = \frac{K_2}{\sigma_2}$$

Properties

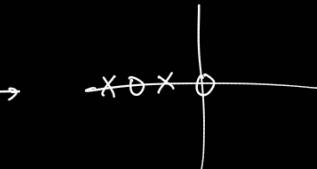1) Poles & zeros lie on -ve real axis and are interlacing \rightarrow

$$2) Z_0(0) = \begin{cases} \infty \rightarrow C_0 \text{ is present} \\ \leq R_i \rightarrow \omega \text{ is missing} \end{cases} \rightarrow Z(s) = \frac{\frac{K_0}{s}}{\frac{1}{s+R_0}} = Z(0) = \infty$$

$$Z(\infty) = \begin{cases} R_{\infty} \rightarrow R_{\infty} \text{ is present} \\ 0, \quad R_{\infty} \text{ is missing} \end{cases}$$




$$Z(0) > Z(\infty) \rightarrow RC$$

$$Z(\infty) > Z(0) \rightarrow RL$$

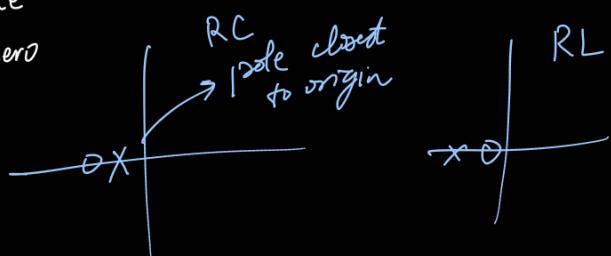3) Critical frequency \Rightarrow singularity σ_1

\hookrightarrow singularity closest to origin (σ_1) should be a pole

\hookrightarrow singularity closest to ∞ (σ_n) should be a zero




4) Residues of poles must be real & +ve

$$\frac{d}{ds} Z_{RL} < 0$$

$$Z_{RL}(\infty) < Z_{RL}(0)$$

Ex 1) Det. which of the following represent RC impedance func.
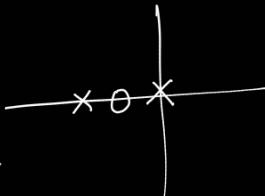
$$Z(s) = \frac{(s+1)(s+4)(s+8)}{s(s+2)(s+6)}$$



\rightarrow it is a RC imp func because

(critical frequency at $s=0 \rightarrow$ is a pole)
and nearest critical frequency to $-\infty$ (-8) is a zero

\rightarrow Poles & zeros interlace

$$(ii) Z(s) = \frac{(s+1)(s+8)}{(s+2)(s+4)} \quad \text{Not RC} \quad \text{impedance} \rightarrow \text{critical frequency closest to origin (-1) is a zero}$$

$$(iii) Z(s) = \frac{(s+2)(s+4)}{(s+1)} \rightarrow \text{Not RC}$$

\hookrightarrow poles & zeros do not interlace

$$(iv) Z(s) = \frac{(s+1)(s+2)}{(s+3)} \quad \text{Not RC}$$

\hookrightarrow closest to origin is a zero

Synthesis of RC Impedance & RL Admittance

→ Foster I → RC impedance

→ Foster II → RC admittance

* If Numerator degree ≥ Denominator → divide till num < denominator and then apply PFE to get series Resistance & parallel impedance

* Quotient is $Z(n)$ → C for Foster I, L for Foster II

$$\text{ex 1 } H(s) = \frac{3(s+2)(s+4)}{s(s+3)} = \frac{3s^2 + 18s + 24}{s^2 + 3s}$$

$$\begin{array}{c} s^2 + 3s \overbrace{3s^2 + 18s + 24}^{(3)} \\ - \cancel{s^2 - 9s} \\ \hline 9s + 24 \end{array}$$

$$H(s) = 3 + \frac{9s + 24}{s(s+3)}$$

$$\frac{9s + 24}{s(s+3)} = \frac{A}{s} + \frac{B}{s+3}$$

$$\frac{1}{RC} = 3 \quad R = \frac{1}{3}$$

$$\begin{array}{l} s=0 \quad A=8 \\ s=-3 \quad B=1 \end{array}$$

$$H(s) = 3 + \frac{8}{s} + \frac{1}{s+3} \rightarrow \begin{array}{c} \frac{V_C}{s+1/R} \\ H(s) \end{array} \quad \begin{array}{c} 3 \quad (1/8)F \\ \text{---} \end{array} \quad \begin{array}{c} V_L \\ 1/H \end{array}$$


If $H(s)$ is realized for RL admittance

(treat $H(s)$ as $\gamma(s)$)

$$H(s) = \frac{8}{s} + 3 + \frac{1}{s+3}$$

$$\frac{V_L}{s+R/L} \quad R=3 \quad L=1$$
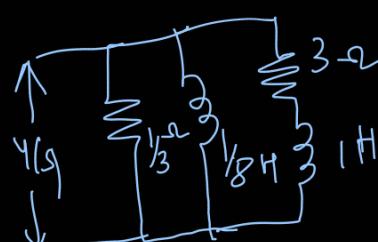
$$\begin{array}{l} L=8 \\ L=1/8 H \end{array}$$



→ Case 1 → numerator in descending order

→ apply CFE

$$\text{ex } H(s) = \frac{3(s+2)(s+4)}{s(s+3)} = \frac{3s^2 + 18s + 24}{s^2 + 3s}$$

$$\frac{s^2 + 3s}{s^2 - 9s} \xrightarrow{3s^2 + 18s + 24} (s+2)^2$$


$$\frac{1}{s^2 - 9s} \xrightarrow{-s^2 - 8s} \frac{1}{s^2 - 9s}$$

$$\frac{24}{s^2 - 9s} \xrightarrow{\frac{24}{s^2 - 9s}} \frac{24}{s^2 - 9s}$$

$$\frac{24}{s^2 - 9s} \xrightarrow{\frac{24}{s^2 - 9s}} \frac{24}{s^2 - 9s}$$

If $H(s)$ is impedance function then
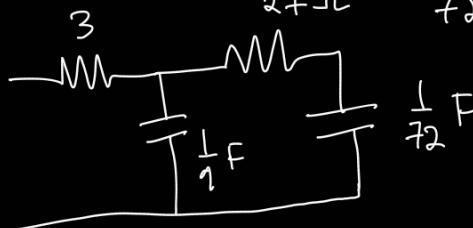
$$Z = \frac{1}{\frac{S}{9} + \left(\frac{1}{27} + \frac{1}{\frac{S}{72}} \right)}$$



$$\frac{1}{s^2 - 9s} \xrightarrow{\frac{1}{s^2 - 9s}} \frac{1}{s^2 - 9s}$$


$$\frac{24}{s^2 - 9s} \xrightarrow{\frac{24}{s^2 - 9s}} \frac{24}{s^2 - 9s}$$

$$\frac{24}{s^2 - 9s} \xrightarrow{\frac{24}{s^2 - 9s}} \frac{24}{s^2 - 9s}$$

$$Z_2 = \frac{1}{L}$$

$$L = \frac{1}{Z_2}$$

If $H(s)$ is admittance function RL func

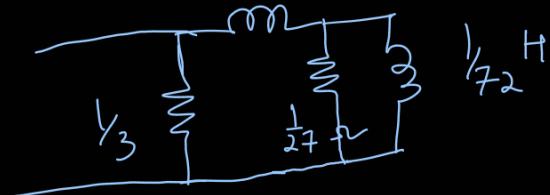

* If $H(s)$ represents RL impedance or RC admittance then the poles & zeros are -ve so we can't use foster so use $\frac{H(s)}{s} = \frac{k_0 + k_1 s + k_2}{s + \sigma_i} \dots \dots$

$$\text{ex } H(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

$$\text{by PFE of } H(s) = 2 - \frac{1/2}{s+2} - \frac{15/2}{s+6} \times 1/(2)(-1)$$

$$\text{so } \frac{H(s)}{s} = \frac{2(s+1)(s+3)}{s(s+2)(s+6)} = 2(s+1)(s+3) = A(s+2)(s+6) + B(s)(s+6) + C(s)(s+2)$$


$$s = -2 \quad s = 0 \quad s = -6$$

$$B = \frac{1/2}{-8} \frac{1}{4} \quad A = \frac{6}{12} \sim \frac{1}{2} \quad C = \frac{2(-5)(-3)}{-6(-4)} = \frac{1}{4}$$


$$\frac{H(s)}{s} = \frac{1/2}{s} + \frac{1/4}{(s+2)} + \frac{5/4}{s+6}$$

$$H(s) = \frac{1}{2} - \frac{5/4}{(s+2)} + \frac{5s/4}{s+6} \quad \left. \right\} \text{represents an impedance function}$$

If $H(s)$ is impedance func.

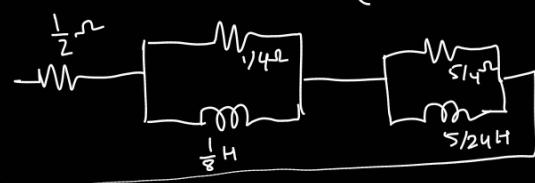

If $H(s)$ is
admittance

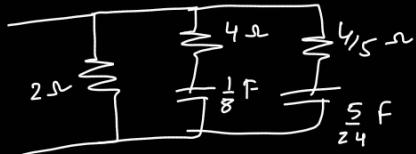


$$\text{Ex3 } H(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)} \quad \text{using Cauer form II}$$

$$\text{Cauer II} \rightarrow \frac{6+8s+2s^2}{12+8s+s^2}$$

CFE

$$\begin{aligned} & 12+8s+s^2 - \cancel{6+4s+s^2} \cancel{(s+2)} \\ & - \cancel{4s+\frac{3}{2}s^2} \cancel{12+8s+s^2} \cancel{(s+\frac{3}{2})} \quad u_s = \frac{7s}{2} \times 2 \\ & - \cancel{s+\frac{9s}{2}} \cancel{\frac{7s}{2}+s^2} \cancel{(s+\frac{8}{7})} \\ & - \cancel{4s-\frac{8}{7}s^2} \cancel{\frac{5}{14}s^2} \cancel{(s+\frac{5}{14}s^2)} \\ & - \cancel{\frac{7s}{2}} \cancel{s^2} \cancel{(s+\frac{5}{14}s^2)} \end{aligned}$$

If $H(s)$ is an impedance func

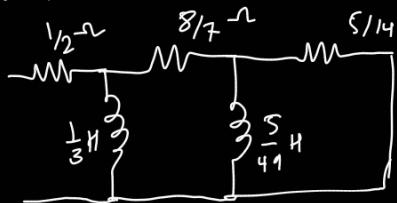

If $H(s)$ is an admittance func

