

# nas UNIT - 3

## Coupled Circuits



→ Inductance - Change in flux linking a coil due to change in current through the coil

$$L_p \propto \frac{d\phi_p}{di_p} \Rightarrow L_p = N_p \frac{d\phi_p}{di_p}$$

→ By Faraday's Law, change in flux in one coil induces voltage across that coil

$$e_p = N_p \frac{d\phi_p}{dt} \Rightarrow e_p = \left( L_p \frac{d\phi_p}{di_p} \right) \frac{di_p}{dt} \Rightarrow e_p = L_p \frac{di_p}{dt}$$

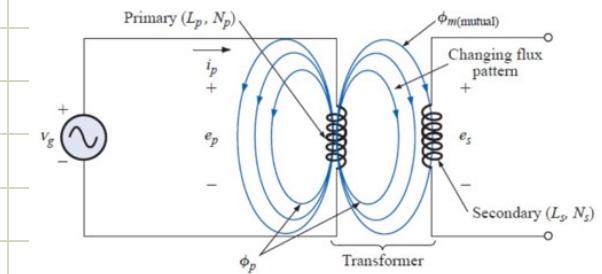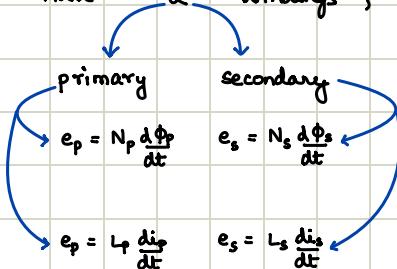→ In Coupled circuits, we have 2 windings, in which current flows



→ We can create a relation,

$$\frac{\phi_s}{\phi_p} = K$$

K: coefficient of coupling

K = 1 for ferromagnetic cores

$$e_s = N_s K \frac{d\phi_p}{dt}$$


$$M = N_s \frac{d\phi_p}{di_p}$$

$$(or) \quad N_p \frac{d\phi_p}{di_s}$$

→ Mutual Inductance

(Measure of change in flux linking one coil due to change in current flow in other coil)

$$M = K \sqrt{L_p L_s}$$

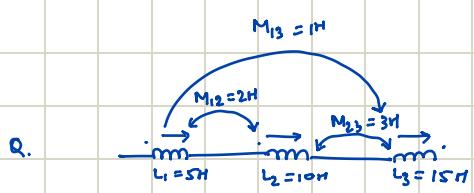


A.  $L_1 + M_{23} - M_{13} = 5 + 2 - 1 = 6H$

$$L_2 + M_{12} - M_{23} = 10 + 2 - 3 = 9H$$


$$L_3 - M_{13} - M_{23} = 15 - 1 - 3 = 11H$$

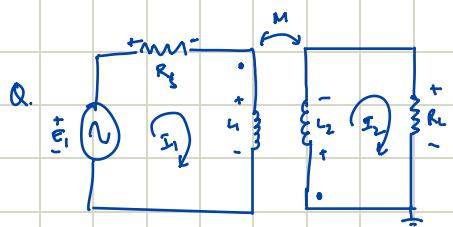Total Inductance  $\Sigma = 6 + 9 + 11 = 26H$



$$E_1 - L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} - R_1 i_1 = 0$$
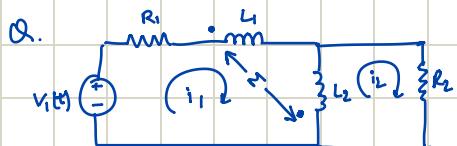
$$-L_2 \frac{di_2}{dt} - R_2 i_2 - M \frac{di_1}{dt} = 0$$



$$v_1(t) - i_1 R_1 - L_1 \frac{di_1}{dt} - L_2 \frac{d(i_1 - i_2)}{dt} + M \frac{d(i_1 - i_2)}{dt} + M \frac{di_1}{dt} = 0$$

$$R_1 i_1(t) + (L_1 + L_2 - 2M) \frac{di_1}{dt} - (L_2 - M) \frac{di_2}{dt} = v_1(t)$$

$$R_1 i_1(t) + j X_{LA} i_1(t) - j X_{LB} i_2(t) = v_1(t)$$

$$X_{LA} = \omega(L_1 + L_2 - 2M) \quad X_{LB} = \omega(L_2 - M)$$

$$L_2 \frac{di_2}{dt} + i_2 R_2 - L_2 \frac{di_1}{dt} + M \frac{di_1}{dt}$$


$$(L_2 + M) \frac{di_2}{dt} + R_2 i_2 + L_2 \frac{di_1}{dt}$$

$$-j X_{LC} i_1(t) + R_2 i_2 + j X_{LD} \dot{i}_2(t)$$

$$X_{LC} = \omega(L_1 - M)$$

$$X_{LD} = \omega L_2$$

Q.

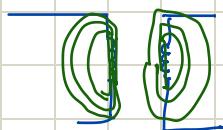

$$L_p = 200 \text{ mH} \quad L_s = 800 \text{ mH}$$

$$N_p = 50 \quad N_s = 100$$

$$K = 0.6 \quad \frac{d\phi}{dt} = 450 \text{ mWb/s}$$

a)  $M = ?$

b)  $e_p = ?$

c)  $e_s = ?$

d)  $e_p \& e_s$  if  $\frac{d\phi}{dt} = 0.2 \text{ A/ms}$

A. a)  $M = K \sqrt{L_p L_s} = 0.6 \sqrt{200 \times 800 \times 10^{-3} \times 10^{-3}} = 0.24 \text{ H}$

b)  $e_p = N_p \frac{d\phi}{dt} = 50 \times 0.45 = 22.5 \text{ V}$


c)  $e_s = N_s \frac{d\phi}{dt} = 100 \times 0.45 = 45 \text{ V}$

d)  $\frac{d\phi}{dt} = 0.2 \text{ A/ms} \approx 200 \text{ Vs/s}$


$$e_p = L_p \frac{d\phi}{dt} = 200 \times 10^{-3} \times 200 = 40 \text{ V}$$

$$e_s = M \frac{d\phi}{dt} = 0.24 \times 200 = 48 \text{ V}$$

Q.

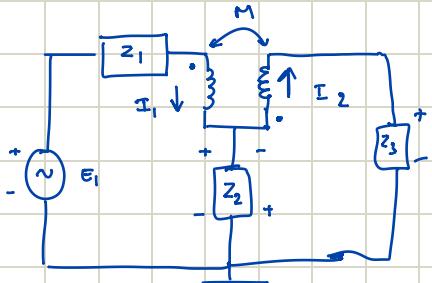


A.

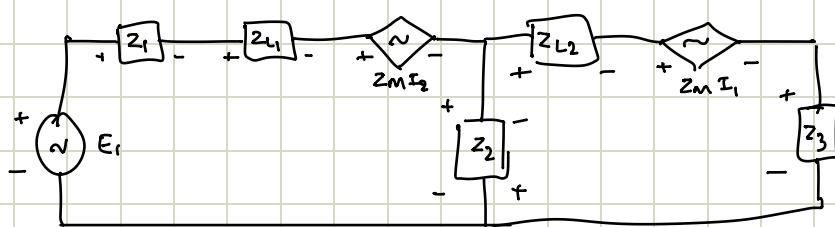

$$E_1 - I_1 Z_1 - I_1 Z_{L1} - z_M I_2 - Z_2 I_1 + Z_2 I_2 = 0 \Rightarrow (z_1 + z_2 + z_{L1}) I_1 + (z_M - z_2) I_2 = E_1$$

$$Z_{L2} I_2 + Z_2 I_2 - Z_2 I_1 + Z_3 I_2 + z_M I_1 = 0 \Rightarrow (z_M - z_2) I_1 + (z_2 + z_3 + z_{L2}) I_2 = 0$$

Q.

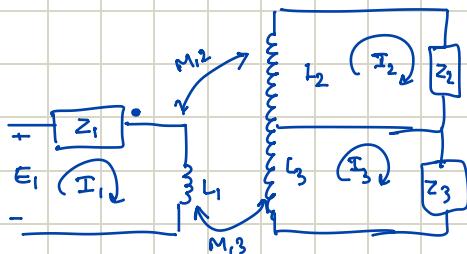

$$A. \quad I_1 Z_1 + L_1 \frac{dI_1}{dt} - M_{12} \frac{dI_2}{dt} - M_{13} \frac{dI_3}{dt} = E_1$$

$$L_2 \frac{dI_2}{dt} + Z_2 I_2 - M_{12} \frac{dI_1}{dt} = 0$$

$$L_3 \frac{dI_3}{dt} + Z_3 I_3 - M_{13} \frac{dI_1}{dt} = 0$$

$$Q. \quad I = 5A \quad \Phi_{11} = 0.2 \text{ mWb} \quad \Phi_{12} = 0.4 \text{ mWb}$$

$$N_1 = 500 \quad N_2 = 1500$$

$$L_1, L_2, M, K = ?$$

$$A. \quad \Phi_1 = \Phi_{11} + \Phi_{12} = 0.2 + 0.4 = 0.6 \text{ mWb}$$

$$L_1 = \frac{N_1 \Phi_1}{I_1} = \frac{500 \times 0.6}{5} \times 10^{-3} = 0.06 \text{ H}$$

$$\Phi_s = K \Phi_p$$

$$\Phi_{12} = K \Phi_1 \Rightarrow K = \frac{0.4}{0.6} = 0.67 = \frac{2}{3}$$

$$M = N_2 \frac{\Phi_{12}}{I_1} = 1500 \times \frac{0.4 \times 10^{-3}}{5} = 0.12 \text{ H}$$

$$M = K \sqrt{L_1 L_2}$$

$$L_2 = \left( \frac{M}{K} \right)^2 \times \frac{1}{L_1} = \left( \frac{0.12}{\frac{2}{3}} \right)^2 \times \frac{1}{0.06} = 0.18 \times 3 = 0.54 \text{ H}$$

$$Q. \quad L_1 = 50 \text{ mH} \quad L_2 = 200 \text{ mH}$$

$$K = 0.5 \quad N_2 = 1000$$

$$I_1 = 5 \sin 400t$$

$$\text{Find } e_2 = ? \quad \Phi_1 = ?$$

$$A. \quad M = K \sqrt{L_1 L_2} = 0.5 \sqrt{10000 \times 10^{-6}} = 0.05 \text{ H}$$

$$e_2 = M \frac{di_1}{dt} = 0.05 \frac{d}{dt} (5 \sin 400t)$$

$$\approx 0.05 \times 5 \cos 400t \times 400$$

$$\approx 10.0 \cos 400t$$

$$\approx 10.0 \sin \left( 400t + \frac{\pi}{2} \right)$$

$$M = N_2 \frac{\Phi_s}{I_1} = \frac{N_2 K \Phi_1}{I_1} = \frac{0.05 \times 5}{1000 \times 0.5} = 5 \times 10^{-4} \text{ Wb}$$

## System Analysis

### → Ports in a network

→ Sometimes a circuit can't be described using branch elements, so we use port based parameters which relate  $I$  &  $V$  across different ports under special conditions applied on one or more ports




Port consists of terminals & independent sources/load can be connected to a port

→ Port parameters:  $I$  &  $V$  across the ports are related using these parameters  
ex:  $z$ ,  $y$ , Hybrid, Transmission

### → Configurations

→ Includes development of 2, 3, multiport models

→ Some common configurations are:

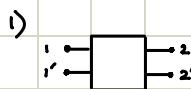

Two port network




Single Port  
Terminals 1' & 2'  
are common



Multiport

### → One port network

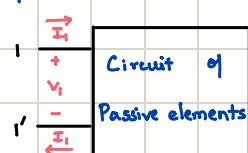

Nodal eq in terms of passive elements is given by

$$\begin{bmatrix} i_1 \\ 0 \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \cdots & Y_{1N} \\ Y_{21} & Y_{22} & \cdots & Y_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{N1} & Y_{N2} & \cdots & Y_{NN} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{bmatrix}$$


$$\Delta y = \begin{vmatrix} Y_{11} & Y_{12} & \cdots & Y_{1N} \\ Y_{21} & Y_{22} & \cdots & Y_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{N1} & Y_{N2} & \cdots & Y_{NN} \end{vmatrix}$$

$$\Delta_{11} = \begin{vmatrix} Y_{22} & \cdots & Y_{2N} \\ \vdots & \ddots & \vdots \\ Y_{N2} & \cdots & Y_{NN} \end{vmatrix}$$

$$V_1 = \frac{i_1 \Delta_{11}}{\Delta y}$$


$$Y_{11} = \frac{i_1}{v_1} = \frac{\Delta y}{\Delta_{11}} \Rightarrow i_1 = y_{11} v_1$$

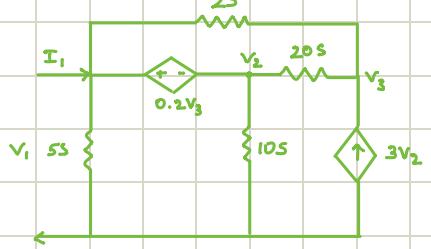Q. Find input impedance & input admittance



A. 1)  $v_1 - v_2 = 0.2v_3 \Rightarrow 10v_1 - 10v_2 - 2v_3 = 0$

2)

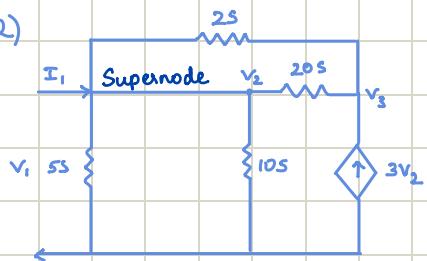

3) KCL at supernode

$$7v_1 + 30v_2 - 22v_3 = I_1$$

4) KCL for node 3

$$-2v_1 - 23v_2 + 22v_3 = 0$$

5) Find  $Z_{11}$  &  $y_{11}$  of the given one port network

$$\begin{bmatrix} 7 & 30 & -22 \\ -2 & -23 & 22 \\ 10 & -10 & -2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ 0 \\ 0 \end{bmatrix}$$


$$v_1 = I_1 \frac{\begin{vmatrix} -23 & 22 \\ -10 & -2 \end{vmatrix}}{\begin{vmatrix} 7 & 30 & -22 \\ -2 & -23 & 22 \\ 10 & -10 & -2 \end{vmatrix}} = I_1 \chi$$

$$Z_{11} = \frac{v_1}{I_1} = 0.0936 \Omega$$

$$y_{11} = \frac{1}{Z_{11}} = 10.68 S$$

→ Two port network

→ 2 separate ports for input & output

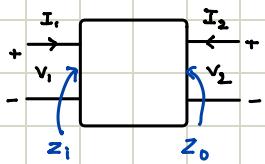

→ Current entering one terminal of a pair leaves the other terminal in the pair

→ Impedance parameters

$Z_1$  : input impedance b/w Terminals 1 & 1'

$Z_0$  : output impedance b/w Terminals 2 & 2'

$$Z_1 = \frac{E_1}{I_1} \quad \text{and} \quad Z_0 = \frac{E_0}{I_0}$$

→ Open Circuit Analysis

$$\text{If } I_2 = 0 \Rightarrow Z_{11} = \left. \frac{E_1}{I_1} \right|_{I_2=0}$$

$$Z_{21} = \left. \frac{E_2}{I_1} \right|_{I_2=0}$$


$$\text{If } I_1 = 0 \Rightarrow Z_{12} = \left. \frac{E_1}{I_2} \right|_{I_1=0}$$

Symmetry Condition :  $Z_{11} = Z_{22}$

Reciprocal Condition :  $Z_{12} = Z_{21}$


$$Z_{22} = \left. \frac{E_2}{I_2} \right|_{I_1=0}$$

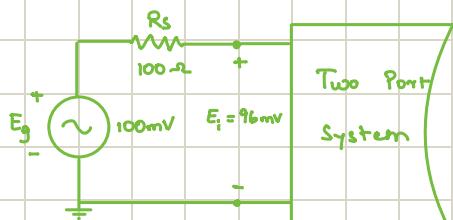Q. Determine  $Z_i$  if input impedance is purely resistive



$$A. \quad Z_i = R_i = \frac{E_i}{I_i} = \frac{E_i}{\frac{V_{RS}}{R_S}} = \frac{\frac{96m}{(100-96)m}}{100} = \frac{96 \times 100}{4} = 2.4 \text{ k}\Omega$$

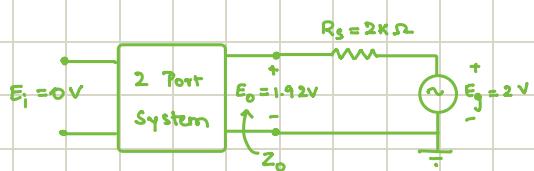Q. Determine  $Z_o$  if output impedance is purely resistive




$$A. \quad Z_o = \frac{E_o}{I_o} = \frac{E_o}{\frac{V_{RS}}{R_S}} = \frac{\frac{1.92}{2-1.92}}{\frac{2000}{2000}} = 48 \text{ k}\Omega$$

Q. Determine impedance parameters




Symmetry condition  $z_{11} = z_{22}$

Reciprocal condition  $z_{12} = z_{21}$

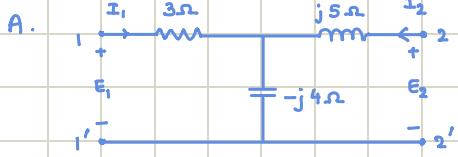


If  $I_2 = 0$

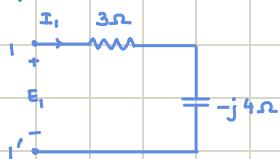

$$\text{By KVL, } z_{11} = \left. \frac{E_1}{I_1} \right|_{I_2=0} = 3 - j4\Omega$$


$$z_{21} = \left. \frac{E_2}{I_1} \right|_{I_2=0} = -j4\Omega$$

If  $I_1 = 0$

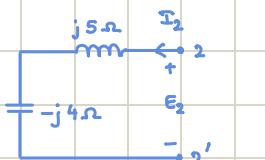

$$z_{12} = \left. \frac{E_1}{I_2} \right|_{I_1=0} = -j4\Omega$$

$$z_{22} = \left. \frac{E_2}{I_2} \right|_{I_1=0} = j1\Omega$$

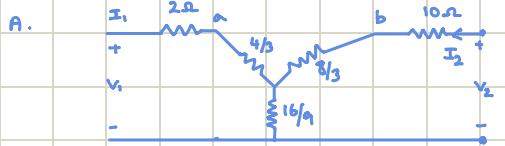

If  $I_2 = 0$




By KVL,

$$z_{11} = \frac{2 + 4}{3} + \frac{16}{9} = 5.11\Omega$$

$$z_{21} = \frac{16}{9} = 1.77\Omega$$

If  $I_1 = 0$

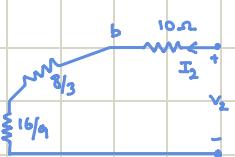


By KVL,


$$z_{22} = 10 + \frac{8}{3} = 12.67$$

$$z_{12} = \frac{16}{9} = 1.77\Omega$$

Q. Find z-parameters in the circuit

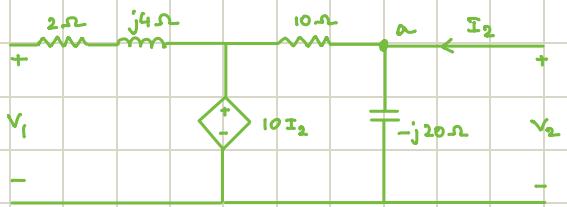


A. If  $I_2 = 0$

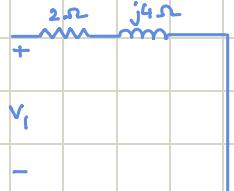

$$Z_{11} = (2 + j4) \Omega$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{0}{\frac{1}{2}} = 0$$

If  $I_1 = 0$

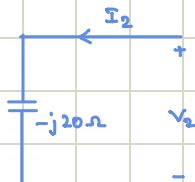

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{10I_2}{I_2} = 10 \Omega$$

KCL at a,

$$\frac{V_2 - 10I_2}{10} + \frac{V_2}{-j20} = I_2$$

$$V_2 = \frac{2I_2}{\left(\frac{1}{10} - \frac{1}{j20}\right)} \Rightarrow \frac{V_2}{I_2} = (16 - j8) \Omega$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = (16 - j8) \Omega$$

Q.




$$A. Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 20 + 40 = 60 \Omega$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = 40 \Omega$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = 40 \Omega$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = 30 + 40 = 70 \Omega$$

→ Admittance ( $\mathbf{Y}$ ) Parameters

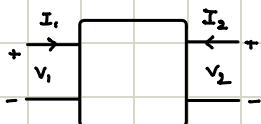

Using 2 port  $\mathbf{Y}$  parameters,

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$y_{11} \xrightarrow{\text{input admittance}} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$y_{12} \xrightarrow{\text{transfer admittance (port 1 to port 2)}} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$y_{21} \xrightarrow{\text{transfer admittance (port 2 to port 1)}} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$y_{22} \xrightarrow{\text{output admittance}} = \frac{I_2}{V_2} \Big|_{V_1=0}$$



So,

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}^{-1}$$


→ For a network that is linear & no dependant sources,  $y_{12} = y_{21}$

→ A reciprocal network ( $y_{12} = y_{21}$ ) can be modelled with  $\Pi$ -equivalent

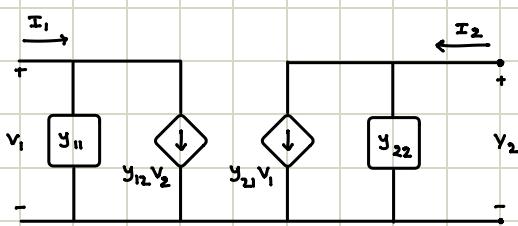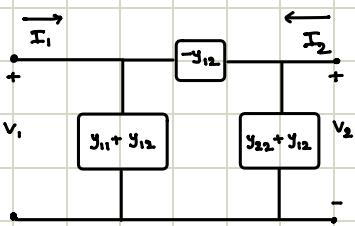else, a more general equivalent circuit is used



Q.

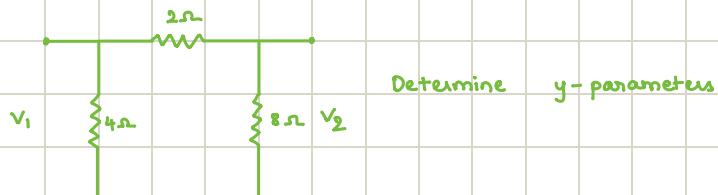


Determine  $\mathbf{y}$ -parameters

$$A. \quad y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{I_1}{(4+\frac{1}{2})^{-1} I_1} = \frac{1}{4} + \frac{1}{2} = 0.75 S$$

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = \frac{-8}{(8+2)^{-1} I_2} = -0.5 S$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{-4 I_1}{(4+\frac{1}{2})^{-1} I_1} = -0.5 S$$

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{I_2}{(8+2)^{-1} I_2} = 0.625 S$$

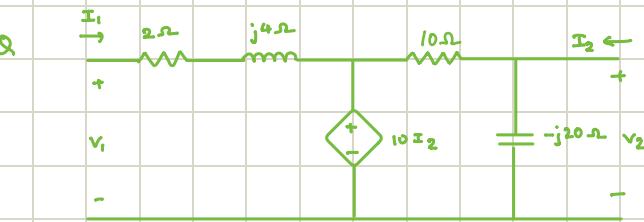

A.  $v_2 = 0$ ,

$$y_{11} = \frac{I_1}{V_1} = \frac{I_1}{I_1(2+4j)} = \frac{1}{2+4j} \quad \left( -v_1 + I_1(2+4j) + 10I_2 = 0 \right)$$

$$v_1 = I_1(2+4j)$$


$$y_{21} = \frac{I_2}{V_1} = 0$$

$$v_1 = 0$$

$$y_{22} = \frac{I_2}{V_2} = \left( \frac{1}{10} - \frac{1}{j20} \right) \times \frac{1}{2} = 0.05 + j0.025$$

$$y_{12} = \frac{I_1}{V_2} = \frac{-10I_2}{2+j4} = -10 \times (0.05 + j0.025) = -0.1 + j0.025$$

Q.

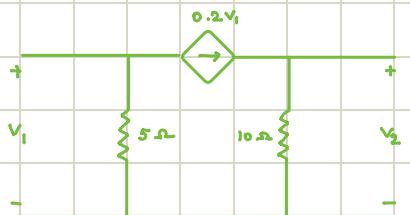

A.  $v_2 = 0$ ,

$$y_{11} = \frac{I_1}{V_1} = 0.4 \text{ S} \quad \left( -I_1 + \frac{V_1}{5} + 0.2V_1 = 0 \right)$$


$$y_{21} = \frac{I_2}{V_1} = -0.2 \text{ S} \quad (I_2 = -0.2V_1)$$

$$v_1 = 0$$


$$y_{12} = \frac{I_1}{V_2} = \frac{0.2V_1}{V_2} = \frac{0}{V_2} = 0$$

$$y_{22} = \frac{I_2}{V_2} = 0.1 \text{ S} \quad \left( \frac{V_2}{10} = I_2 \right)$$

Q.

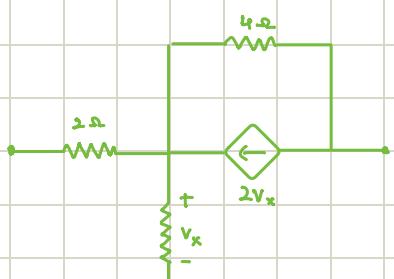

A.

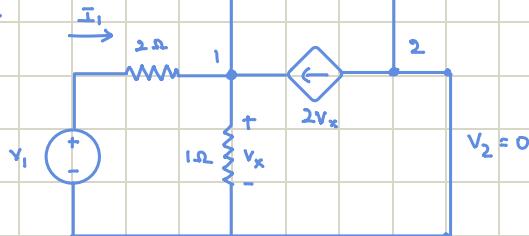


$$\text{At } 1, \frac{V_x}{1} + \frac{V_x}{4} = 2V_x + \frac{V_1 - V_x}{2} \Rightarrow 2V_1 = -V_x$$

$$\text{Also, } I_1 = \frac{V_1 - V_x}{2} = \frac{V_1 + 2V_1}{2} = 1.5V_1$$

$$y_{11} = 1.5S$$

$$\text{And, } I_2 + \frac{V_x}{4} = 2V_x \Rightarrow I_2 = 1.75V_x = -3.5V_1$$

$$y_{21} = \frac{I_2}{V_1} = -3.5S$$

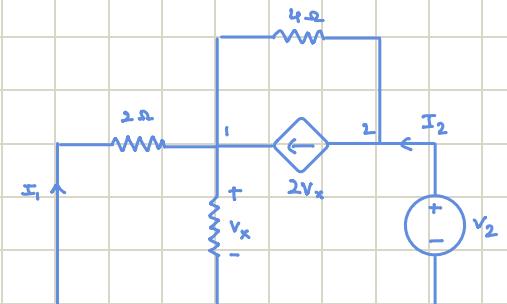

$$\text{At } 2, \frac{V_2 - V_x}{4} = I_2 - 2V_x$$

$$\text{At } 1, \frac{V_x}{2} + \frac{V_x}{1} + \frac{V_x - V_2}{4} = 2V_x$$

$$\hookrightarrow V_2 = -V_x$$

$$I_2 = -1.5V_2$$

$$y_{22} = -1.5S$$

$$\text{and, } I_1 = \frac{-V_x}{2} \Rightarrow \frac{I_1}{V_2} = 0.5S = y_{12}$$

→ Hybrid Parameters

→ Mixture of  $I$  &  $V$  variables on 1 side

$$E_1 = h_{11}I_1 + h_{12}E_2$$

$$I_2 = h_{21}I_1 + h_{22}E_2$$


$$\begin{bmatrix} E_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ E_2 \end{bmatrix}$$

$$\rightarrow \text{If } E_2 = 0, h_{11} = \left. \frac{E_1}{I_1} \right|_{E_2=0} \quad (\text{short circuit input impedance})$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{E_2=0} \quad (\text{short circuit current gain})$$

$$\text{If } E_1 = 0, h_{12} = \left. \frac{I_1}{I_2} \right|_{E_1=0} \quad (\text{open reverse voltage})$$

$$h_{22} = \left. \frac{E_2}{V_2} \right|_{E_1=0} \quad (\text{open circuit output impedance})$$

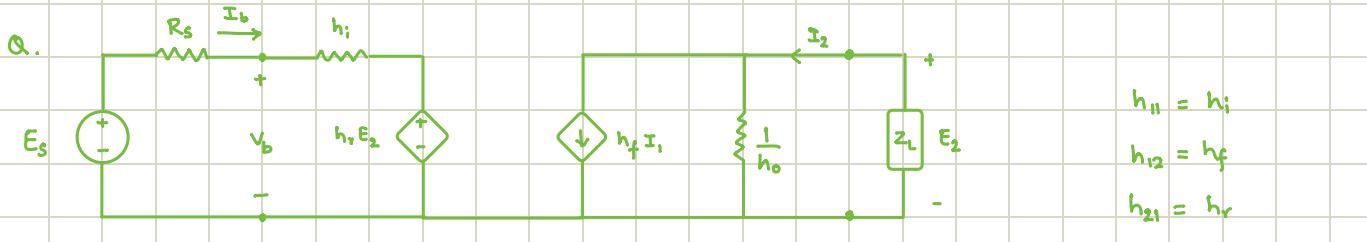

$$h_{11} = h_i$$

$$h_{12} = h_f$$

$$h_{21} = h_r$$

$$h_{22} = h_o$$

$$E_1 = h_{11} I_1 + h_{12} E_2$$

$$I_2 = h_{21} I_1 + h_{22} E_2$$

For the hybrid equivalent circuit, derive the following

i) Current ratio (gain)  $A_i = \frac{I_2}{I_1}$

ii) Voltage ratio (gain)  $A_v = \frac{E_2}{E_1}$

A. i)  $I_2 = \frac{\frac{1}{h_o} \cdot h_f I_1}{\frac{1}{h_o} + Z_L}$

$$\frac{I_2}{I_1} = \frac{h_f}{1 + h_o Z_L} = A_i$$

ii) KVL on input side,

$$E_1 = h_i I_1 + h_f E_2$$

$$\frac{E_1 - h_f E_2}{h_i} = I_1 \rightarrow \textcircled{1}$$

$$I_2 = h_f I_1 + h_o E_2$$

$$\frac{-E_2}{Z_L} = h_f I_1 + h_o E_2 \rightarrow \textcircled{2}$$

Put \textcircled{1} in \textcircled{2}

$$\frac{-E_2}{Z_L} = h_f \left( \frac{E_1 - h_f E_2}{h_i} \right) + h_o E_2$$

$$-h_i E_2 = Z_L h_f E_1 - Z_L h_f E_2 + Z_L h_o h_i E_2$$

$$E_2 (Z_L h_f - Z_L h_o h_i - h_i) = Z_L h_f E_1$$

$$\frac{E_2}{E_1} = \frac{Z_L h_f}{Z_L h_f - Z_L h_o h_i - h_i} = \frac{Z_L h_f}{Z_L h_f - h_i (Z_L h_o + 1)} = A_v$$



Q. Suppose  $h_i = 1\text{k}\Omega$ ,  $h_r = 4 \times 10^4$ ,  $h_f = 50$ ,  $h_o = 25\mu\text{s}$  &  $Z_L = 2\text{k}\Omega$

Calculate  $A_i$  &  $A_v$

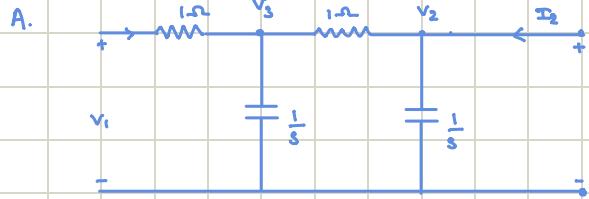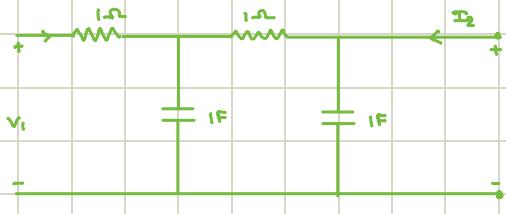A.  $A_i = \frac{h_f}{1 + h_o Z_L} = \frac{50}{1 + (25 \times 10^{-6} \times 2 \times 10^3)} = 47.62$

$$A_v = \frac{Z_L h_f}{Z_L h_f - h_i (Z_L h_o + 1)} = \frac{2000 \times 50}{(2000 \times 50) - 1000(2 \times 10^3 \times 25 \times 10^{-6} + 1)} = -99$$

Q. Find  $\gamma$ -parameters of network system



$$I_1 = \frac{v_1 - v_3}{1} \rightarrow ①$$

$$\text{at node 3, } \frac{v_3}{1/s} + \frac{v_3 - v_2}{1} = I_1 \Rightarrow (s+1)v_3 - v_2 = I_1 \rightarrow ②$$

$$\text{at node 2, } \frac{v_2 - v_3}{1/s} + \frac{v_2}{1} = I_2 \Rightarrow (s+1)v_2 - v_3 = I_2 \rightarrow ③$$


$$① = ② \Rightarrow v_1 - v_3 = (s+1)v_3 - v_2 \Rightarrow v_3 = \frac{v_1}{s+2} + \frac{v_2}{s+2}$$

$$I_1 = \frac{(s+1)(v_1 + v_2)}{s+2} - v_2 = \left(\frac{s+1}{s+2}\right)v_1 - \frac{v_2}{s+2}$$

$$I_2 = (s+1)v_2 - \left(\frac{v_1 + v_2}{s+2}\right) = \frac{-v_1}{s+2} + \left(\frac{s^2 + 3s + 1}{s+2}\right)v_2$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{s+1}{s+2} & \frac{-1}{s+2} \\ \frac{-1}{s+2} & \frac{s^2 + 3s + 1}{s+2} \end{bmatrix}$$

Q.

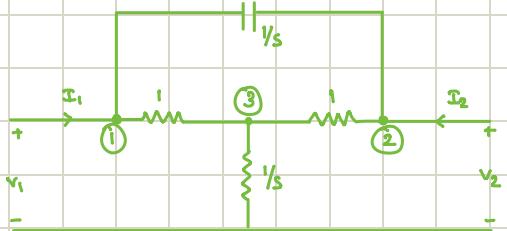

A. At node ①,  $\frac{v_1 - v_3}{1} + \frac{v_1 - v_2}{1/s} = I_1 \Rightarrow (s+1)v_1 - sv_2 - v_3 = I_1$

At node ②,  $\frac{v_2 - v_1}{1/s} + \frac{v_2 - v_3}{1} = I_2 \Rightarrow I_2 = (s+1)v_2 - sv_1 - v_3$


At node ③,  $\frac{v_3 - v_1}{1} + \frac{v_3 - v_2}{1} + \frac{v_3}{1/s} = 0 \Rightarrow v_3 = \frac{v_1 + v_2}{s+2}$

$$I_1 = (s+1)v_1 - sv_2 - \left(\frac{v_1 + v_2}{s+2}\right) = \frac{s^2 + 3s + 1}{s+2}v_1 - \left(\frac{s^2 + 2s + 1}{s+2}\right)v_2$$


$$I_2 = (s+1)v_2 - sv_1 - \left(\frac{v_1 + v_2}{s+2}\right) = -\left(\frac{s^2 + 2s + 1}{s+2}\right)v_1 + \frac{s^2 + 3s + 1}{s+2}v_2$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{s^2 + 3s + 1}{s+2} & -\left(\frac{s^2 + 2s + 1}{s+2}\right) \\ -\left(\frac{s^2 + 2s + 1}{s+2}\right) & \frac{s^2 + 3s + 1}{s+2} \end{bmatrix}$$

Q.

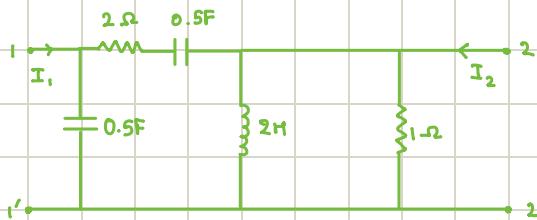

A.

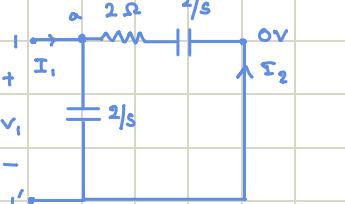For  $y_{11}$  &  $y_{21}$ ,

$$\text{KCL at } a : \frac{v_1}{2/s} + \frac{v_1}{2 + \frac{2}{s}} = I_1$$


$$I_1 = v_1 \left[ \frac{2}{2} + \frac{s}{2s+2} \right]$$

$$= v_1 \left( \frac{2s^2 + 4s}{4s+4} \right)$$

$$= v_1 \left( \frac{s^2 + 2s}{2s+2} \right)$$

$$y_{11} = \frac{s^2 + 2s}{2s+2}$$

$$v_1 = -I_2 \left( 2 + \frac{2}{s} \right) \Rightarrow y_{21} = \frac{-s}{2(s+1)}$$

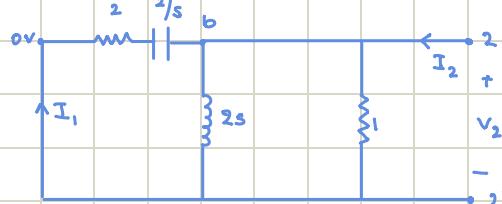
For  $y_{12}$  &  $y_{22}$ ,

$$v_2 = -I_1 \left( 2 + \frac{2}{s} \right) \Rightarrow y_{12} = \frac{-s}{2s+2}$$


KCL at b,

$$\frac{v_2}{2s} + \frac{v_2}{1} + \frac{v_2}{2 + \frac{2}{s}} = I_2$$
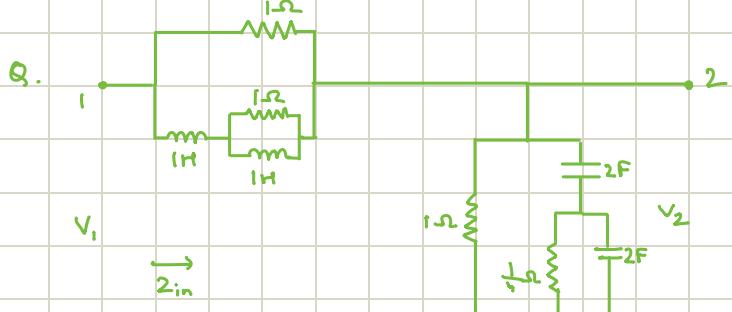
$$\frac{I_2}{v_2} = \frac{1}{2s} + 1 + \frac{s}{2s+2} = \frac{4s^2 + 4s + 2s + 2 + 2s^2}{2s(2s+2)} = \frac{6s^2 + 6s + 2}{4s^2 + 4s}$$



A.

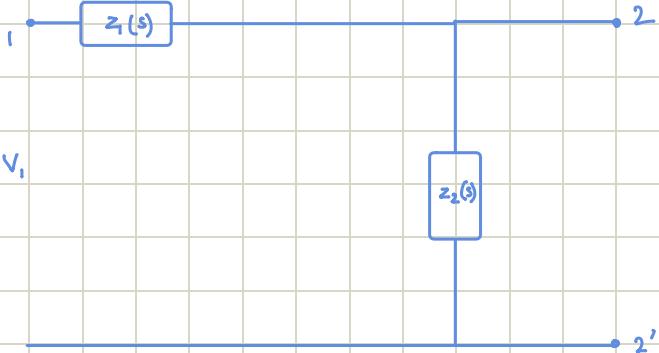

$$\begin{aligned} z_1(s) &= 1 \parallel (s + (1 \parallel s)) \\ &= 1 \parallel \left( s + \frac{s}{s+1} \right) \\ &= 1 \parallel \left( \frac{s^2+2s}{s+1} \right) = \frac{s^2+2s}{s^2+3s+1} \end{aligned}$$

$$\begin{aligned} z_2(s) &= 1 \parallel \left( \frac{1}{2s} + \left( \frac{1}{4} \parallel \frac{1}{2s} \right) \right) \\ &= 1 \parallel \left( \frac{1}{2s} + \left( \frac{1}{4+2s} \right) \right) \\ &= 1 \parallel \left( \frac{4+2s+2s}{2s(4+2s)} \right) \\ &= \frac{1 \times 2+2s}{\frac{s(4+2s)}{s(4+2s)+2+2s}} = \frac{s+1}{s^2+3s+1} \end{aligned}$$

$$z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = z_1(s) + z_2(s) = 1 \Omega$$


$$z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = z_2(s)$$

$$z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = z_2(s)$$

$$z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = z_2(s)$$

Q

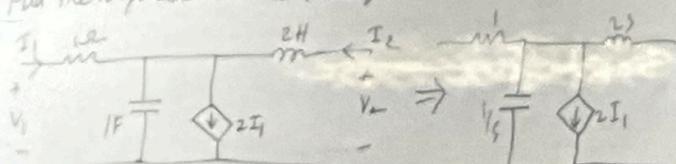Find the h-parameters in the circuit given below




$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

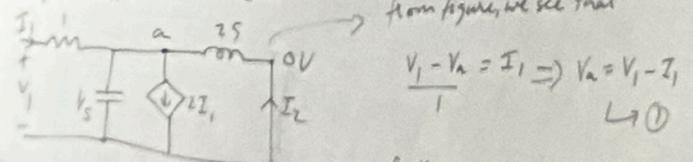To find  $h_{11}$  and  $h_{21}$ , set  $V_2 = 0$



from figure, we see that

$$\frac{V_1 - V_a}{1} = I_1 \Rightarrow V_a = V_1 - I_1$$

further,  $V_a = -2s \times I_2 \rightarrow \textcircled{2}$

KCL at node a

$$-I_1 + \frac{V_a}{1/2s} + 2I_1 + \frac{V_a}{2s} = 0$$

$$\Rightarrow I_1 = -V_a \left[ \frac{1}{2s} + \frac{1}{2s} \right] \Rightarrow V_a = \frac{-2s}{2s^2 + 1}. I_1 \rightarrow \textcircled{1}$$

→ Transmission Parameters (Relation b/w currents & voltages)

$$V_1(s) = A V_2(s) - B I_2(s)$$

$$V_1 = AV_2 - BI_2$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0}$$

Open circuit reverse voltage gain

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

open circuit reverse transfer admittance

$$I_1(s) = C V_2(s) - D I_2(s)$$

$$I_1 = CV_2 - DI_2$$

⇒ Inductance / Capacitances

⇒ Reactances

$$B = -\frac{V_1}{I_2} \Big|_{V_2=0}$$

short circuit reverse transfer circuit impedance

$$D = -\frac{I_1}{I_2} \Big|_{V_2=0}$$

short circuit reverse current gain

$$\text{In } z\text{-parameters, } V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow ③$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow ④$$

To derive transmission parameters in terms of z-parameters

$$V_1 = AV_2 - BI_2 \rightarrow ①$$

$$I_1 = CV_2 - DI_2 \rightarrow ②$$

Divide ① by  $I_1$  & set  $I_2=0$

$$\frac{V_1}{I_1} \Big|_{I_2=0} = A \cdot \frac{V_2}{I_1} \Big|_{I_2=0} - B \cdot \frac{I_2}{I_1} \Big|_{I_2=0}$$

$$Z_{11} = A \cdot Z_{21} \Rightarrow A = \frac{Z_{11}}{Z_{21}}$$

$$\left. \begin{aligned} Z_{11} &= \frac{V_1}{I_1} \Big|_{I_2=0} \\ Z_{21} &= \frac{V_2}{I_1} \Big|_{I_2=0} \\ Z_{12} &= \frac{V_1}{I_2} \Big|_{I_1=0} \\ Z_{22} &= \frac{V_2}{I_2} \Big|_{I_1=0} \end{aligned} \right.$$

Divide ② by  $I_1$  & set  $I_2=0$

$$\frac{I_1}{I_1} \Big|_{I_2=0} = C \cdot \frac{V_2}{I_1} \Big|_{I_2=0} - D \cdot \frac{I_2}{I_1} \Big|_{I_2=0}$$

$$1 = C \cdot Z_{21}$$

$$C = \frac{1}{Z_{21}}$$

Divide ① by  $I_2$  & set  $I_1=0$

$$\frac{V_1}{I_2} \Big|_{I_1=0} = A \cdot \frac{V_2}{I_2} \Big|_{I_1=0} - B \cdot \frac{I_2}{I_2} \Big|_{I_1=0}$$

$$Z_{12} = A \cdot Z_{22} - B \Rightarrow B = \frac{Z_{11} \cdot Z_{22}}{Z_{21}} - Z_{12} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}} \Rightarrow B = \frac{A Z_{22}}{Z_{21}}$$

Divide ② by  $I_2$  & set  $I_1=0$

$$\frac{I_1}{I_2} \Big|_{I_1=0} = C \cdot \frac{V_2}{I_2} \Big|_{I_1=0} - D \cdot \frac{I_2}{I_2} \Big|_{I_1=0}$$

$$0 = C Z_{22} - D \Rightarrow D = \frac{C Z_{22}}{Z_{21}}$$

To derive transmission parameters in terms of admittance parameters

$$V_1 = A V_2 - B I_2 \rightarrow \textcircled{1}$$

$$I_1 = C V_2 - D I_2 \rightarrow \textcircled{2}$$

$$\left| \begin{array}{l} Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \\ Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \\ Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \\ Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \end{array} \right.$$

Divide  $\textcircled{1}$  by  $V_1$  and set  $V_2 = 0$

$$\frac{V_1}{V_1} \Big|_{V_2=0} = A \frac{V_2}{V_1} \Big|_{V_2=0} - B \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$1 = -B y_{21} \Rightarrow B = -\frac{1}{y_{21}}$$

Divide  $\textcircled{2}$  by  $V_1$  and set  $V_2 = 0$

$$\frac{I_1}{V_1} \Big|_{V_2=0} = C \frac{V_2}{V_1} \Big|_{V_2=0} - D \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$y_{11} = 0 - D y_{21} \Rightarrow D = -\frac{y_{11}}{y_{21}}$$

Divide  $\textcircled{1}$  by  $V_2$  and set  $V_1 = 0$

$$\frac{V_1}{V_2} \Big|_{V_1=0} = A \frac{V_2}{V_2} \Big|_{V_1=0} - B \frac{I_2}{V_2} \Big|_{V_1=0}$$

$$0 = A - B y_{22} \Rightarrow A = -\frac{y_{22}}{y_{21}}$$

Divide  $\textcircled{2}$  by  $V_2$  and set  $V_1 = 0$

$$\frac{I_1}{V_2} \Big|_{V_1=0} = C \frac{V_2}{V_2} \Big|_{V_1=0} - D \frac{I_2}{V_2} \Big|_{V_1=0}$$

$$y_{12} = C - D y_{22}$$

$$y_{12} - \frac{y_{11} y_{22}}{y_{21}} = C \Rightarrow C = \frac{\Delta y}{y_{21}}$$

To derive transmission parameters in terms of h-parameters

$$V_1 = A V_2 - B I_2 \rightarrow \textcircled{1}$$

$$I_1 = C V_2 - D I_2 \rightarrow \textcircled{2}$$

Divide  $\textcircled{1}$  by  $I_1$  and set  $V_2 = 0$

$$\frac{V_1}{V_1} \Big|_{V_2=0} = A \frac{V_2}{V_1} \Big|_{V_2=0} - B \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$h_{11} = -B h_{21} \Rightarrow B = -\frac{h_{11}}{h_{21}}$$

Divide  $\textcircled{2}$  by  $I_1$  and set  $V_2 = 0$

$$\frac{I_1}{I_1} \Big|_{V_2=0} = C \frac{V_2}{I_1} \Big|_{V_2=0} - D \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$C = -D h_{21} \Rightarrow D = -\frac{1}{h_{21}}$$

Divide  $\textcircled{1}$  by  $V_2$  and set  $V_1 = 0$

$$\frac{V_1}{V_2} \Big|_{I_1=0} = A \frac{V_2}{V_2} \Big|_{I_1=0} - B \frac{I_2}{V_2} \Big|_{I_1=0}$$

$$h_{12} = A - B \cdot h_{22} \Rightarrow A = -\Delta h$$

Divide  $\textcircled{2}$  by  $V_2$  and set  $V_1 = 0$

$$\frac{I_1}{V_2} \Big|_{I_1=0} = C \frac{V_2}{V_2} \Big|_{I_1=0} - D \frac{I_2}{V_2} \Big|_{I_1=0}$$

$$C = D h_{22} \Rightarrow C = -\frac{h_{22}}{h_{21}}$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

To derive z parameters in terms of h-parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Divide ① by  $I_1$  and set  $V_2 = 0$

$$\frac{V_1}{I_1} \Big|_{V_2=0} = Z_{11} \frac{I_1}{I_1} \Big|_{V_2=0} + Z_{12} \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$h_{11} = Z_{11} + Z_{12} h_{21} \rightarrow ③$$

Divide ① by  $V_2$  and set  $I_1 = 0$

$$\frac{V_1}{V_2} \Big|_{I_1=0} = Z_{11} \frac{I_1}{V_2} \Big|_{I_1=0} + Z_{12} \frac{I_2}{V_2} \Big|_{I_1=0}$$

$$h_{12} = Z_{12} \cdot h_{22} \Rightarrow Z_{12} = \frac{h_{12}}{h_{22}}$$

$$③ \text{ can be written as } Z_{11} = h_{11} - Z_{12} h_{21}$$

$$Z_{11} = h_{11} - \frac{h_{21} h_{12}}{h_{22}} = \frac{\Delta h}{h_{22}}$$

Divide ② by  $V_2$  and set  $I_1 = 0$

$$\frac{V_2}{V_2} \Big|_{I_1=0} = Z_{21} \frac{I_1}{V_2} \Big|_{I_1=0} + Z_{22} \frac{I_2}{V_2} \Big|_{I_1=0}$$

$$Z_{22} = \frac{1}{h_{22}}$$

Divide ② by ① and set  $V_2 = 0$

$$\frac{V_2}{V_1} \Big|_{V_2=0} = Z_{21} \frac{I_1}{I_1} \Big|_{V_2=0} + Z_{22} \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$Z_{21} = -Z_{22} h_{21} \Rightarrow Z_{21} = -\frac{h_{21}}{h_{22}}$$

Condition for reciprocity :  $Z_{12} = Z_{21}$

$$\frac{h_{12}}{h_{22}} = -\frac{h_{21}}{h_{22}} \Rightarrow h_{12} = -h_{21}$$

Condition for symmetry :  $Z_{11} = Z_{22}$

$$\frac{\Delta h}{h_{22}} = \frac{1}{h_{22}} \Rightarrow \Delta h = 1$$

$$h_{11} h_{22} - h_{12} h_{21} = 1$$

$$\frac{V_1}{V_2} \Big|_{I_1=0} = Z_{11} \frac{I_1}{V_2} \Big|_{I_1=0} + Z_{12} \frac{I_2}{V_2} \Big|_{I_1=0}$$

$$h_{12} = Z_{12} \cdot h_{22} \Rightarrow Z_{12} = \frac{h_{12}}{h_{22}}$$


③ can now be rewritten as

$$Z_{11} = h_{11} - Z_{12} h_{21}$$

Q.




Find A, B, C &amp; D

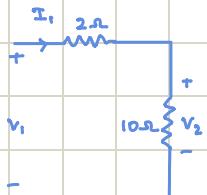A. Set  $I_2 = 0$  to find A & C

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{12}{10}$$

$$V_2 = \frac{10V_1}{10+2} = \frac{10V_1}{12}$$

$$10I_1 = V_2 \Rightarrow C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{1}{10} \text{ n}$$

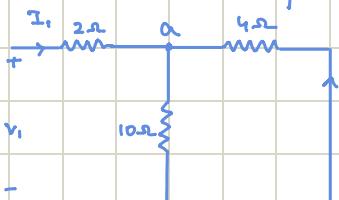Set  $V_2 = 0$  to find B and D

$$B = -\frac{V_1}{I_2} \Big|_{V_2=0}$$

$$\text{and } D = -\frac{I_1}{V_2} \Big|_{V_2=0}$$

$$I_1 = \frac{V_1 - V_a}{2}$$

By KCL at a

$$I_2 = -\frac{V_a}{4}$$

$$\frac{V_a - V_1}{2} + \frac{V_a}{10} + \frac{V_a}{4} = 0$$

$$\frac{V_1}{2} = V_a \left( \frac{1}{2} + \frac{1}{4} + \frac{1}{10} \right)$$

$$= V_a \left( \frac{10+5+2}{20} \right) = 17 \frac{V_a}{20} \Rightarrow V_a = \frac{10V_1}{17}$$

$$I_1 = \frac{V_1 - 5V_1}{2} = \frac{7V_1}{34}$$


$$I_2 = -\frac{10V_1}{17}$$

$$B = \frac{-V_1}{-\frac{10V_1}{17}} = 1.7$$

$$D = \frac{-\frac{7V_1}{34}}{\frac{-10V_1}{17}} = \frac{7}{20}$$

Q. Determine T-parameters of the following parameters

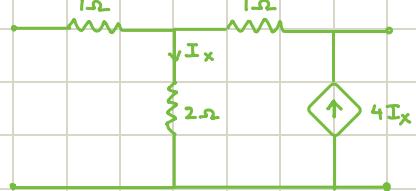Is the network reciprocal or symmetrical?



$$A. \text{ Let } V_a = 2I_x$$

$$\text{KCL at } a : \frac{V_a - V_1}{1} + \frac{V_a}{2} + \frac{V_a - V_2}{1} = 0 \rightarrow ①$$

$$\text{KCL at } b : \frac{V_2 - V_a}{1} = 2V_a \Rightarrow V_a = \frac{V_2}{3} \rightarrow ②$$


$$\text{Using } ① \text{ & } ② \Rightarrow \frac{V_2}{3} - V_1 + \frac{V_2}{6} + \frac{V_2}{3} - V_2 = 0 \Rightarrow V_1 = \left[ \frac{1}{3} + \frac{1}{6} + \frac{1}{3} + -1 \right] V_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = -\frac{1}{6}$$

$$\text{From figure, } \frac{V_1 - V_a}{1} = I_1 \rightarrow ③$$

$$③ \text{ can be written as } AV_2 - \frac{V_2}{3} = I_1$$

$$V_2 \left[ -\frac{1}{6} - \frac{1}{3} \right] = I_1 \Rightarrow C = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -\frac{1}{2} s$$

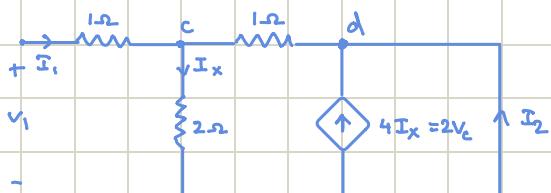

$$\text{KCL at } c, \frac{V_c - V_1}{1} + \frac{V_c}{2} + \frac{V_c - 0}{1} = 0$$

$$\text{KCL at } d, \frac{0 - V_c}{1} = 2V_c + I_2$$

eliminate  $V_c$  from ③ and ④

$$V_1 = \frac{5V_c}{2} = \frac{5}{2} \left( -\frac{I_2}{3} \right)$$

$$\text{or } B = \left. \frac{-V_1}{I_2} \right|_{V_2=0} = \frac{5}{6} \Omega$$

$$\text{From figure, } \frac{V_1 - V_c}{1} = I_1 \rightarrow ⑤$$

We can rewrite ⑤ as  $-B I_2 - \left( -\frac{I_2}{3} \right) = I_1$

$$-\frac{5}{6} I_2 + \frac{I_2}{3} = I_1 \Rightarrow \frac{I_1}{I_2} = -\frac{1}{2}$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$D = \left. \frac{-I_1}{I_2} \right|_{V_2=0} = \frac{1}{2}$$