




1. Basics

Active Elements → Supplies energy (current leaves +ve terminal)
 ex: Voltage/ current Sources

Passive Elements → Absorbs energy (current enters +ve terminal)

- $I = \frac{Q}{t}$ (or) $\frac{dq}{dt}$ unit : A (or) C/s
 \hookrightarrow D.C \hookrightarrow AC

- $V = \frac{W}{Q}$ unit : V (or) J/C

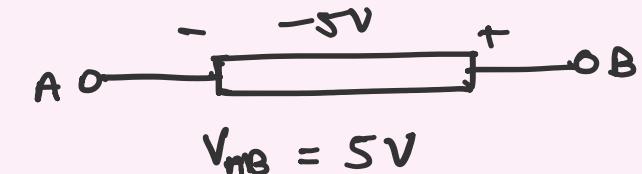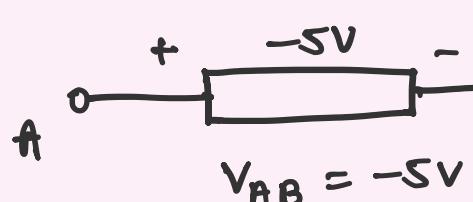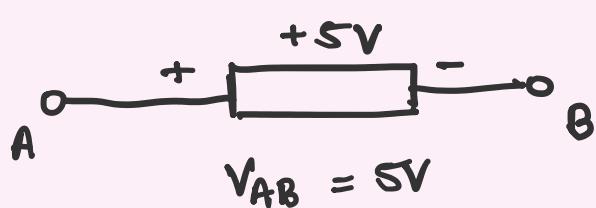


- $P = VI$ unit : W (or) VA

- $V = IR$ (Ohm's Law) ; $G = \frac{1}{R}$
 \downarrow Unit : V $\rightarrow R = \rho \frac{l}{A}$ \rightarrow Unit : $\Omega = \frac{1}{S}$

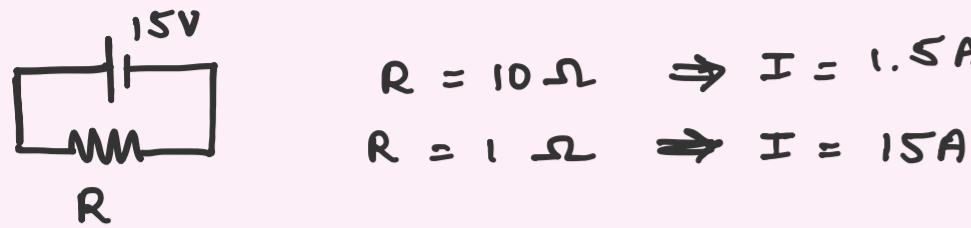
2. Active Elements and Kirchoff Laws

Ideal Voltage Source


- Independant of current flowing through it
- Current depends on circuit




Practical Voltage Source

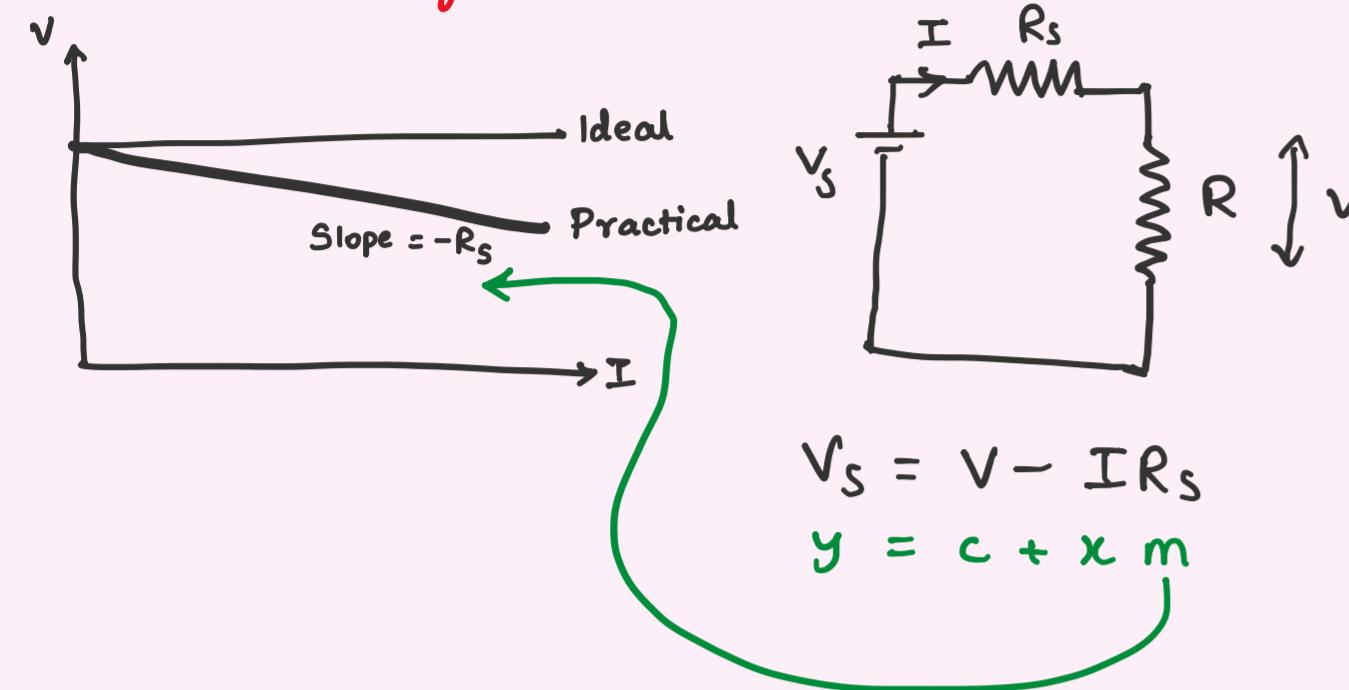

KCL

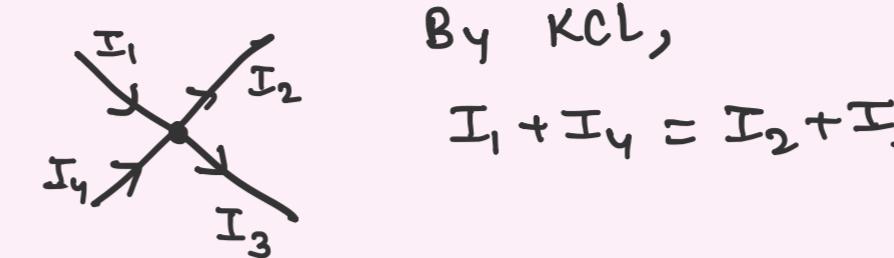

KVL

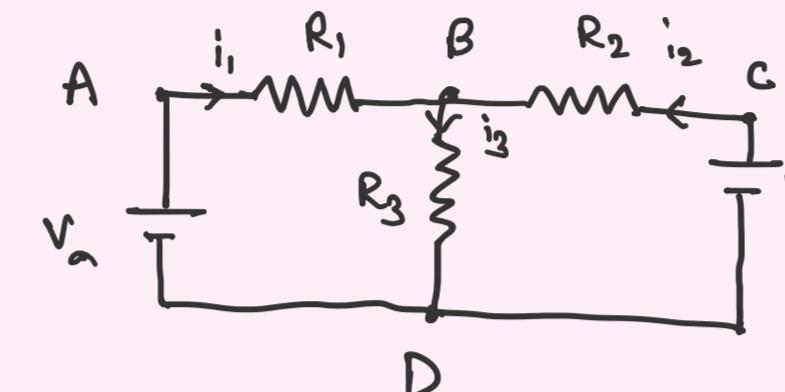


$$\text{Loop ABDA, } V_a - i_1 R_1 - i_3 R_3 = 0$$

$$\text{Loop ACDA, } V_a - i_1 R_1 + i_2 R_2 - V_b = 0$$




$$\text{Loop BCDB, } V_b - i_2 R_2 - i_3 R_3 = 0$$

Ideal Current Source

- Independant of Voltage across it

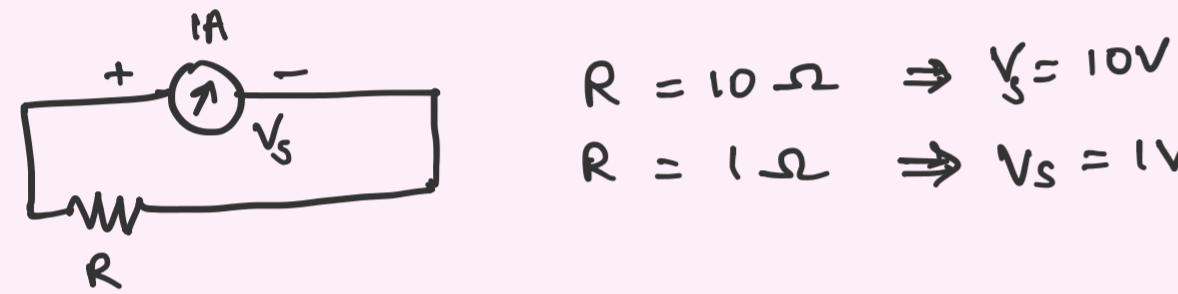

Practical Current Source

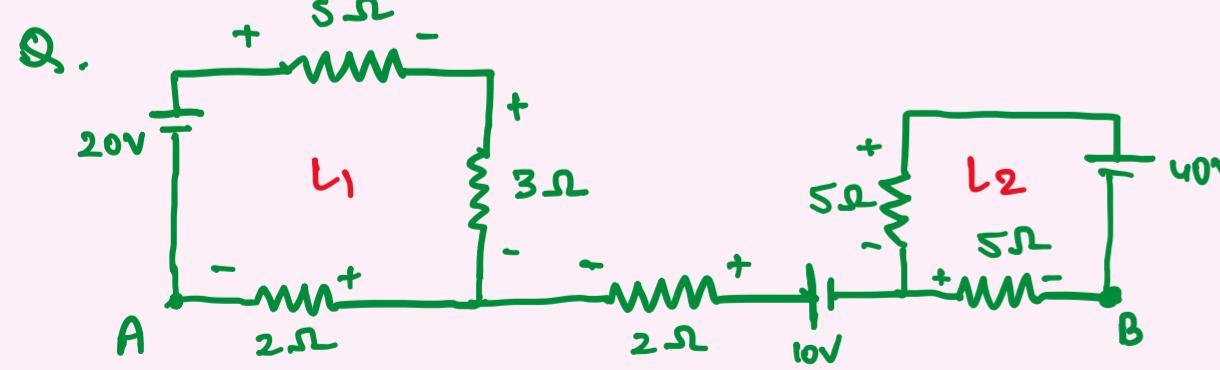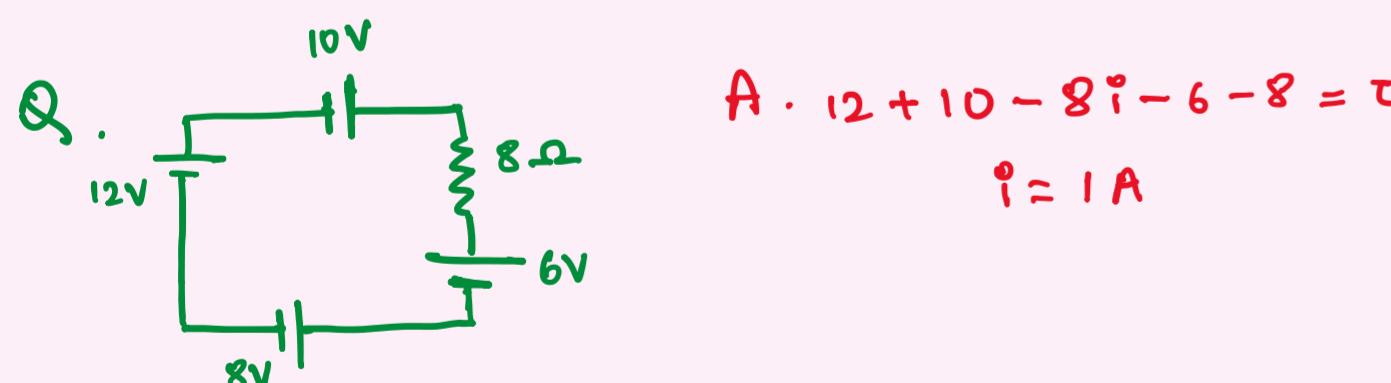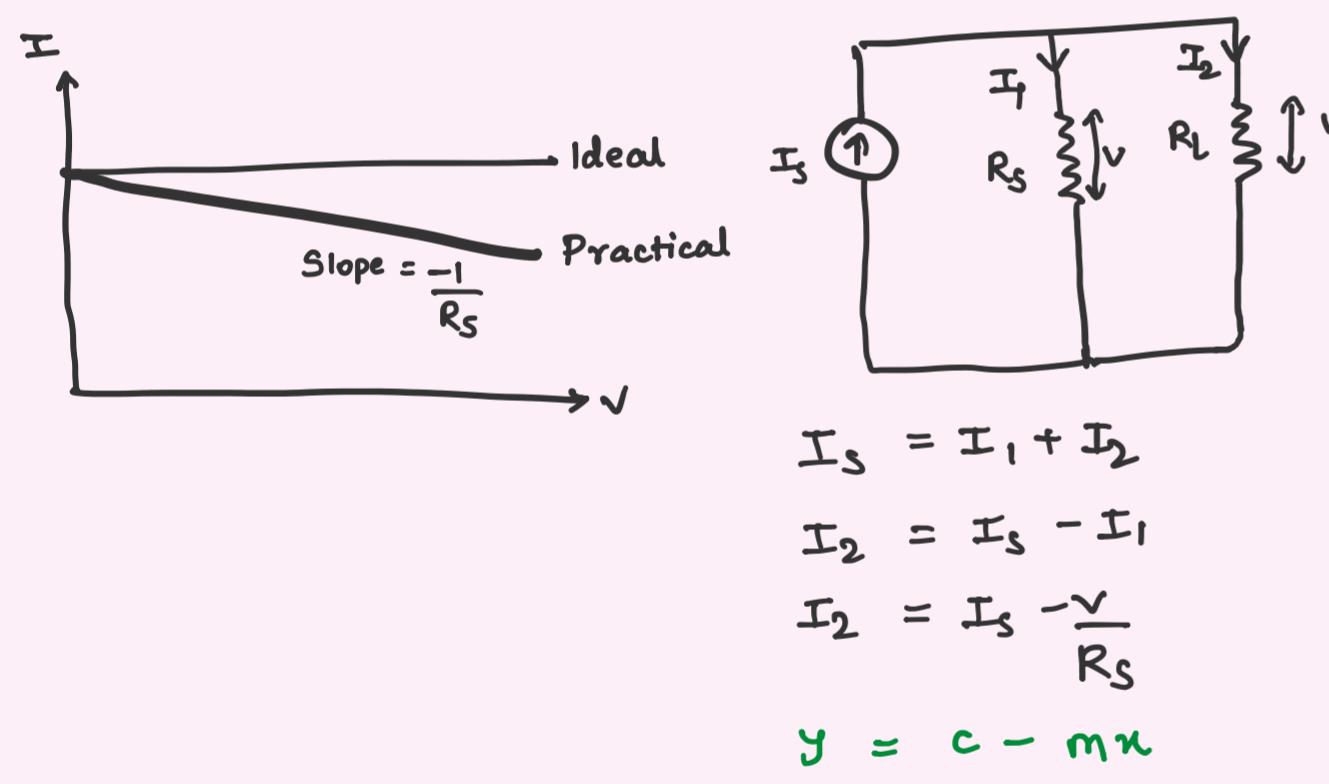

A. $I_1 \Rightarrow 20 - 5i_1 - 3i_1 - 2i_1 = 0 \Rightarrow i_1 = 2A$



$I_2 \Rightarrow 40 - 5i_2 - 5i_2 = 0 \Rightarrow i_2 = 4A$

$i_3 = 0$

$V_{AB} + 2i_1 + 2i_3 - 10 - 5i_2 = 0$

$V_{AB} + 4 + 0 - 10 - 20 = 0$

$V_{AB} = 26V$

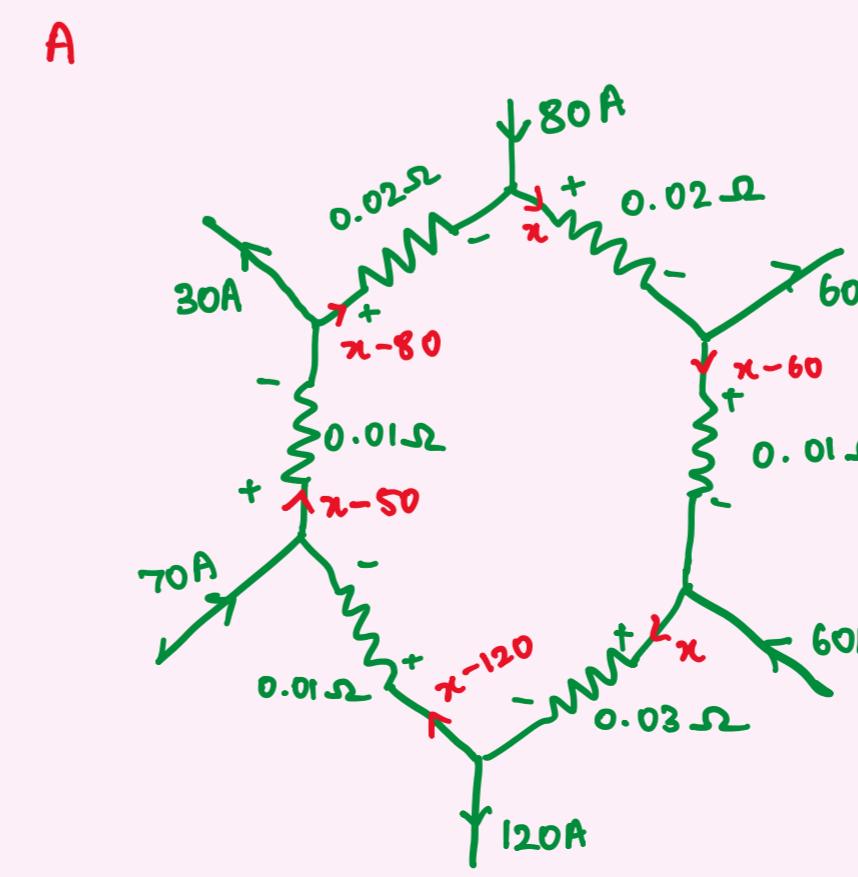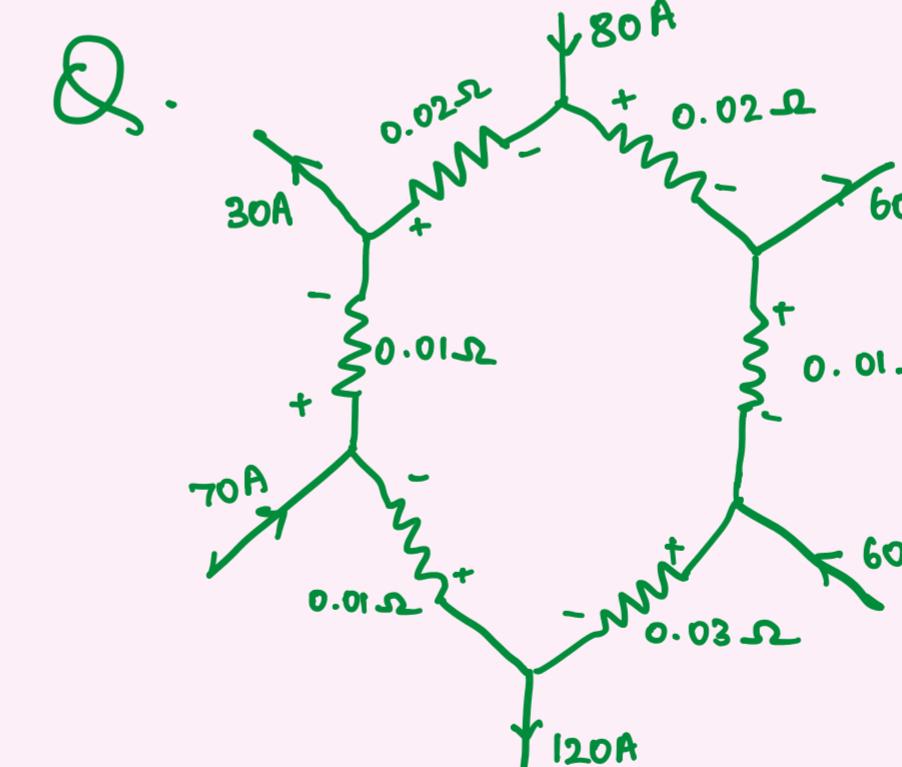

$$-0.02(x) - 0.01(x-60) - 0.03(x) - 0.01(x-120) - 0.01(x-50) - 0.02(x-80) = 0$$


$$0.1x = 0.6 + 1.2 + 0.5 + 1.6$$

$$0.1x = 3.9$$

$$x = 39A$$

3. Voltage, Current Division Rule and Open & Closed Circuit

Voltage Division Rule

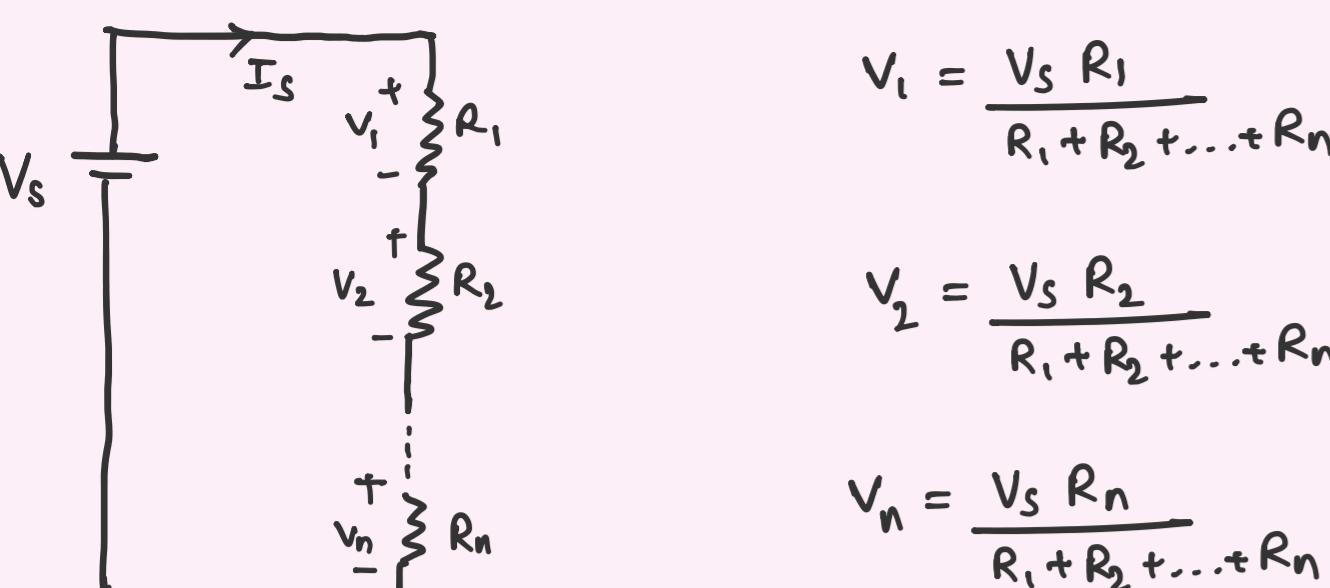


$$V_1 = \frac{V_s R_1}{R_1 + R_2 + \dots + R_n}$$

$$I_S = \frac{V_s}{R_1 + R_2 + \dots + R_n}$$


$$V_2 = \frac{V_s R_2}{R_1 + R_2 + \dots + R_n}$$

$$V_n = \frac{V_s R_n}{R_1 + R_2 + \dots + R_n}$$


Open Circuit

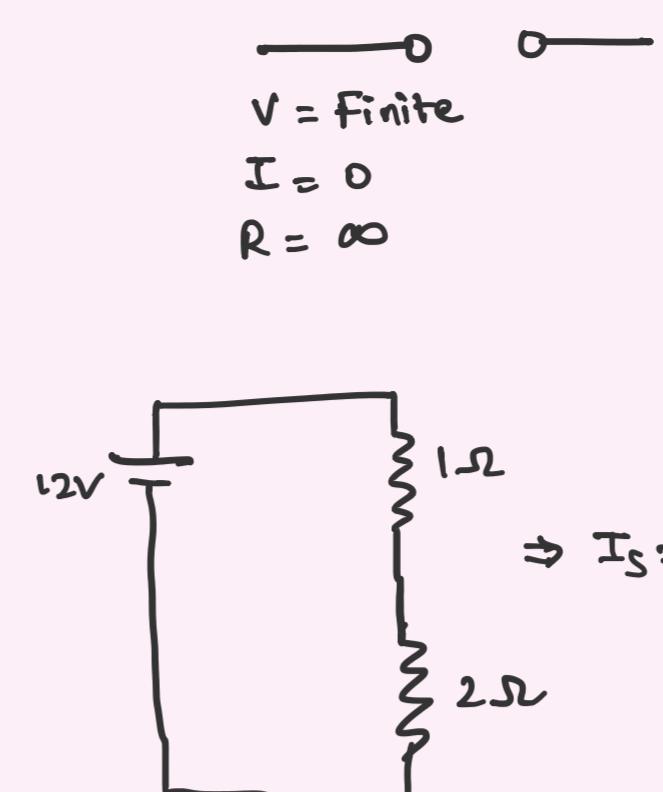

Closed Circuit

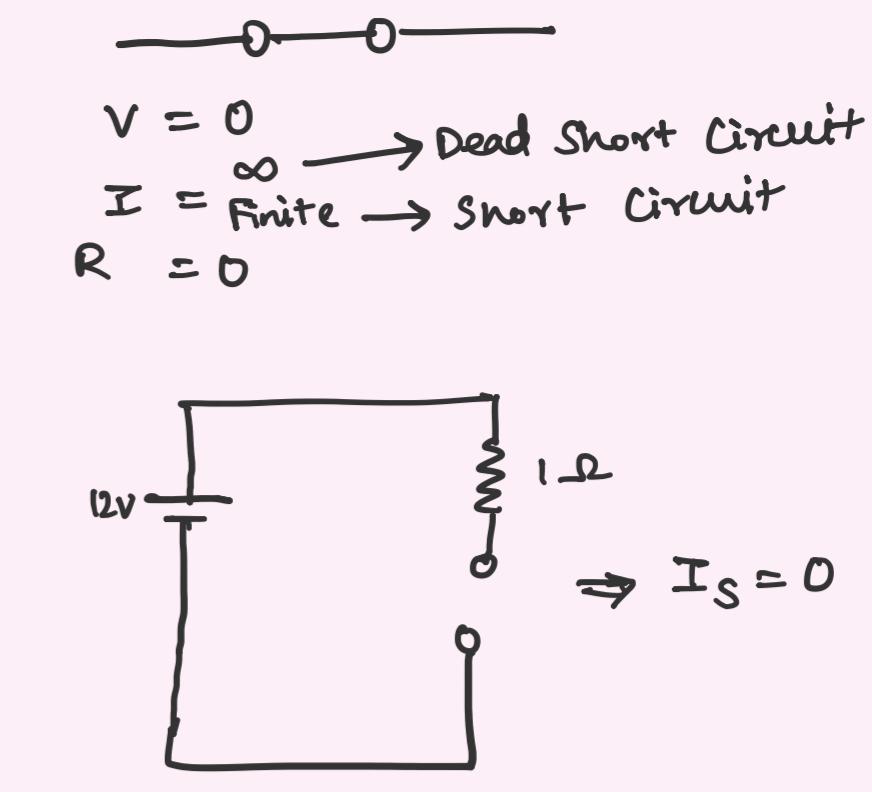


Current Division Rule

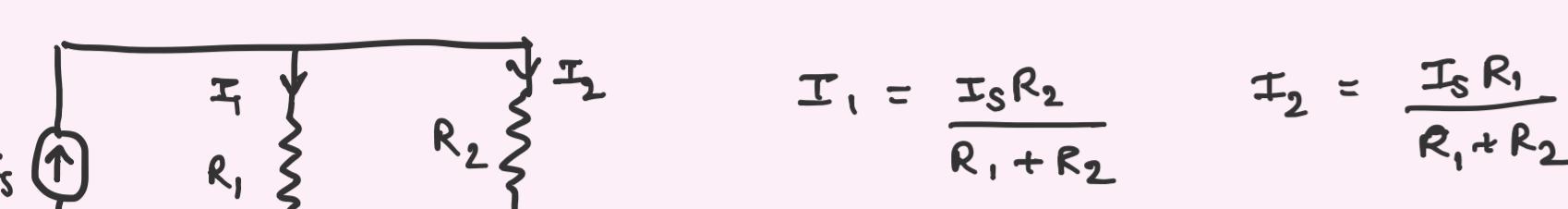




$$I_1 = \frac{I_s R_2}{R_1 + R_2}$$

$$I_2 = \frac{I_s R_1}{R_1 + R_2}$$

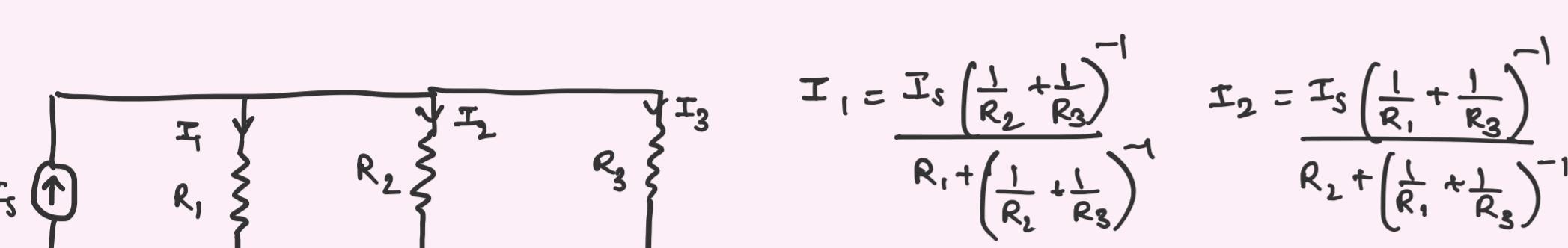

$$I_1 = \frac{I_s \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}}{R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}}$$
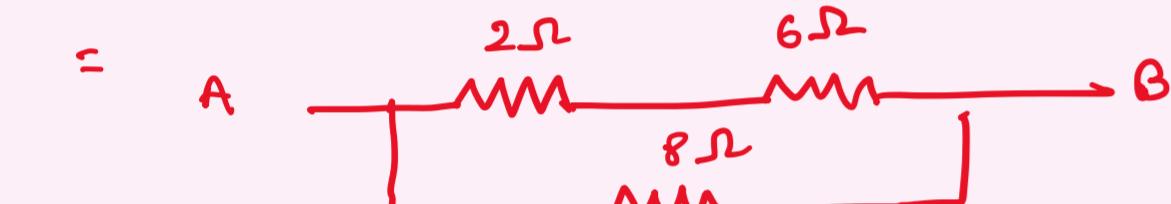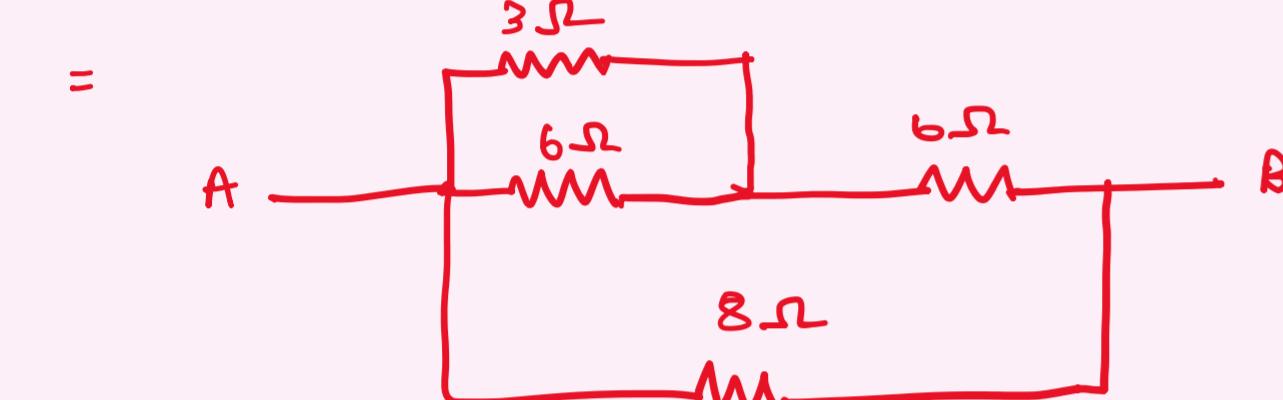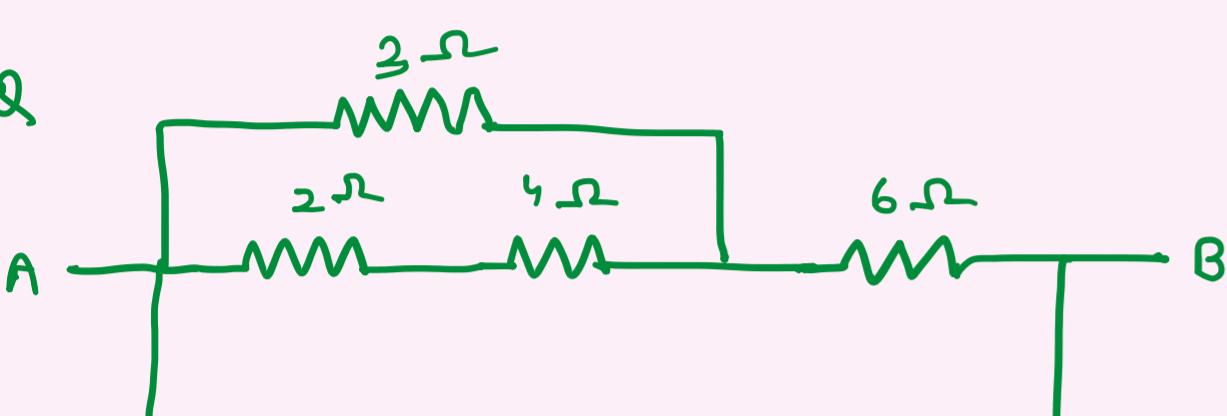
$$I_2 = \frac{I_s \left(\frac{1}{R_1} + \frac{1}{R_3} \right)^{-1}}{R_2 + \left(\frac{1}{R_1} + \frac{1}{R_3} \right)^{-1}}$$



$$= A - \frac{10\Omega}{B}$$


Q. i) $R_a = \infty$ & $R_b = \infty$

ii) $R_a = 0$ & $R_b = \infty$

iii) $R_a = \infty$ & $R_b = 0$

iv) $R_a = 0$ & $R_b = 0$

Find R_{eq} b/w X & Y

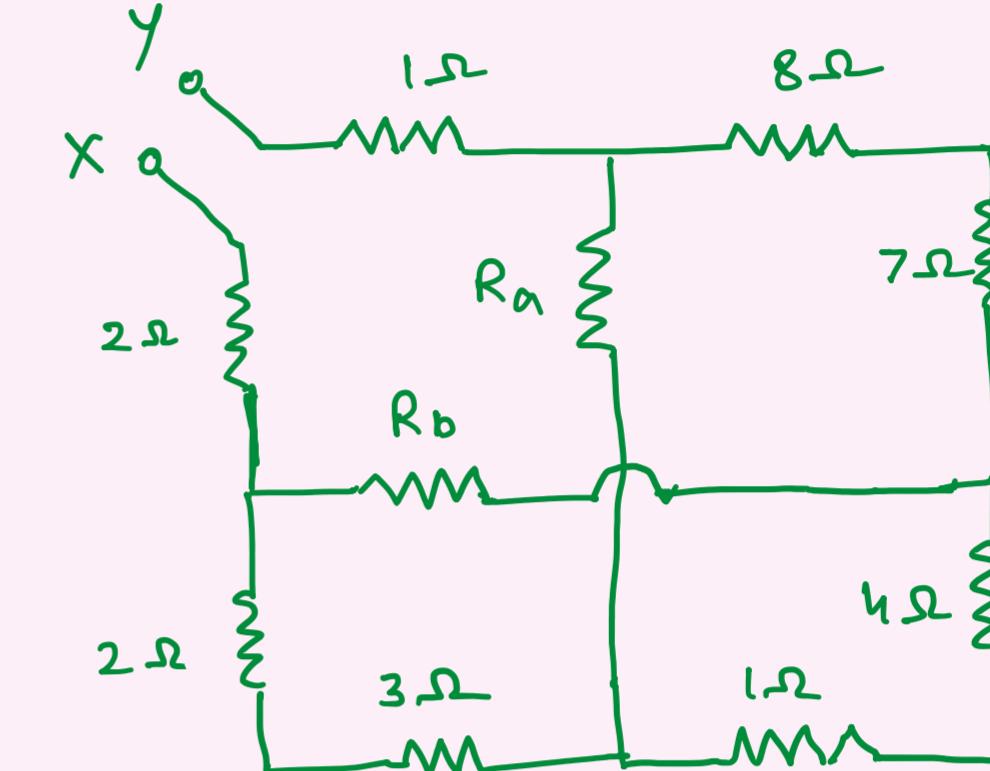



$$A. i) \frac{2}{X} \frac{2}{2} \frac{3}{3} \frac{1}{1} \frac{4}{7} \frac{7}{8} \frac{1}{1} Y = 28\Omega$$

$$ii) \frac{2}{X} \frac{2}{2} \frac{3}{3} \frac{1}{1} \frac{4}{7} \frac{7}{8} Y = 8\Omega$$


$$iii) \frac{2}{X} \frac{7}{7} \frac{8}{8} \frac{1}{1} Y = 18$$

$$iv) \frac{2}{2} \frac{5}{5} \frac{15}{15} \frac{1}{1} Y = 5.14\Omega$$

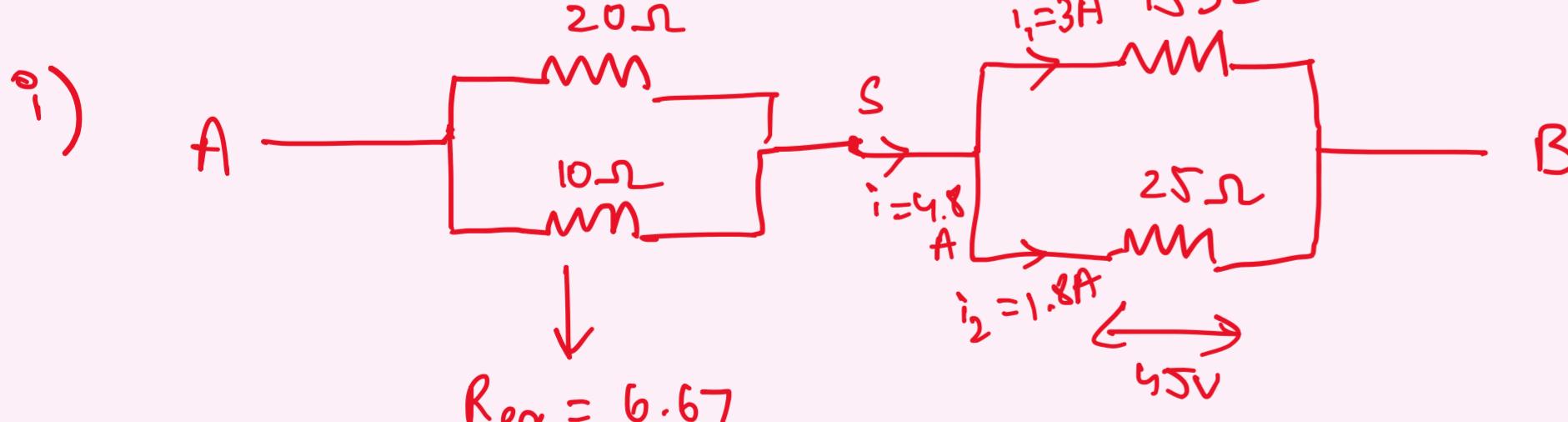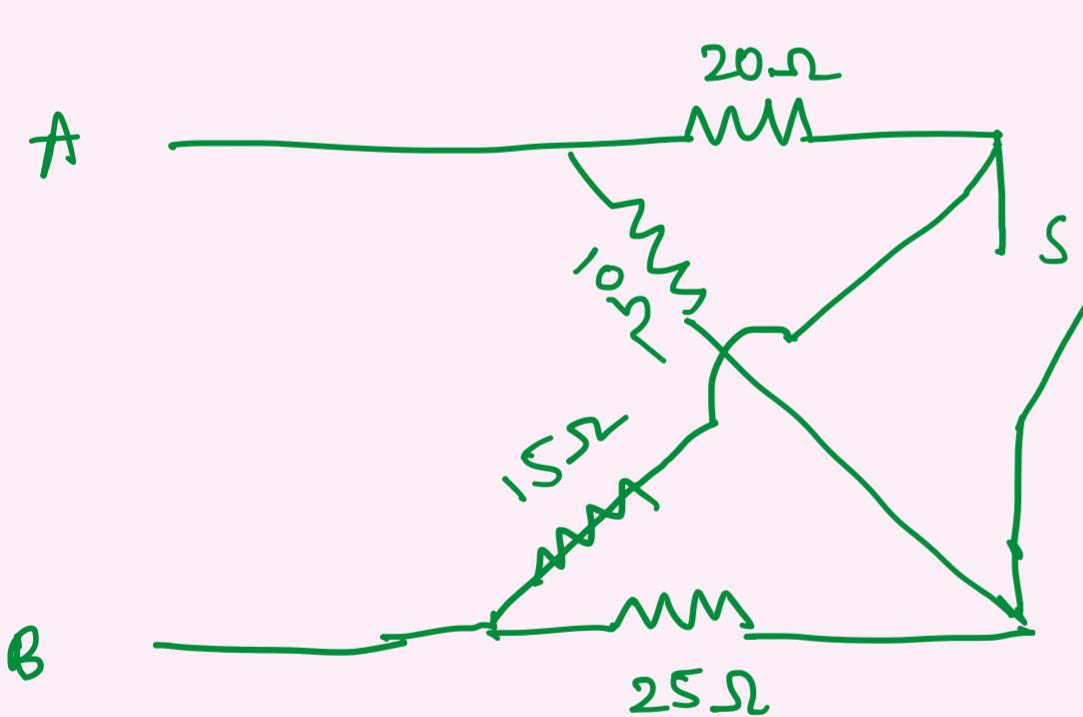Q. Find V_{AB} , if current thru 15Ω resistor is 3A when switch S is i) closed
ii) open



$$V = V_1 + V_2 = 32 + 45 = 77V$$

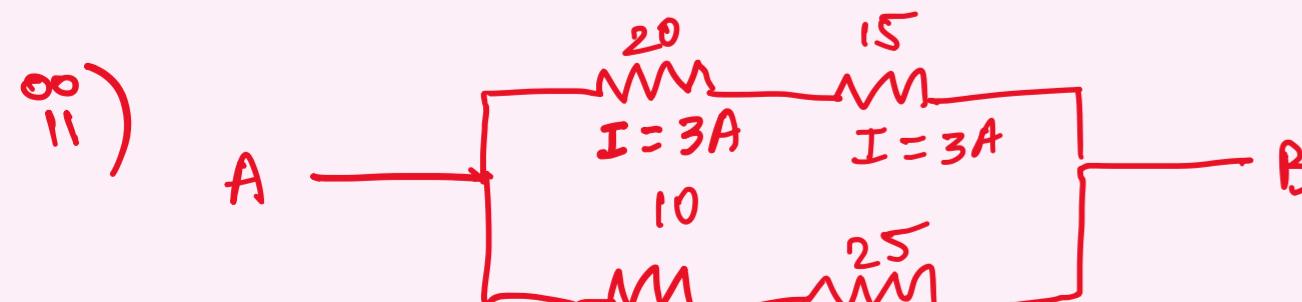

$$V_1 = 20 \times 3 = 60V$$


$$V_2 = 15 \times 3 = 45V$$

$$V_1 + V_2 = 105V \Rightarrow \text{First } 1^{\text{st}} \text{ wire} = 105V$$

Since they are parallel, both will be 105V

Q. Find V_1, V_2, P

Given $I_1 = 5mA$ $I_2 = 3mA$

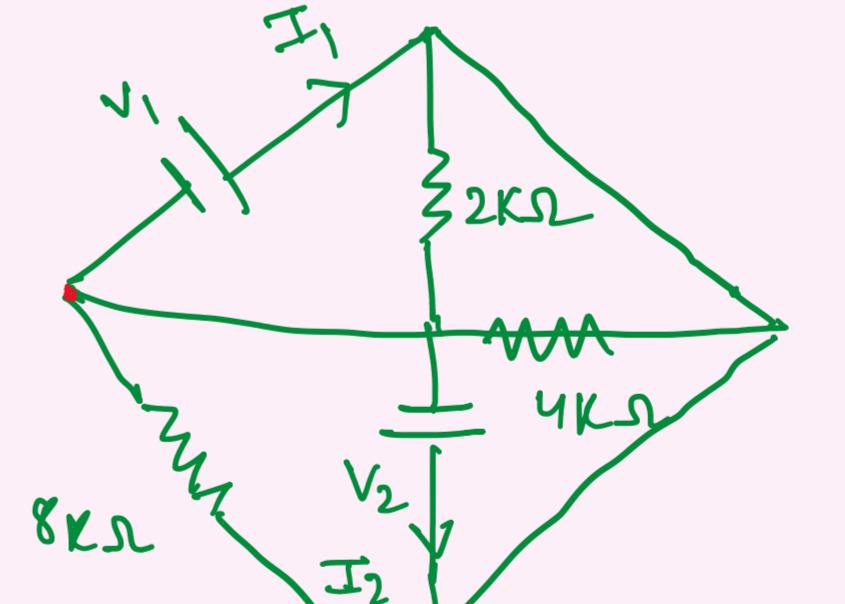

$$R_{eq} = \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right)^{-1}$$


$$= 1.142 k\Omega$$

$$V = 8 \times 1.142 = 9.142V$$

$$P_{(2)} = \frac{V^2}{R_1} = \frac{(9.142)^2}{2 \times 10^3} = 0.041W$$




$$P_{(4)} = \frac{V^2}{R_2} = \frac{(9.142)^2}{4 \times 10^3} = 0.020W$$
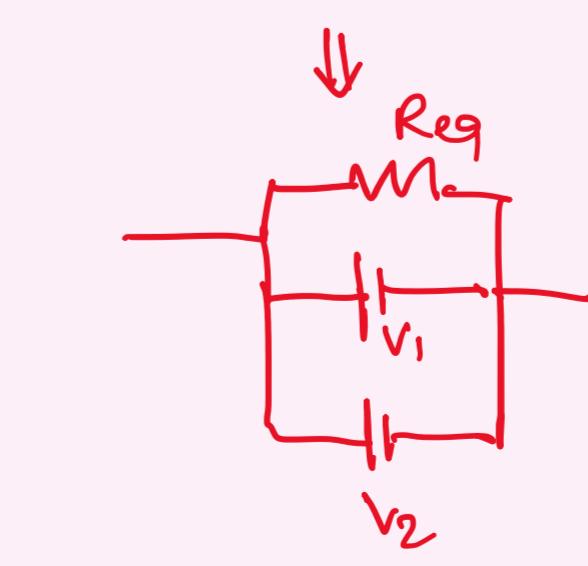
$$P_{(8)} = \frac{V^2}{R_3} = \frac{(9.142)^2}{8 \times 10^3} = 0.01W$$



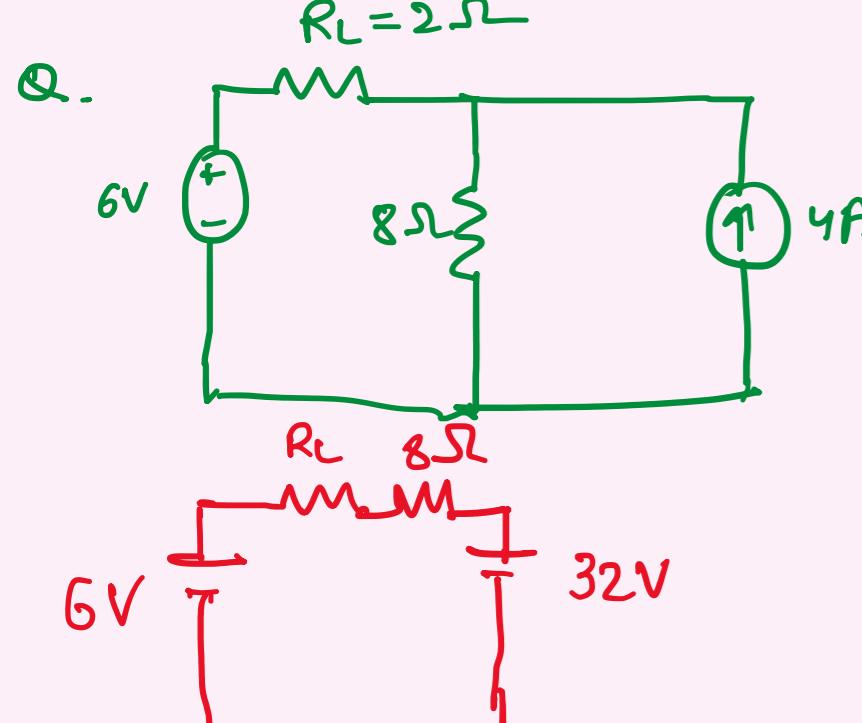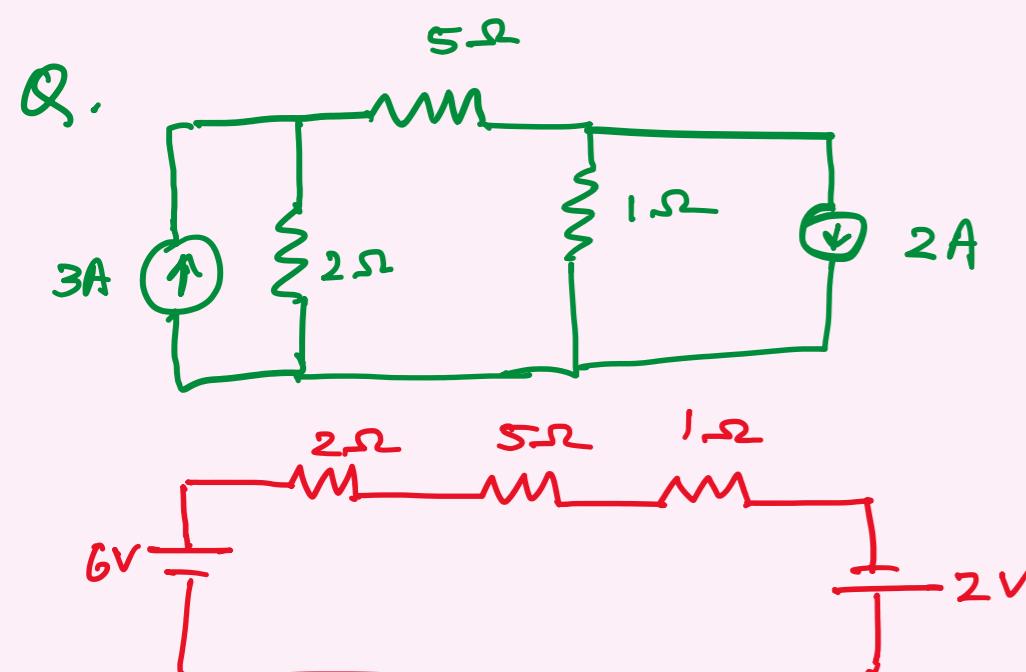
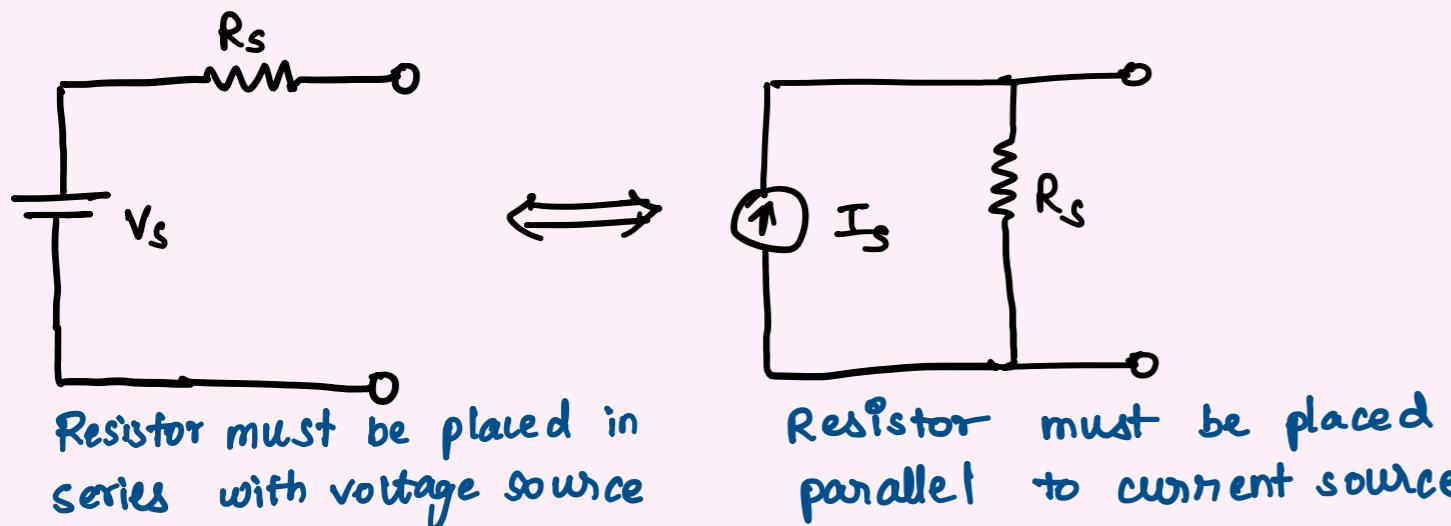
4. Source transformation

- Practical voltage source can be transformed to practical current source & vice versa




$$26 = 10i$$

$$2.6A = i$$

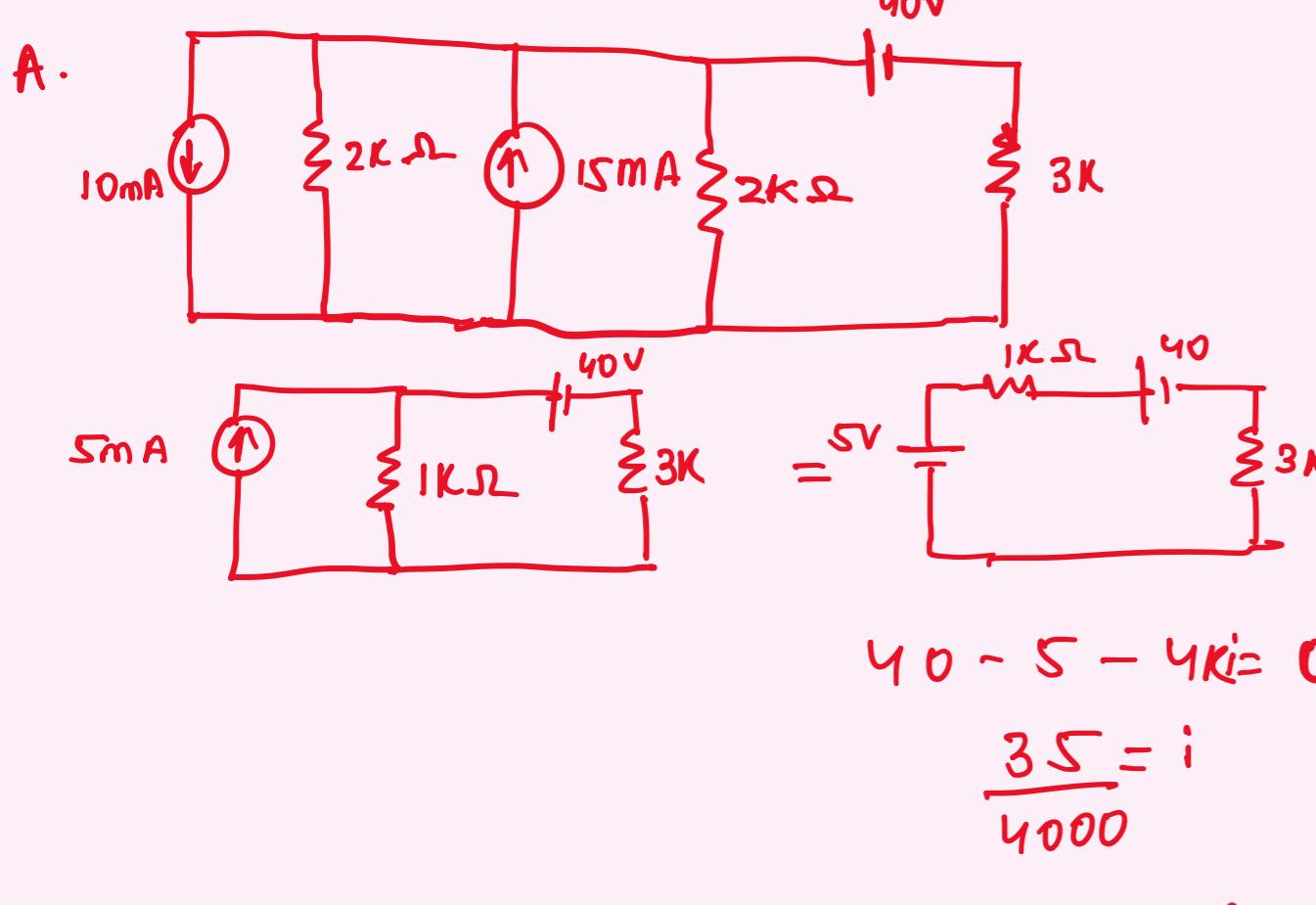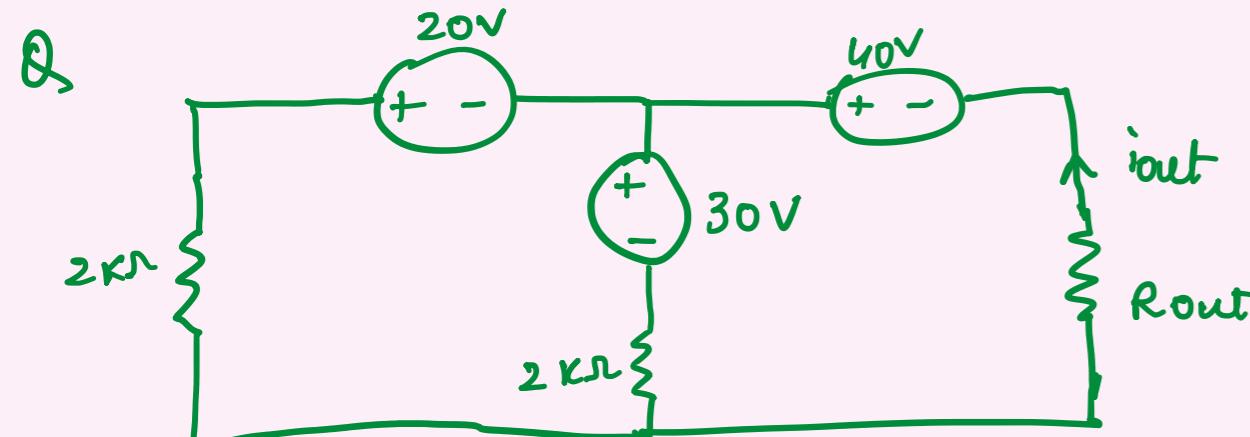

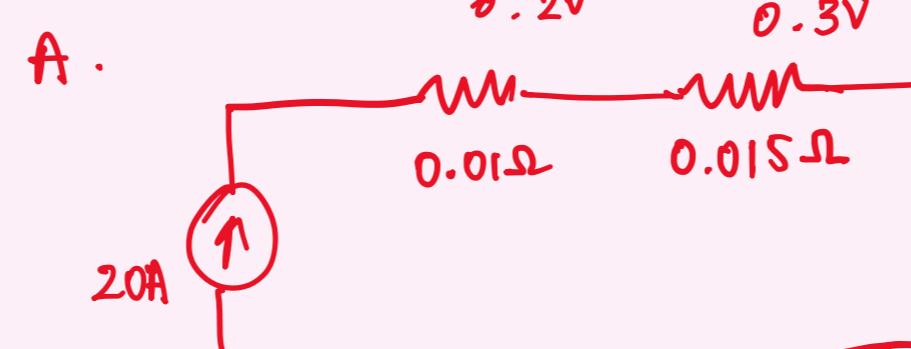Q. A current of 20A flows through 2 ammeters A & B joined in series. Across A, the potential diff is 0.2V & across B it is 0.3V. Find how same current divides b/w A & B when joined in parallel



$$i_1 = \frac{20 \times 0.015}{0.025} = 12A$$

$$i_2 = \frac{20 \times 0.012}{0.025} = 8A$$

Q. Battery of EMF 12V & internal resistance = 0.05Ω supplies power to load resistance R_L . Determine % change in voltage as load resistance varies from 10Ω to 100Ω

A. i)

$$V_{(10)} = \frac{12 \times 10}{10 + 0.05} = 11.94$$

ii)


$$V_{(100)} = \frac{12 \times 100}{100 + 0.05} = 11.99$$

$$\% \text{ change} = \frac{11.99 - 11.94}{11.94} \times 100 = 0.42\%$$

Q. 2 batteries connected in 1^{st} & load of 10Ω connected across them. Battery A = 9V & internal resistance = 0.5Ω . Battery B = 12V & internal resistance = 1Ω .

- Find R_L magnitude & direction
- Find current supplied by both batteries
- Potential diff across R_L

A.

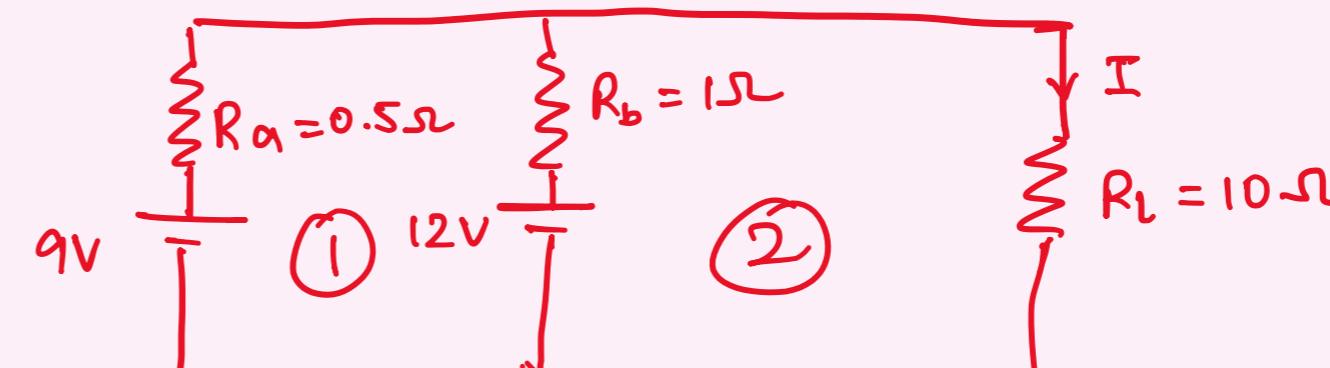

$$\textcircled{1} \Rightarrow 9V - 0.5i_1 + i_2 - 12V = 0$$

$$3 = i_2 - \frac{i_1}{2}$$

$$\textcircled{2} \Rightarrow i_2 - i_1 - 10(i_1 + i_2) = 0$$

$$12 = 10i_1 + 11i_2$$

$$i_1 = -\frac{42}{31}, \quad i_2 = \frac{72}{31}$$

$$i = i_1 + i_2 = 0.97A$$

$$V_L = iR_L = 0.97 \times 10 = 9.7V$$

i) $R_L = 10\Omega$ Clockwise

ii) $i_A = -1.35A$ $i_B = 2.32A$


iii) $V_L = 9.7V$

6. Mesh Analysis

→ Most Fundamental loop in a circuit



Steps:

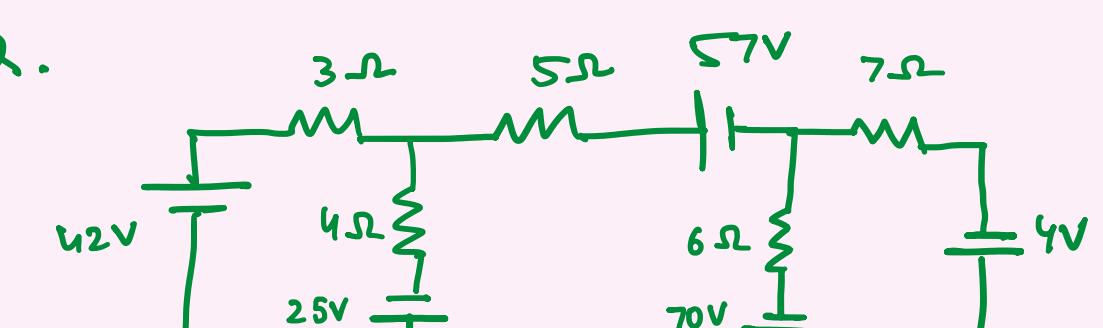- 1) Find all mesh
- 2) Apply KVL in clockwise & give a current to each mesh
- 3) Solve simultaneous equations



$$\begin{aligned} A. \quad & 7I_1 - 4I_2 - 0I_3 = 25 + 4 \\ & -4I_1 + 15I_2 - 6I_3 = -70 - 25 - 57 \\ & -0I_1 - 6I_2 + 13I_3 = 4 + 70 \\ \hline & I_1 = 5, \quad I_2 = -8, \quad I_3 = 2 \end{aligned}$$
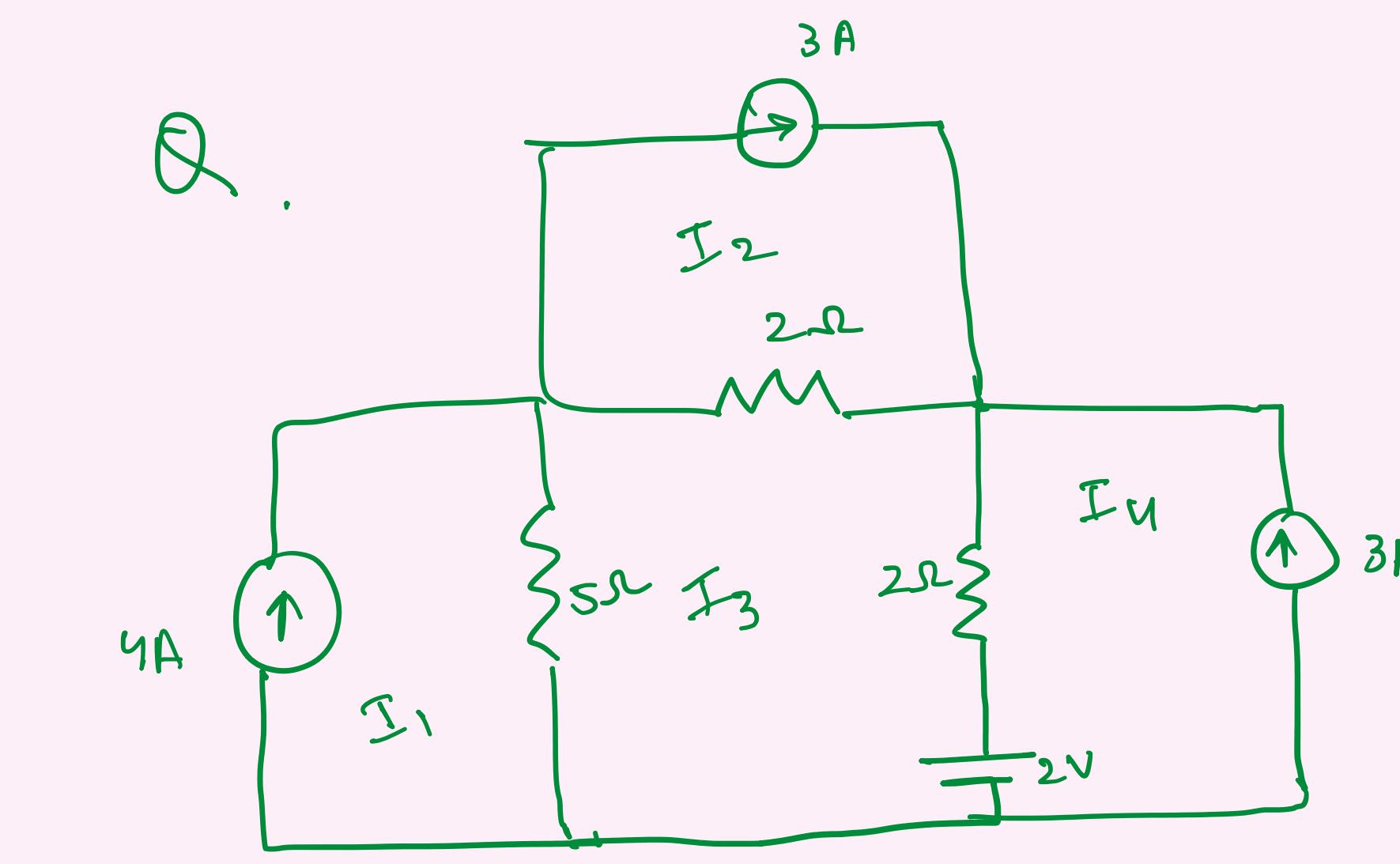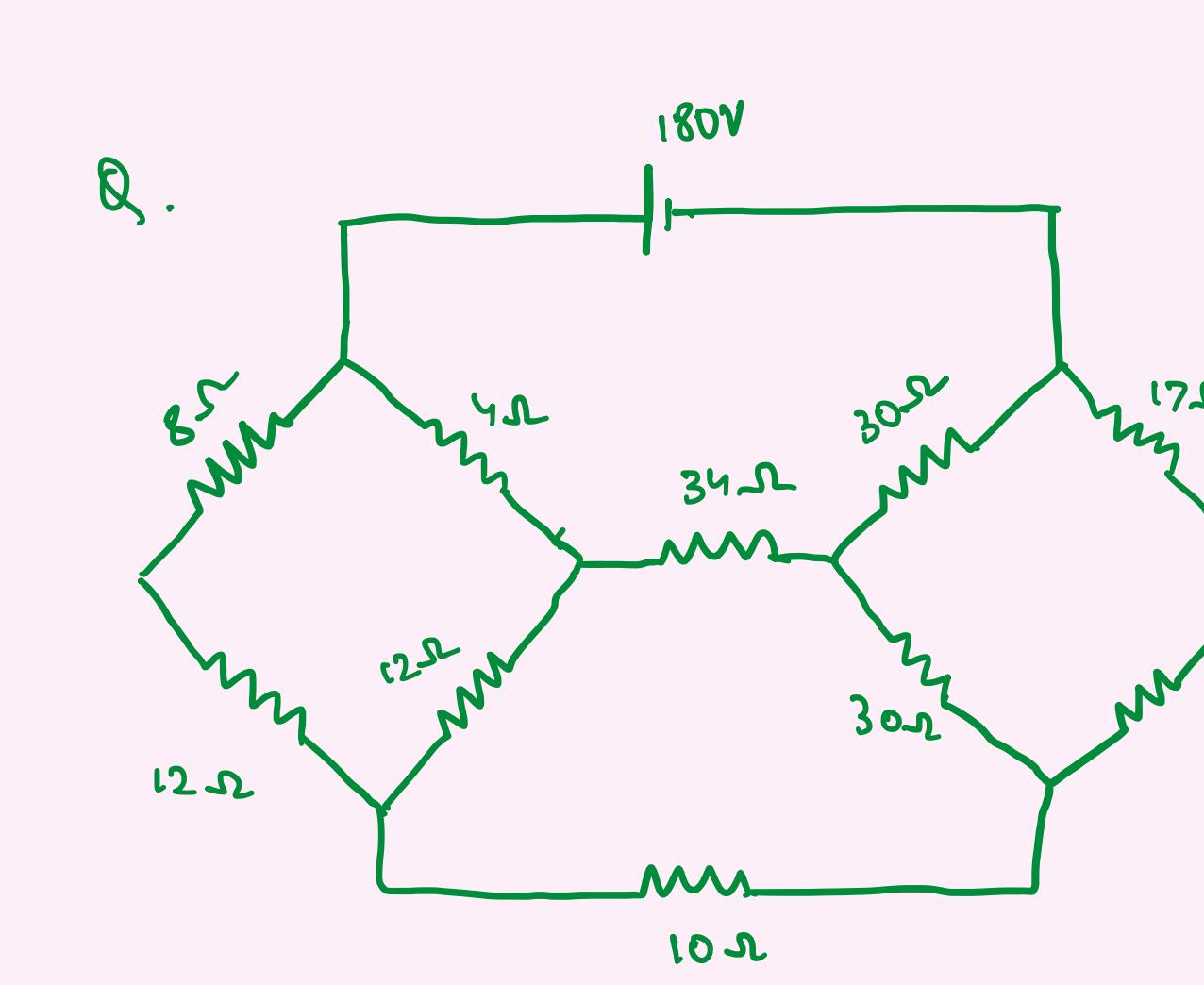
$$\begin{aligned} I \text{ thru } 6\Omega &= I_3 - I_2 \\ &= 2 - (-8) \\ &= 10 \text{ A} \end{aligned}$$







$$I_1 = 4 \text{ A}$$

$$I_2 = 3 \text{ A}$$

$$\begin{aligned} 5I_1 - 2I_2 + 9I_3 - 2I_4 &= -2 \\ I_4 &= 3 \text{ A} \end{aligned}$$

$$\begin{aligned} \Rightarrow 20 - 6 + 9I_3 + 6 &= -2 \\ I_3 &= 2 \text{ A} \end{aligned}$$

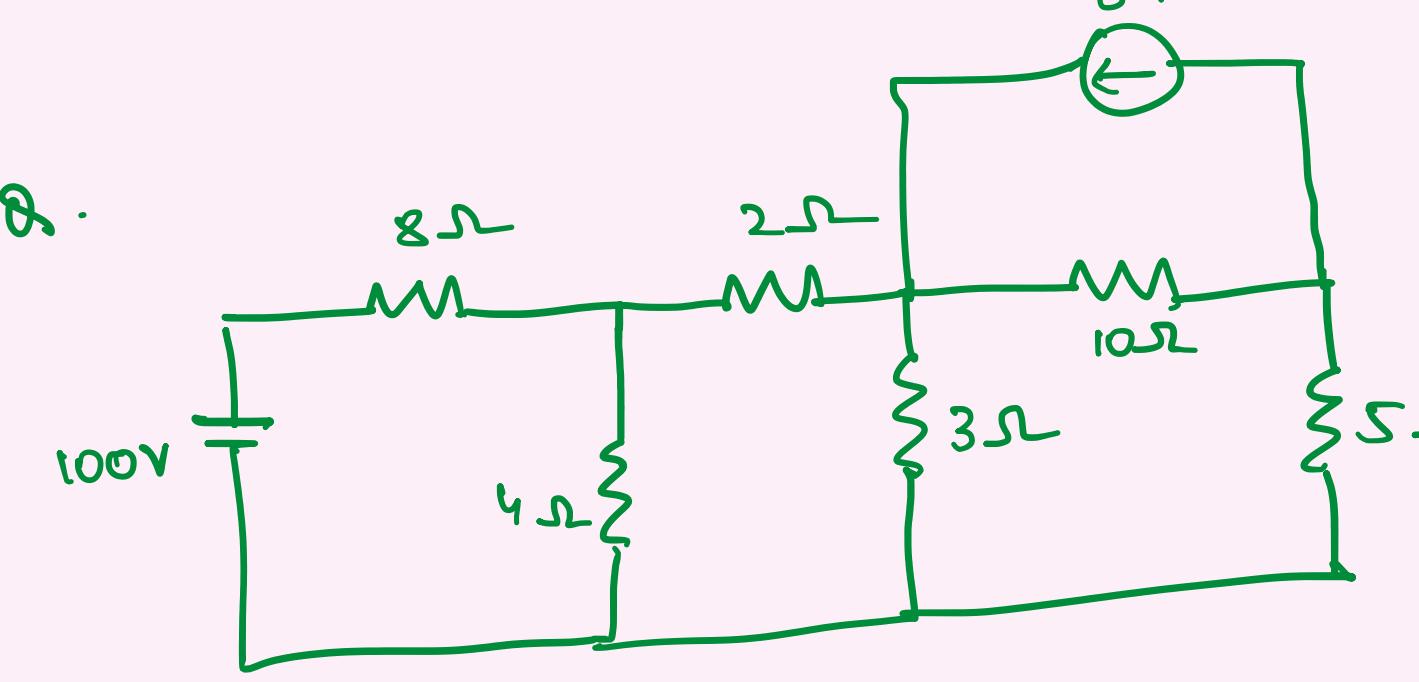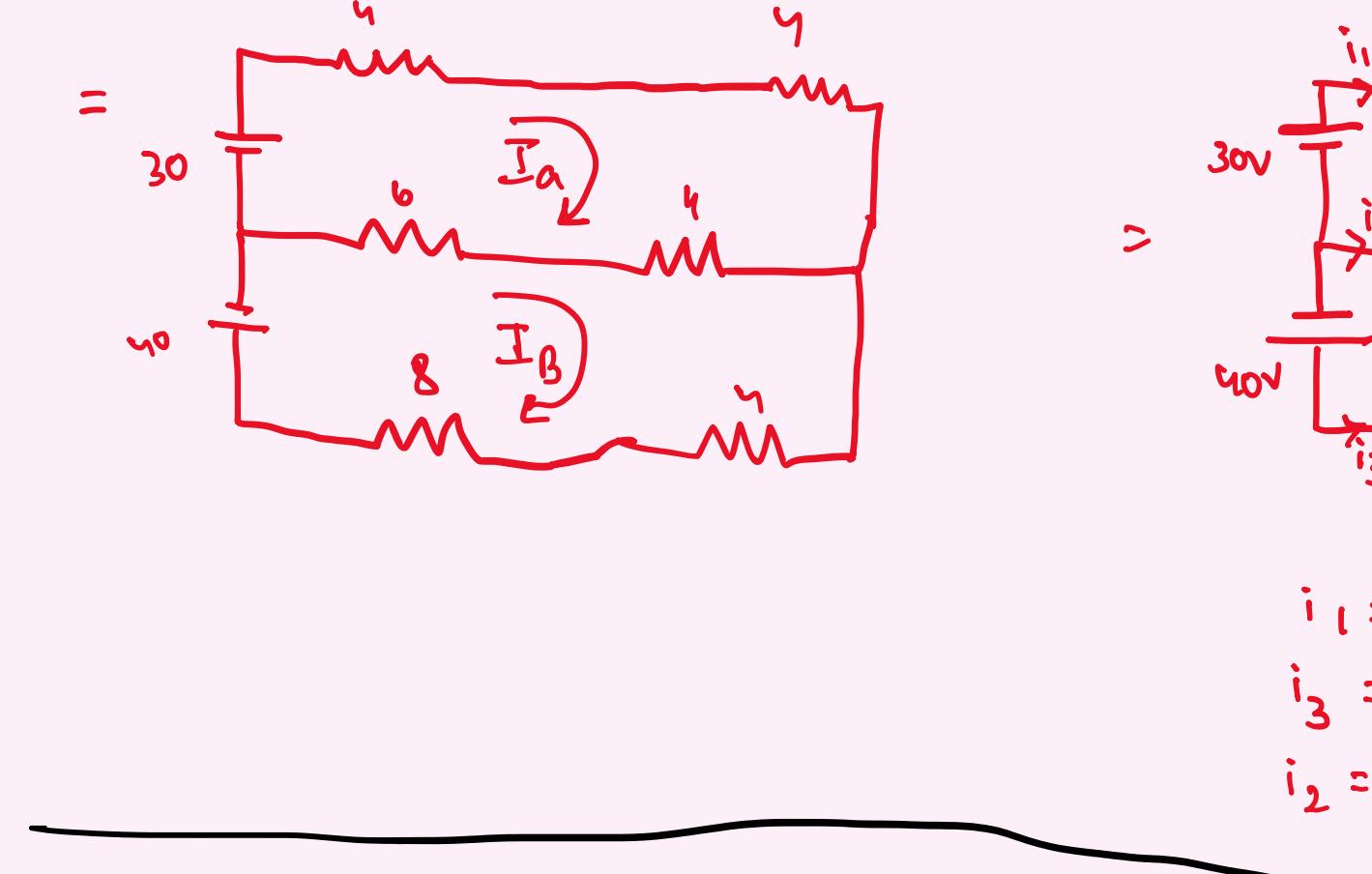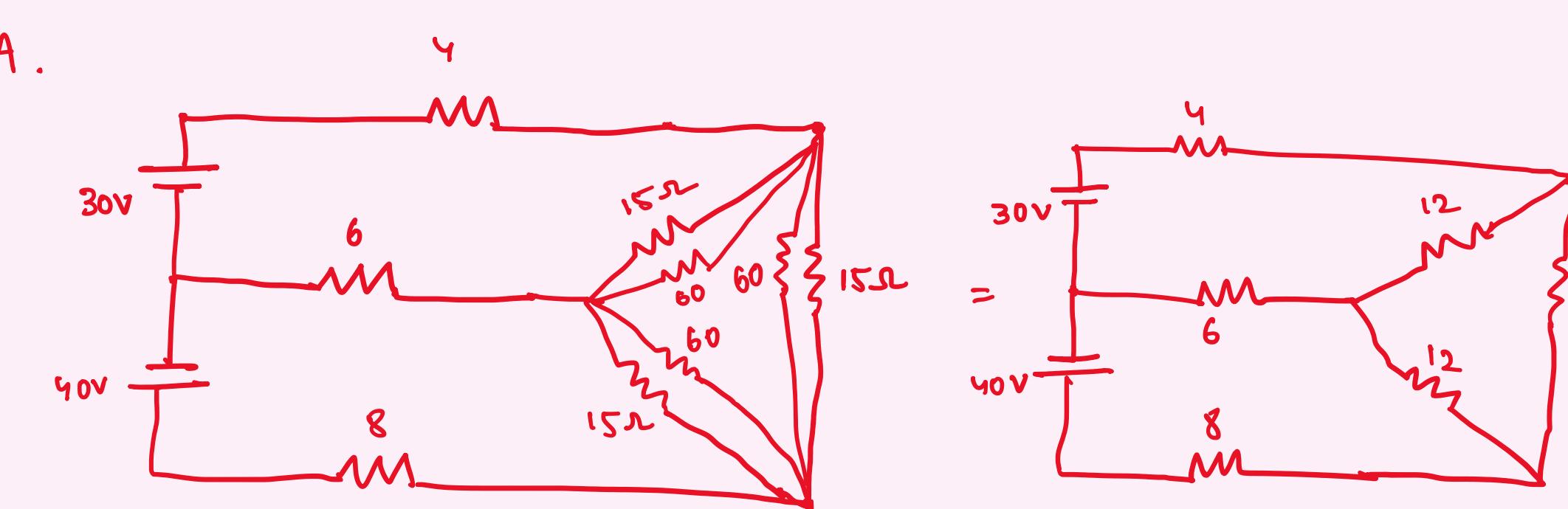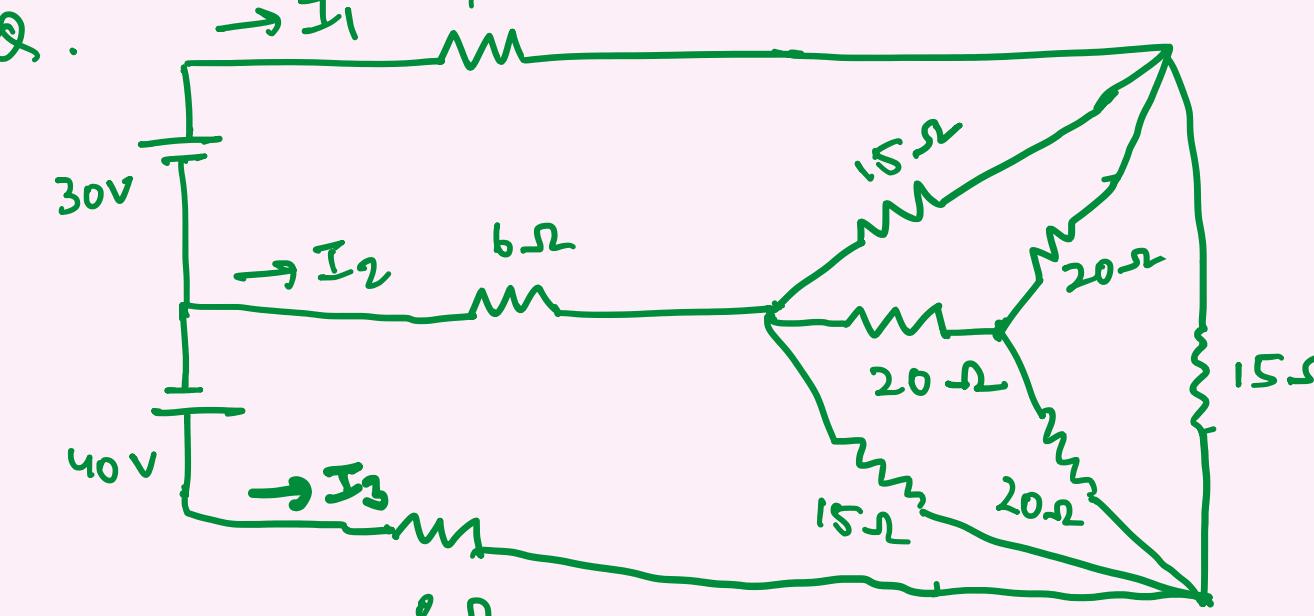
$$I_{(5\Omega)} = I_1 - I_3 = 2 \text{ A}$$




Find $I_{(4\Omega)}$

$$\begin{aligned} 12I_1 - 4I_2 + 0I_3 + 0I_4 &= 100 \\ -4I_1 + 9I_2 - 3I_3 + 0I_4 &= 0 \\ 0I_1 - 3I_2 + 18I_3 - 10I_4 &= 0 \\ I_4 &= -8 \text{ A} \end{aligned}$$

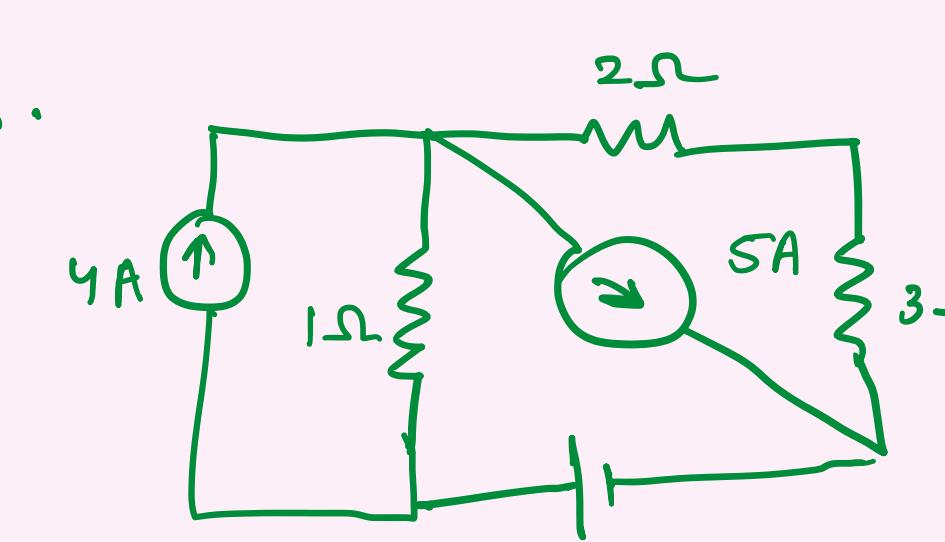
$$\begin{aligned} I_1 &= 9.26 \\ I_2 &= 2.79 \\ I_3 &= -3.98 \\ I_4 &= -8 \\ I_{(4\Omega)} &= 6.47 \end{aligned}$$



A.

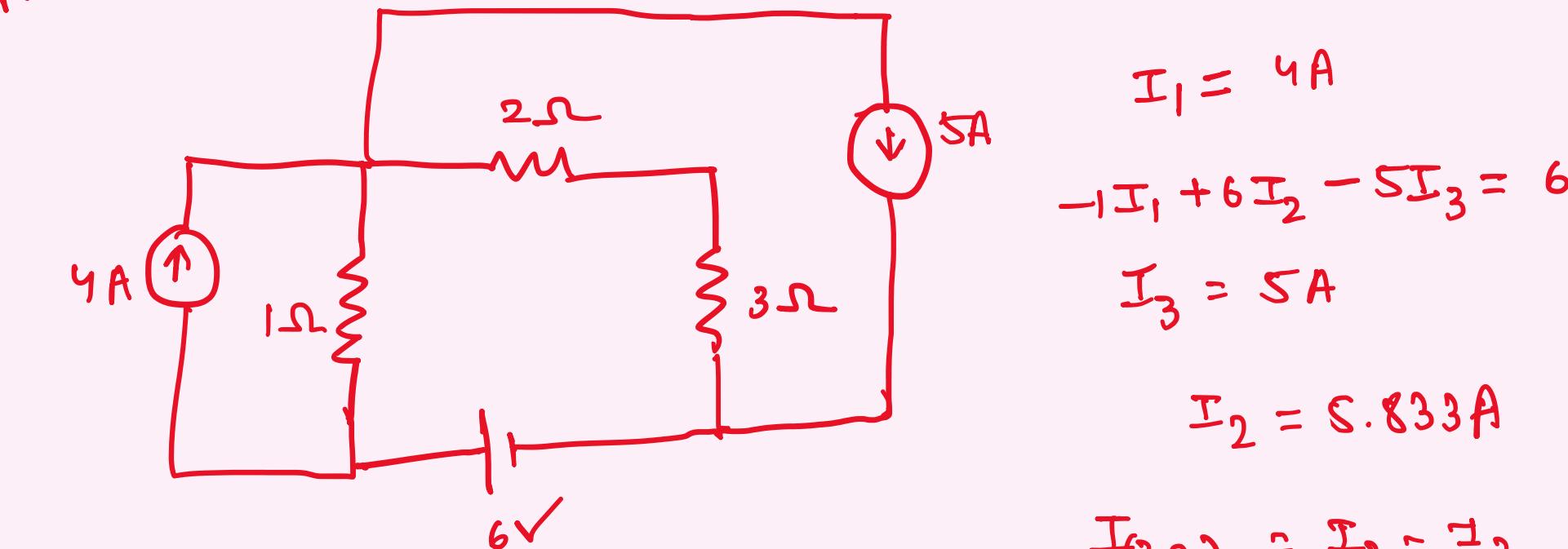
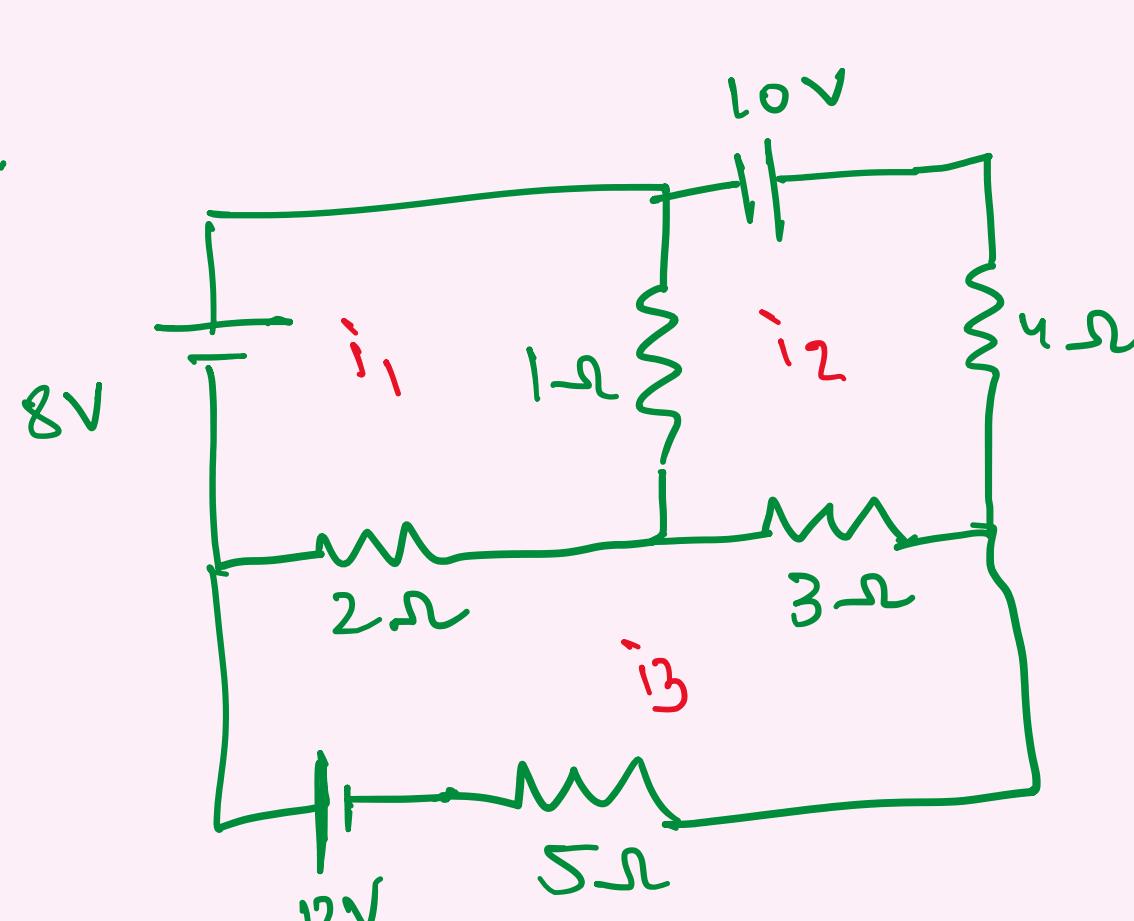
$$\begin{aligned} I_1 &= 4 \text{ A} \\ -I_1 + 6I_2 - 5I_3 &= 6 \\ I_3 &= 5 \text{ A} \\ I_2 &= 5.833 \text{ A} \\ I_{(3\Omega)} &= I_2 - I_3 \\ &= 0.833 \text{ A} \\ V_{(3\Omega)} &= 0.833 \times 3 \\ &= 2.5 \text{ V} \end{aligned}$$




$$\begin{aligned} 3i_1 - i_2 - 2i_3 &= 8 \\ -1i_1 + 8i_2 - 3i_3 &= 10 \\ -2i_1 - 3i_2 + 10i_3 &= 12 \end{aligned}$$


$$i_1 = 6.01$$

$$i_2 = 3.27$$

$$i_3 = 3.38$$

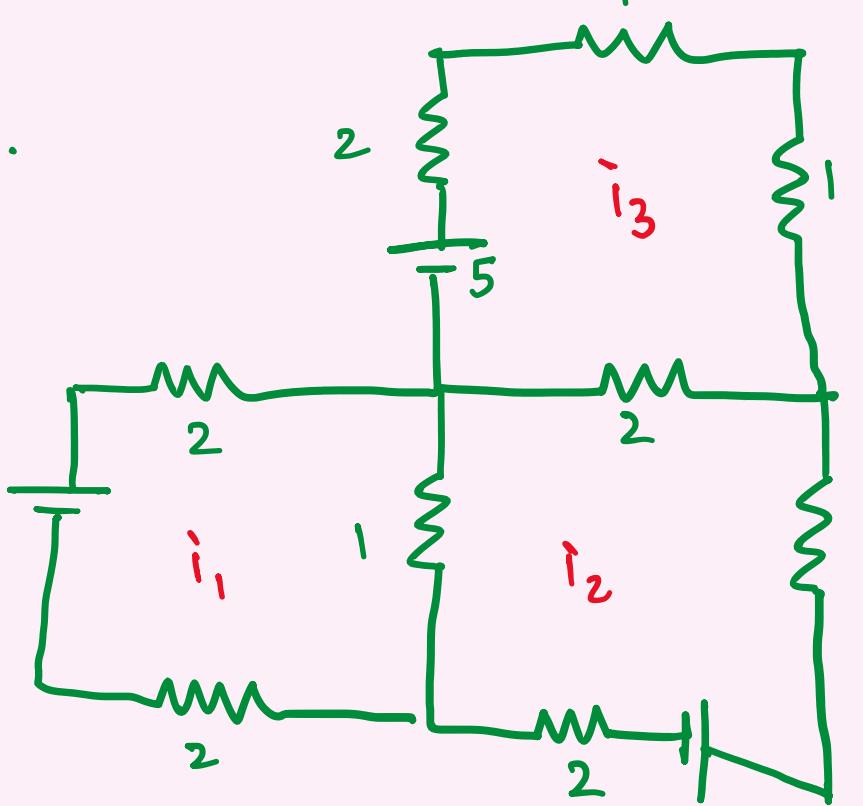
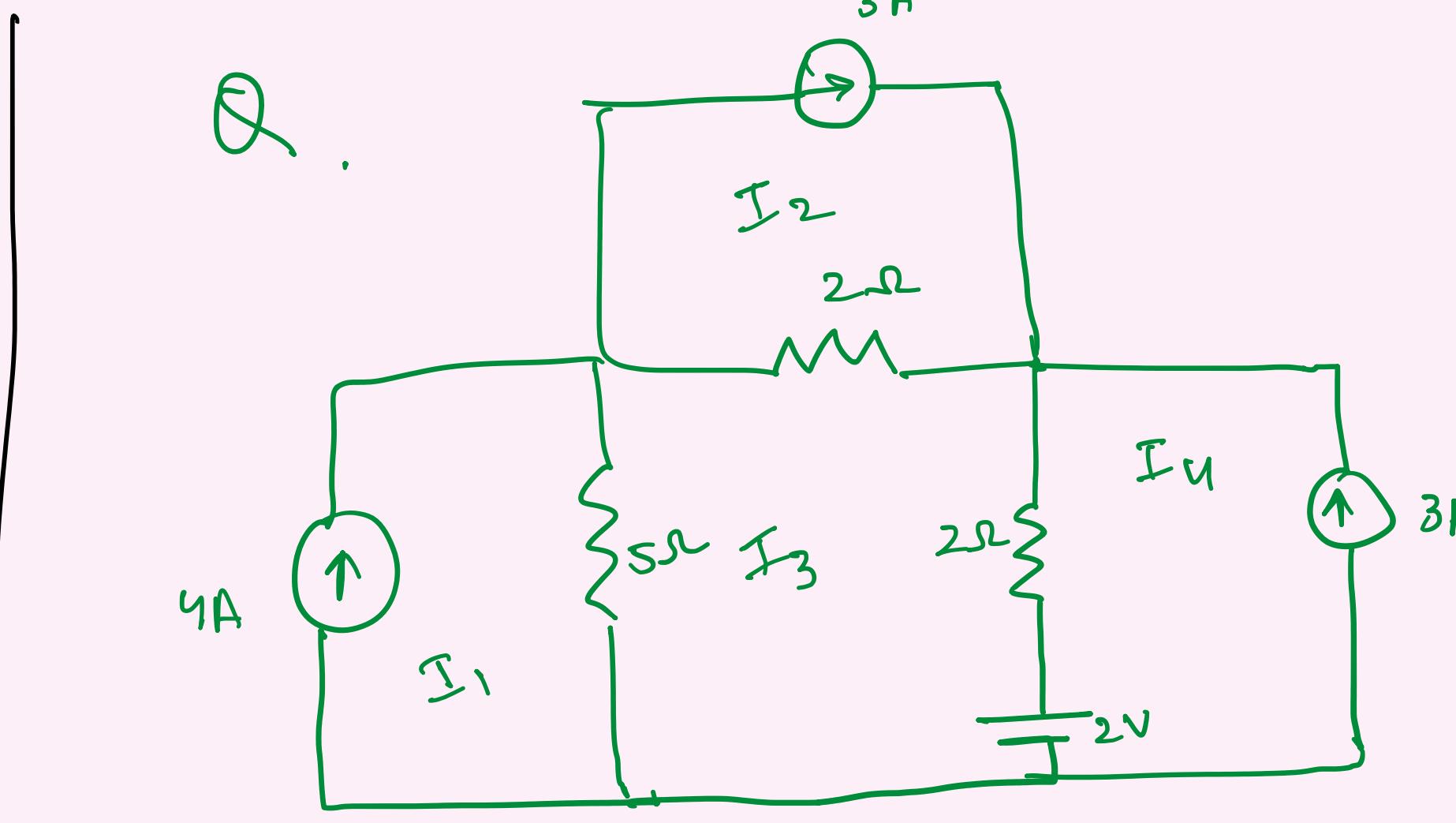
$$\begin{aligned} 5i_1 - 1i_2 - 0i_3 &= 5 \\ -1i_1 + 7i_2 - 2i_3 &= -5 \\ 0i_1 - 2i_2 + 6i_3 &= +5 \\ i_1 &= 0.92 \\ i_2 &= -0.38 \\ i_3 &= 0.706 \end{aligned}$$



7. Superposition Theorem

→ In a linear network with 1 or more than 1 independent source, the total response in any element is the algebraic sum of individual responses caused by each independent source acting alone, while all other independent sources are replaced by their internal resistances i.e., all other ideal voltage sources with short circuit & all other ideal current sources with open circuit.

Q.

A.

$$10I_1 - 6I_2 = 6V$$

$$-6I_1 + 9I_2 = 0$$

$$I_1 = 1A \quad I_2 = 0.67$$

$$10I_1 - 6I_3 = 0$$

$$-6I_1 + 9I_3 = -22$$

$$I_1 = -2.44$$

$$I_2 = -4.074$$

$$I_3 = 0.56$$

Q.

A.

$$I_{10} = \frac{4 \times 3}{3 + (1+2)} = 2A$$

$$I'_{10} = -1 \times \frac{2}{12+2} = -\frac{1}{7} A = -0.142A$$

$$I'' = 0.428A$$

$$I''' = 0.142A$$

Q.

A.

$$I'_{50} = \frac{1 \times 200}{250} = -\frac{4}{5} A$$

$$I''_{50} = \frac{100}{250} = \frac{2}{5} A$$

$$I'''_{50} = +\frac{0.5 \times 200}{250} = \frac{2}{5}$$

$$I_{50} = I' + I'' + I''' = -\frac{4}{5} A = -800mA$$

Q.

A.

$$8I_1 - 6I_2 = 10$$

$$-6I_1 + 16I_2 = 0$$

$$I_1 = 1.739A$$

$$I_2 = 0.65A$$

$$I'_6 = I_1 - I_2 = 1.08A$$

$$I''_6 = 5 \times \frac{\left(\frac{1}{10} + \frac{1}{2}\right)^{-1}}{6 + \left(\frac{1}{10} + \frac{1}{2}\right)^{-1}} = 1.08A$$

$$I'''_6 = I_1 - I_2 = 1.08A$$

Now,

$$-I' + I'' - I''' = -0.26A$$

↓

0.26A Downward

Q.

A.

$$\frac{22}{200} = 0.16A$$

$$0.16 \times 40 = 6.4V$$

$$V = 4.8 \times 40 = 192V$$

$$\frac{192 \times 40}{200} = -4V$$

$$-192 - 4 + 6.4 = -189.6V$$

189.6V ACW

Q.

A.

$$I'_6 = \frac{100}{18} = 5.55$$

$$I''_6 = \frac{6 \times 12}{18} = 2$$

$$I = I' + I'' = 7.55$$

Q.

A.

$$I' = -\frac{12 \times 12}{6 + 12} = -8$$

$$I'' = \frac{30}{18} = -1.67A$$

$$I''' = \frac{6 \times 12}{18} = 4A$$

$$I = I' + I'' + I''' = -5.67$$

Q.

A.

$$I_{ab} = \frac{2}{3+2} = \frac{2}{5} A$$

$$I^I = \frac{3 \times 2}{5+2} = \frac{6}{7} A$$

$$I^{II} = 0$$

$$I^III = -\frac{1}{7} A$$


$$I^{IV} = \frac{3 \times 2}{5+2} = \frac{6}{7} A$$


$$I^{V} = -\frac{2}{7} A$$

$$I = I^I + I^{II} + I^{III} + I^{IV} + I^{V} = \frac{6+0-1+6-2}{7} = \frac{9}{7} = 1.285A$$

8. Thevenin's theorem

→ A linear network with a large number of independent and dependant sources and resistors b/w 2 terminals can be replaced with a simple 2 element series equivalent in which a voltage source called 'Thevenin's Equivalent Voltage' (V_{TH}) is in series with a resistance called 'Thevenin's Equivalent Resistance' (R_{TH}).

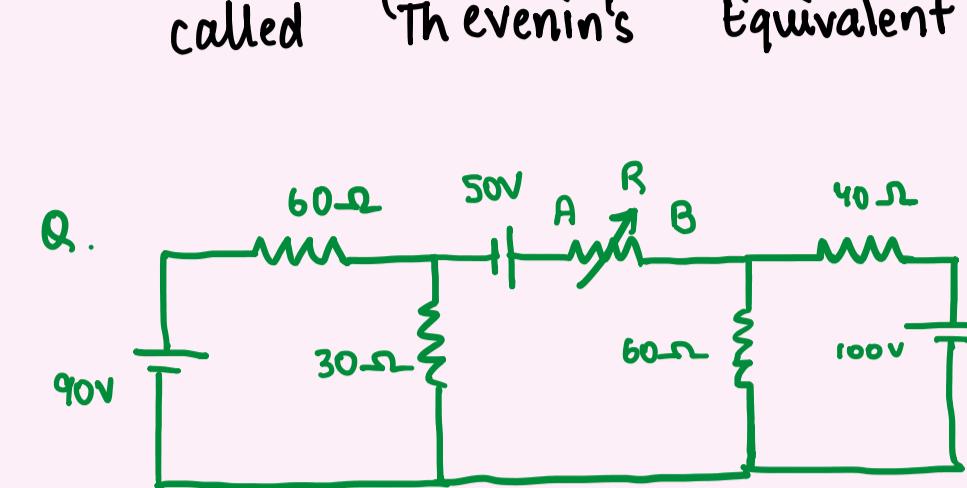
Q. 

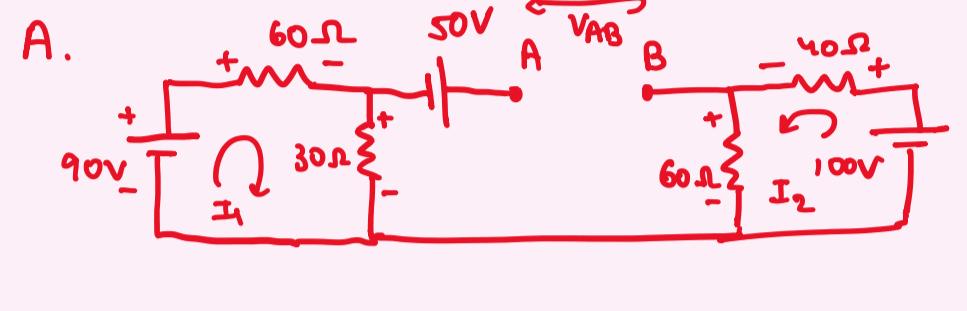A. 

$I_1 = \frac{90V}{90\Omega} = 1A$


$I_2 = \frac{100V}{100\Omega} = 1A$

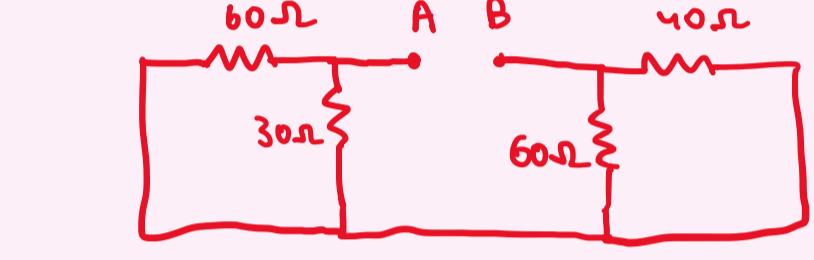$50 - V_{TH} - 60I_1 + 30I_2 = 0 \Rightarrow V_{TH} = 20V$




$R_{TH} = \left(\frac{1}{60} + \frac{1}{30} \right)^{-1} + \left(\frac{1}{60} + \frac{1}{40} \right)^{-1}$

$20 + 24 = 44\Omega$

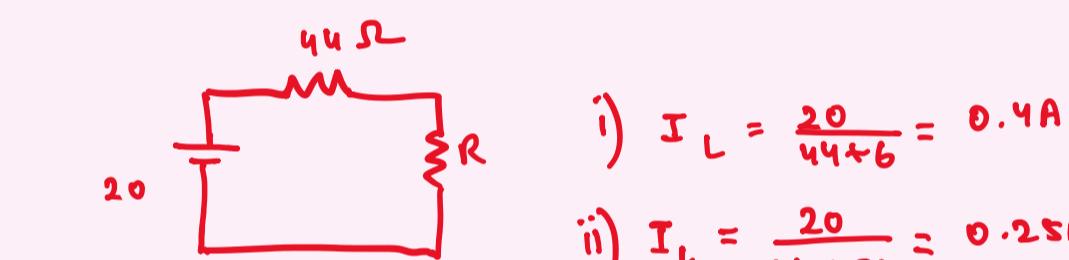

i) $I_L = \frac{20}{44+6} = 0.4A$
ii) $I_L = \frac{20}{44+36} = 0.25A$

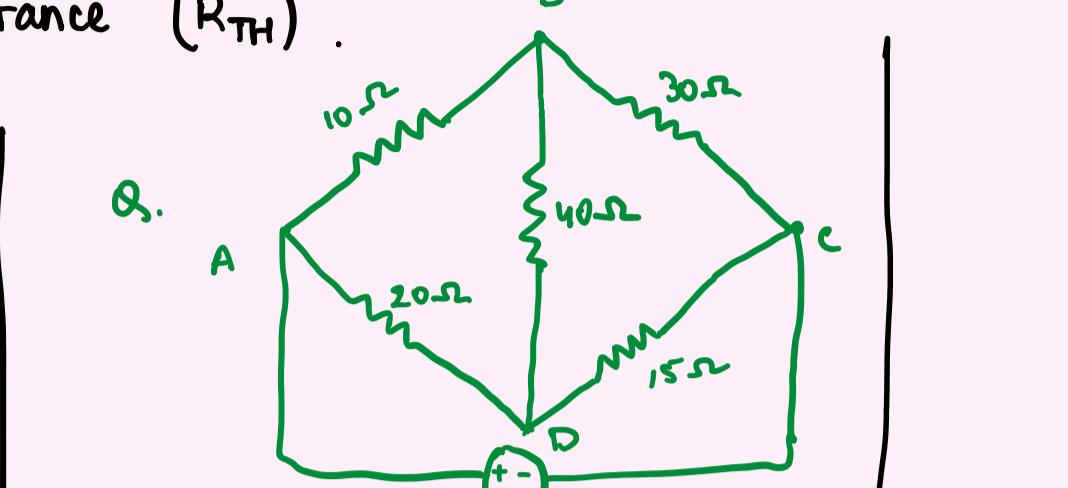
Q. 

A. 


$18I_1 - 12I_2 - 0I_3 = 60$
 $-12I_1 + 24I_2 - 8I_3 = 0$
 $0I_1 + 0I_2 + I_3 = 8$

$I_1 = 7.61A$ $I_2 = 6.5A$ $I_3 = 8A$


$V_{TH} = 8 \times (I_2 - I_3) = -12V$

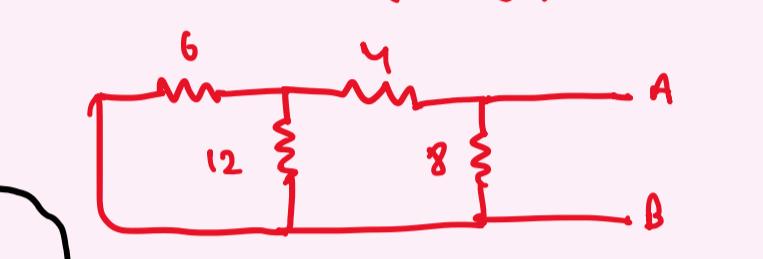

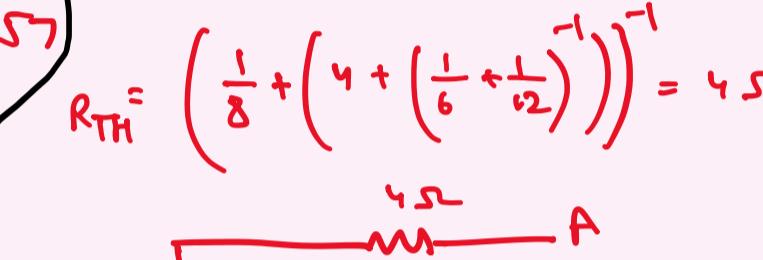$R_{TH} = \left(\frac{1}{8} + \left(4 + \left(\frac{1}{6} + \frac{1}{12} \right)^{-1} \right) \right)^{-1} = 4\Omega$



$I_1 = \frac{2 \times 35}{40+35} = 0.933A$
 $I_2 = \frac{2 \times 40}{75} = 1.067A$

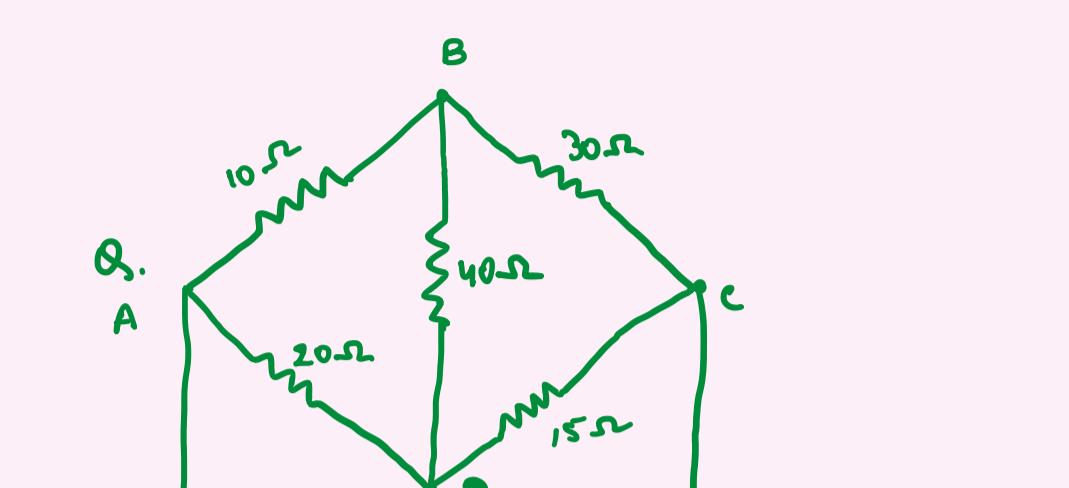
Q. 


A. 

$V_{TH} + 10I_1 - 20I_2 = 0 \Rightarrow V_{TH} = 12.01V$

$R_{TH} = \left(\frac{1}{30} + \frac{1}{45} \right)^{-1} = 18\Omega$


$I_L = \frac{12.01}{18+40} = 0.207A$

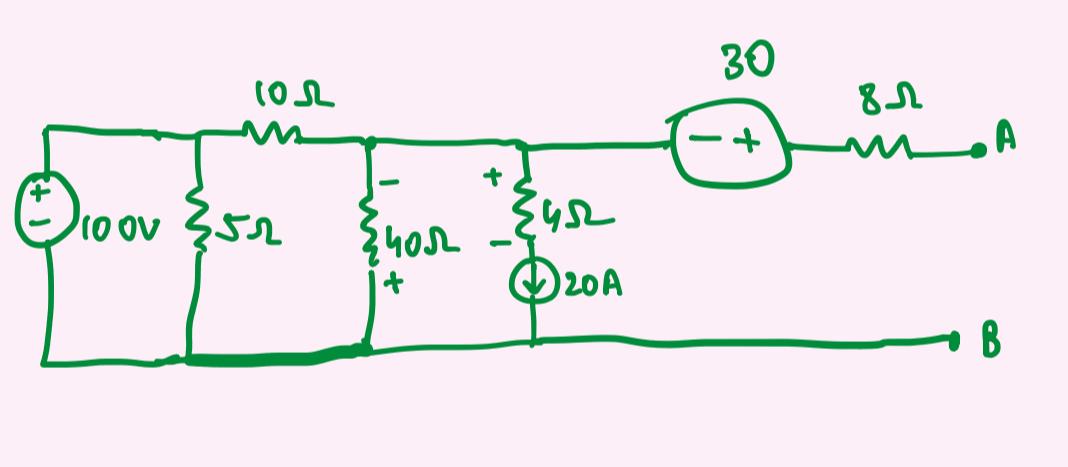Q. 

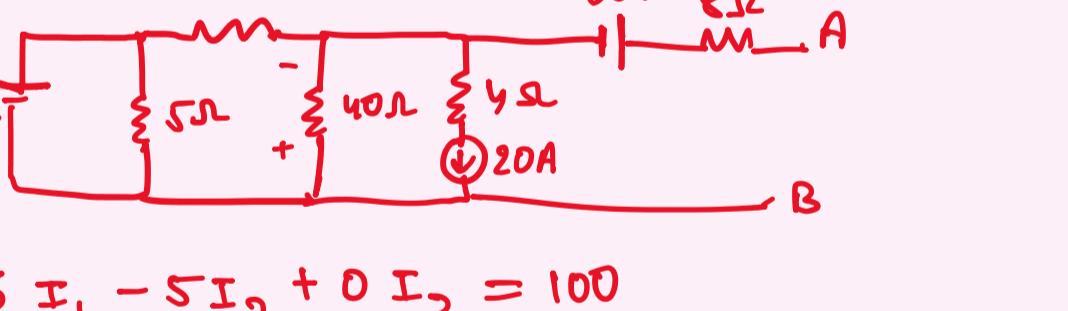
A. 

$5I_1 - 5I_2 + 0I_3 = 100$
 $-5I_1 + 55I_2 - 40I_3 = 0$
 $I_3 = 20$
 $I_1 = 38A$, $I_2 = 18A$, $I_3 = 20A$

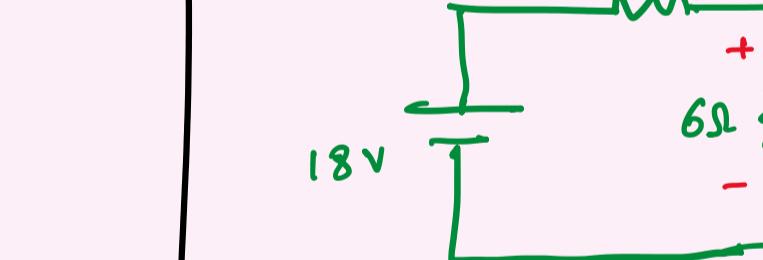
$V_{TH} - 8(0) - 30 + 40(I_3 - I_2) = 0$
 $V_{TH} = 30 - 80 = -50V$



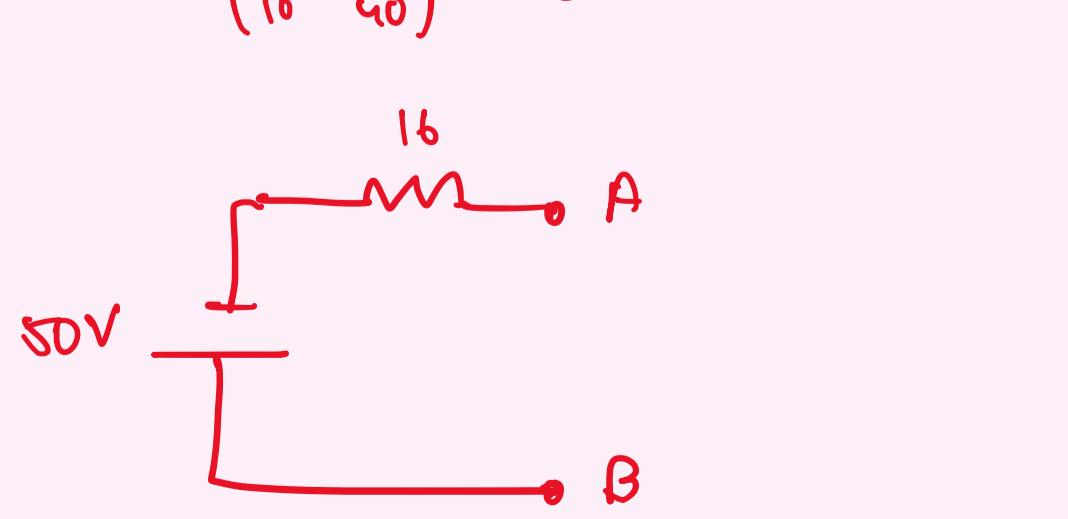$8 + \left(\frac{1}{10} + \frac{1}{40} \right)^{-1} = 16\Omega$



Q. 

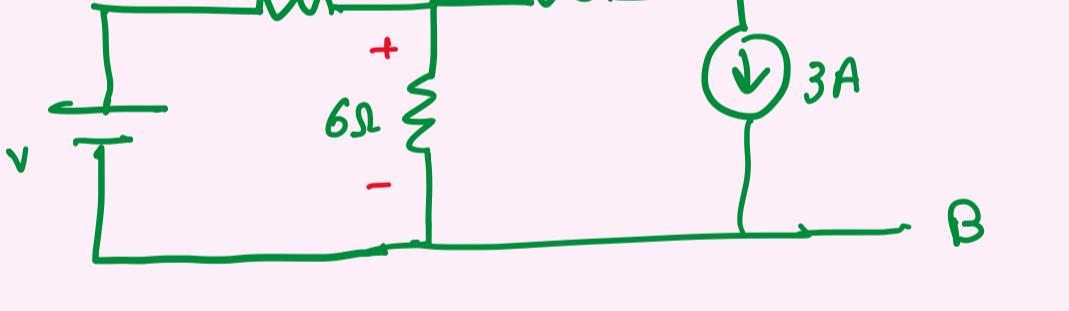
A. 


$9I_1 - 6I_2 = 18$
 $I_2 = 3A$
 $I_1 = 4A$

$V_{TH} + 9 - 6 = 0$
 $V_{TH} = -3V$



$3 + \left(\frac{1}{3} + \frac{1}{6} \right)^{-1} = 3 + 2 = 5\Omega$

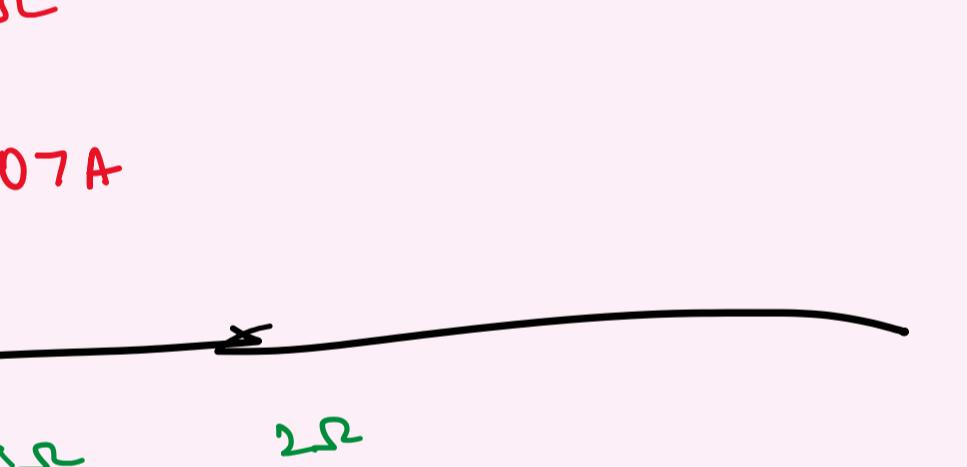Q. 

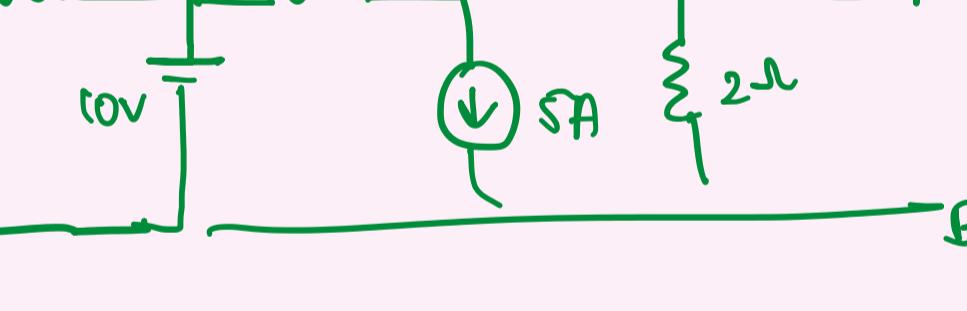A. 

$1I_1 - 0I_2 = -5$
 $0I_1 + 4I_2 = 20$
 $I_2 = 5$

$V_{AB} - 2(I_2) + 10 = 0$
 $V_{AB} = 0V$



$R_{TH} = 2 + 2 = 4\Omega$