

NAS UNIT - 1

→ Circuit

→ Interconnection of active & passive elements

→ Circuit Analysis

→ Process of finding voltages & currents across the circuit using linear algebra or Laplace Transform

→ Active elements :

Diodes, Transistors, Operational Amplifiers, Batteries, Thermal Generators, BJTs, MOSFETs, Voltage & Current regulators, Photodetectors, LEDs, LASERS, Piezoelectric Devices, Thermocouples

→ Passive elements :

Resistors, Inductors, Capacitors, Light Bulb, Heating elements


→ Reference Current Polarity

→ They are chosen for purpose of analysis

→ Polarity of passive elements is marked wrt assumed current direction but actual current may or may not be same as assumed current direction


→ Types of reference current directions

Current Type	Direction	Analysis
Mesh Current	Clockwise	Mesh Analysis
Branch Current	Leaving Node	Nodal Analysis

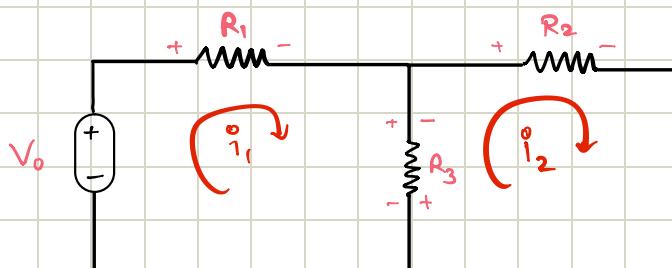

By mesh analysis,

$$V_0 - i_1 R_1 - (i_1 - i_2) R_3 = 0$$

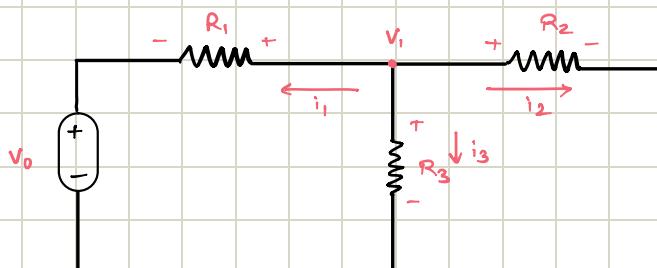

By nodal analysis

$$i_1 + i_2 + i_3 = 0$$

$$\left(\frac{V_1 - V_0}{R_1}\right) + \frac{V_1}{R_2} + \frac{V_1}{R_3} = 0$$

→ Independent Source

- They produce voltage / current at specified value
- Independent sources can be AC/DC

→ Voltage Sources


- Produces fixed voltage at terminals but current can vary with time
- Usually accompanied with series impedance

ex: DC Voltage Sources - Batteries, DC Generators, Power Suppliers


AC Voltage Sources - AC Generator

- Interest in current sources is due to semiconductor devices such as transistors
- Ideal Voltage sources have 0 internal impedance
- Ideal Current sources have 0 internal admittance
- DC Current / Voltage expressed in italics $E \frac{+}{-}$ $I \circlearrowleft$
- AC Current / Voltage expressed in bold $E \underline{\underline{+}}$ $I \underline{\underline{\circlearrowleft}}$

→ DC Source Conversion

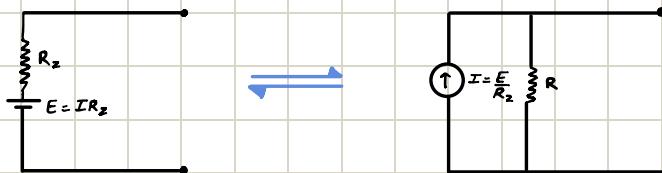


→ AC Source Conversion

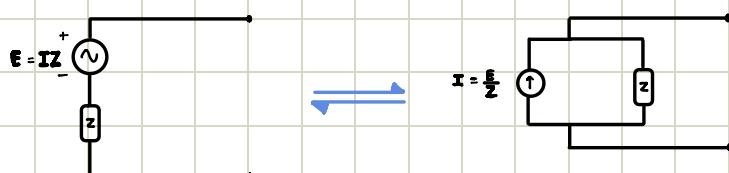


Note :




$$L_T = L_1 + L_2 + L_3$$

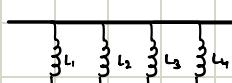

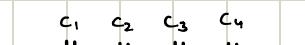
$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4}$$



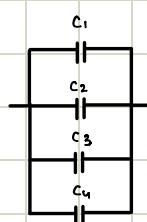
$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4}$$



$$C_T = C_1 + C_2 + C_3 + C_4$$

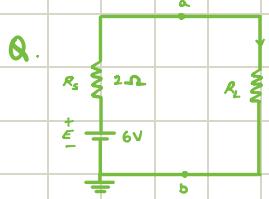

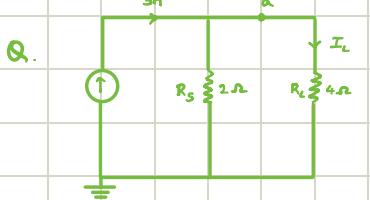
A. $I_L = \frac{E}{R_s + R_L} = \frac{6}{2+4} = 1A$




A. $I_L = \frac{R_s I}{R_s + R_L} = \frac{2 \times 3}{2+4} = 1A$



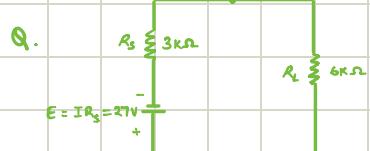
A. $I_L = \frac{R_s I}{R_s + R_L} = \frac{3000 \times 9 \times 10^{-3}}{3000 + 6000} = 3mA$



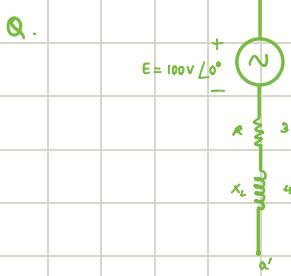
A. $I_L = \frac{E}{R_s + R_L} = \frac{27}{3000 + 6000} = 3mA$



Source Conversion


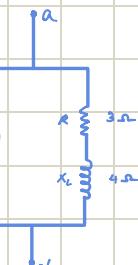


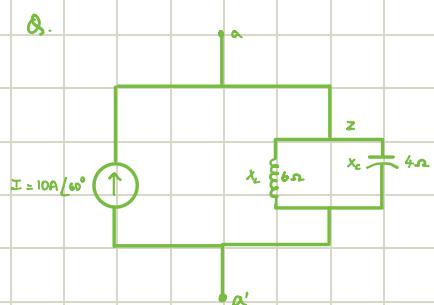$I = \frac{E}{Z} = \frac{100V\angle 0^\circ}{3+4j} = 20A\angle -53.13^\circ$



$$Z = \frac{Z_c Z_L}{Z_c + Z_L} = \frac{(X_c \angle -90^\circ)(X_L \angle 90^\circ)}{-jX_C + jX_L} = \frac{(4\angle -90^\circ)(6\angle 90^\circ)}{-4j + 6j} = \frac{24\angle 0^\circ}{2\angle 90^\circ} = 12\Omega \angle -90^\circ$$
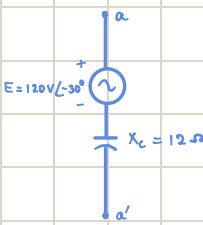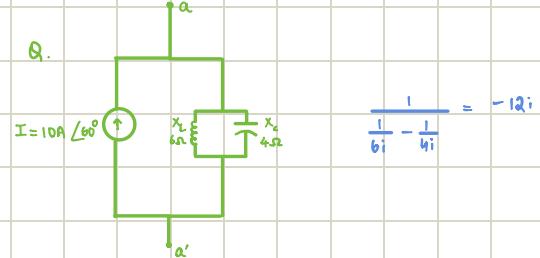
$$E = IZ = (10A\angle 60^\circ)(12\Omega \angle -90^\circ) = 120V\angle -30^\circ$$



→ Dependant Sources


- Magnitude of dependant source is controlled by current or voltage present elsewhere in the circuit
- Circuit symbol is given by diamond shape with sine for AC or w/o sine for DC



→ Dependant sources are classified as

Voltage Controlled
Voltage Source

VCVS

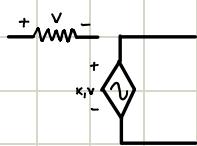


K_1 : Voltage gain

ex: Differential Amplifier

Current Controlled
Current Source

CCCS

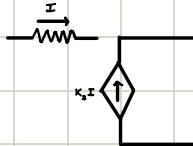


K_2 : Current gain

ex: Common Base Configuration

Voltage Controlled
Current Source

VCVS

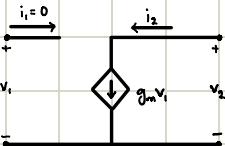


g_m : conductance

ex: MOSFET drain characteristics


Current Controlled
Voltage Source

CCVS

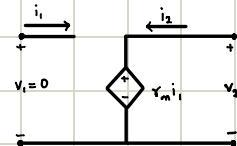


r_m : resistance

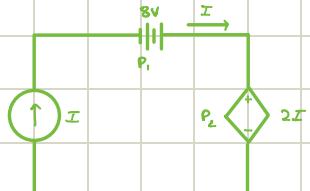Q. Calculate the powers P_1 and P_2 for given cases $I = 4A$ and $I = -3A$



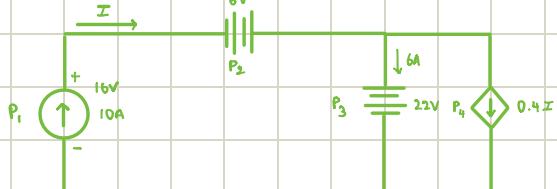A. i) $I = 4A$, $P_1 = -8 \times I = -32W$, $P_2 = 2I \times I = 32W$
ii) $I = -3A$, $P_1 = -8 \times I = 24W$, $P_2 = 2I \times I = 18W$


Q. Calculate the powers P_1 and P_2 , P_3 and P_4 given in the circuit



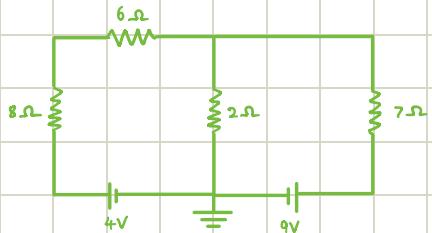
A. $P_1 = -16 \times 10 = -160W$
 $P_2 = -6 \times 10 = -60W$
 $P_3 = 22 \times 6 = 132W$
 $P_4 = 22 \times 0.4I = 88W$

→ Mesh Analysis : DC Circuits

Q. Write mesh equations and find current flowing in the 7Ω resistor



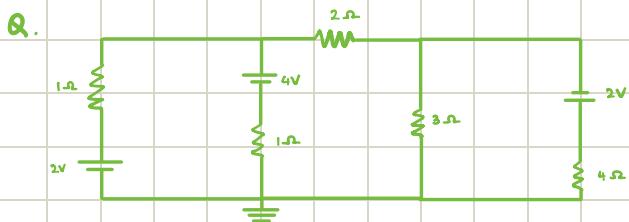
$$\begin{aligned} A. \quad & (8+6+2)i_1 - 2i_2 = 4 \\ & -2i_1 + (2+7)i_2 = -9 \end{aligned} \quad \left. \begin{array}{l} i_1 = 0.128A \\ i_2 = -0.971A = i_{7\Omega} \end{array} \right\}$$




$$\begin{aligned} A. \quad & (1+1)i_1 - (1)i_2 + 0i_3 = 2-4 \\ & -(1)i_1 + (1+2+3)i_2 - 3i_3 = 4 \\ & 0i_1 - 3i_2 + (3+4)i_3 = 2 \end{aligned} \quad \left. \begin{array}{l} i_1 = -0.542A \\ i_2 = 0.915A \\ i_3 = 0.678A \end{array} \right\}$$

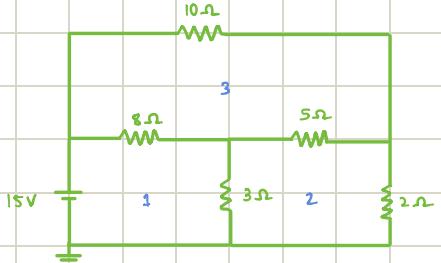Q. Determine the current through 10Ω resistor


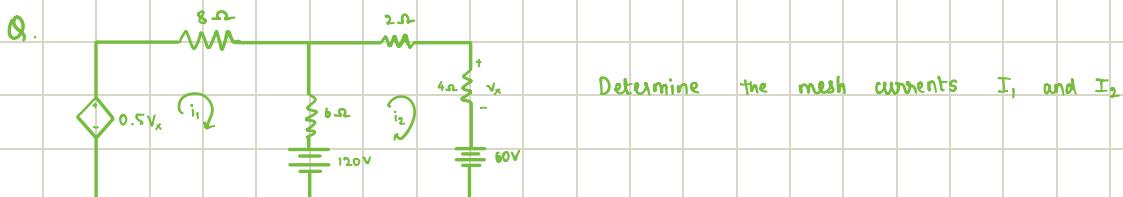
$$\begin{aligned} A. \quad & (8+3)i_1 - (3)i_2 - 8i_3 = 15 \\ & -3i_1 + 10i_2 - 5i_3 = 0 \\ & -8i_1 - 5i_2 + (8+5+10)i_3 = 0 \end{aligned} \quad \left. \begin{array}{l} i_1 = 2.632A \\ i_2 = 1.4A \\ i_3 = 1.22A = i_{10\Omega} \end{array} \right\}$$




$$\begin{aligned} A. \quad & 14i_1 - 6i_2 = -120 + 0.5V_x \Rightarrow 14i_1 - 8i_2 = -120 \\ & -6i_1 + 12i_2 = 120 - 60 \\ & \text{also, } V_x = 4i_2 \end{aligned} \quad \left. \begin{array}{l} i_1 = -8A \\ i_2 = 1A \end{array} \right\}$$

→ Supermesh Analysis


→ Steps :

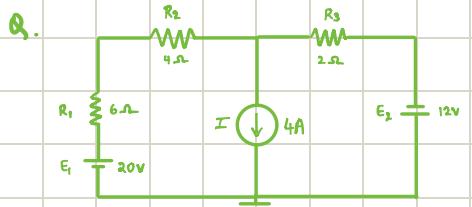- 1) Clockwise mesh currents are drawn as usual
- 2) Current source is removed from the circuit
- 3) This results in a supermesh
- 4) Write KVL for supermesh & represent the current source in terms of corresponding mesh currents



Determine the currents in the network using mesh analysis

A. Step 1:

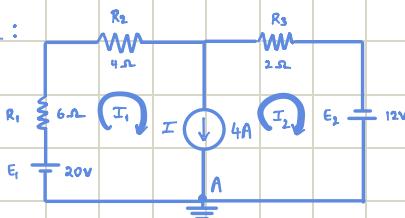


Step 2: KCL at A : $I + I_2 = I_1$

$$4 = I_1 - I_2$$

Step 3: $20 - 6I_1 - 4I_1 - 2I_2 + 12 = 0$

$$10I_1 + 2I_2 = 32$$

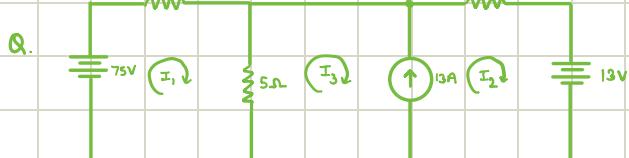
$$\Rightarrow I_1 = 3.33A, I_2 = -0.67A$$



Find the mesh currents in the circuit given.

A. Step 1: KCL at a : $13 + I_3 = I_2$


Step 2:

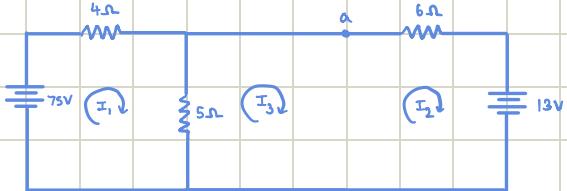

Step 3: $9I_1 - 5I_3 = 75$


$$-5I_1 + 6I_2 + 5I_3 = -13$$
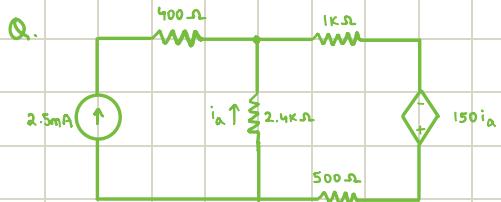
$$\Rightarrow I_1 = 5A, I_2 = 7A, I_3 = -6A$$




Find the current i_a in the circuit given below

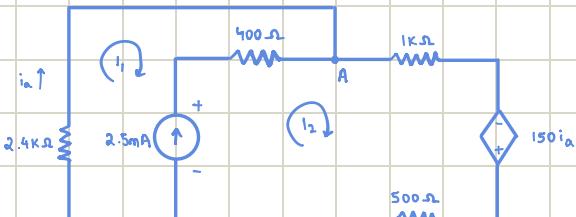A. Step 1: Find dependant source & represent in terms of mesh current



Step 2: KCL at A: $2.5\text{mA} + I_1 = I_2$

Step 3:


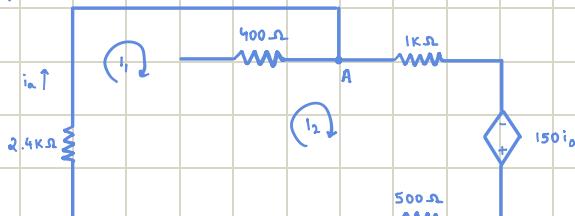


Step 4: $2.4k I_1 + (1k + 0.5k) I_2 = 150 i_a$

$$I_1 = i_a$$

$$\text{So, } 2.25k I_1 + 1.5k I_2 = 0$$

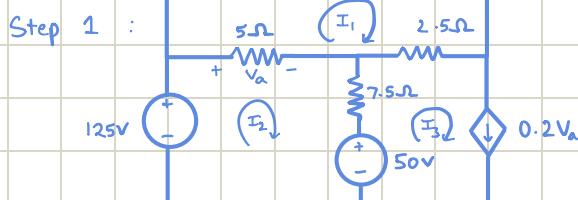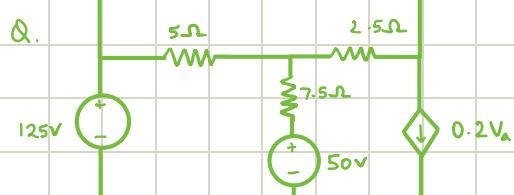
$$\Rightarrow I_1 = -1\text{mA} \quad I_2 = 1.5\text{mA}$$



Step 2: $V_a = 5(I_2 - I_1)$

Step 3: $I_3 = 0.2V_a = 0.2 \times 5(I_2 - I_1) \Rightarrow I_3 = I_2 - I_1$

Step 4:

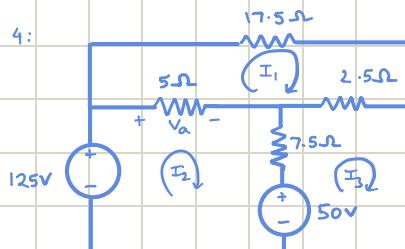

$$25 I_1 - 5 I_2 - 2.5 I_3 = 0$$


$$-5 I_1 + 12.5 I_2 - 7.5 I_3 = -50 + 125$$

↓

$$I_1 = 3.6A, I_2 = 13.2A, I_3 = 9.6A$$

→ Mesh Analysis : AC Circuits

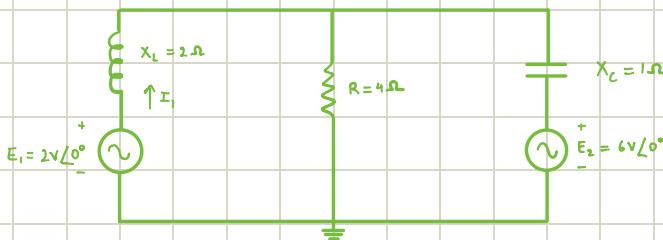
Q. Determine the mesh current I_1 in the circuit given below



$$A. \quad Z_1 = +jX_L = +j2 \Omega = 2 \angle 90^\circ$$

$$Z_2 = R = 4 \Omega$$

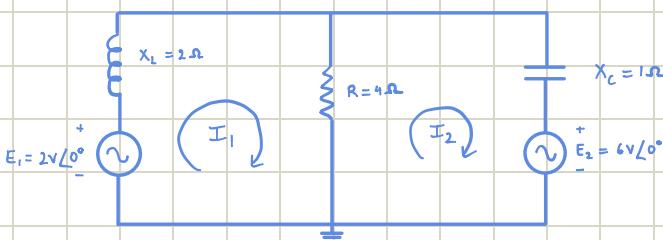
$$Z_3 = -jX_C = -j1 \Omega = 1 \angle -90^\circ$$



$$\text{Mesh 1: } (Z_1 + Z_2)I_1 + Z_2 I_2 = E_1$$

$$\text{Mesh 2: } -Z_2 I_1 + (Z_2 + Z_3)I_2 = -E_2$$
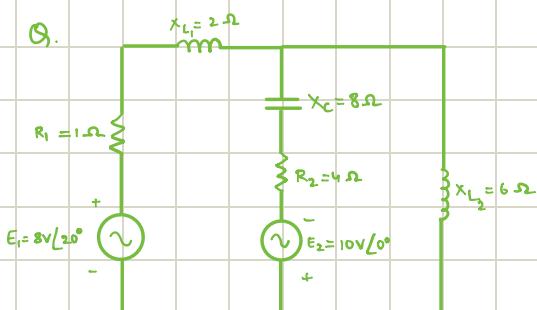
$$I_1 = \frac{\begin{vmatrix} E_1 & -Z_2 \\ -E_2 & Z_2 + Z_3 \\ \end{vmatrix}}{\begin{vmatrix} Z_1 + Z_2 & -Z_2 \\ Z_1 + Z_2 & -Z_2 \\ \end{vmatrix}} = \frac{E_1(Z_2 + Z_3) - E_2 Z_2}{Z_1 Z_2 + Z_1 Z_3 + Z_2^2 + Z_2 Z_3 - Z_2^2} = \frac{2(4 - i) - 6(i)}{8i + 2 - 4i} = \frac{-16 - 2i}{2 + 4i} = 3.605 \angle 123.69^\circ$$



Determine I_2


$$A. \quad Z_1 = R_1 + jX_{L1} = 1 + j2 \Omega ; \quad Z_2 = R_2 - jX_C = 4 - j8 \Omega ; \quad Z_3 = jX_{L2} = j6 \Omega$$

$$\text{Mesh 1: } (Z_1 + Z_2)I_1 - Z_2 I_2 = E_1 + E_2$$

$$\text{Mesh 2: } -Z_2 I_1 + (Z_2 + Z_3)I_2 = -E_2$$

$$I_2 = \frac{\begin{vmatrix} Z_1 + Z_2 & E_1 + E_2 \\ -Z_2 & -E_2 \\ \end{vmatrix}}{\begin{vmatrix} Z_1 + Z_2 & -Z_2 \\ Z_1 + Z_2 & -Z_2 \\ \end{vmatrix}} = \frac{-(Z_1 + Z_2)E_2 + Z_2(E_1 + E_2)}{(Z_1 + Z_2)(Z_2 + Z_3) - Z_2^2} = \frac{E_1 Z_2 - E_2 Z_1}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3} = 1.27 \angle -86.95^\circ$$

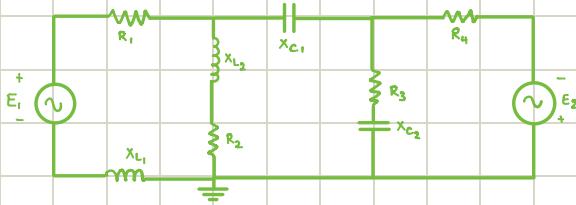Q. Write the KVL equations for the network given below



$$A. \quad z_1 = R_1 + jX_{L1}; \quad z_2 = R_2 + jX_{L2}; \quad z_3 = -jX_{C1}; \quad z_4 = R_3 - jX_{C2}; \quad z_5 = R_4$$


$$\text{Mesh 1: } (z_1 + z_2)I_1 - z_2 I_2 = E_1$$

$$\text{Mesh 2: } -z_2 I_1 + (z_2 + z_3 + z_4)I_2 - z_4 I_3 = 0$$

$$\text{Mesh 3: } -z_4 I_2 + (z_4 + z_5)I_3 = E_2$$

→ Mesh Analysis: Dependant Sources

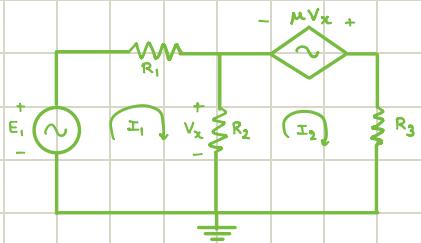Q. Write the mesh currents for the circuit below



A. 1) The dependant source expressed in terms of branch currents as

$$V_x = R_2(I_1 - I_2) \Rightarrow \mu V_x = \mu R_2(I_1 - I_2)$$

2) Write KVL for each mesh

$$\text{Mesh 1: } (R_1 + R_2)I_1 - R_2 I_2 = E_1$$

$$\text{Mesh 2: } -R_2 I_1 + (R_2 + R_3)I_2 = \mu V_x = \mu R_2(I_1 - I_2)$$


$$-R_2 I_1 + R_2 I_2 + R_3 I_2 = \mu R_2 I_1 - \mu R_2 I_2$$

$$-(1 + \mu)R_2 I_1 + (1 + \mu)R_2 I_2 + R_3 I_2 = 0$$

$$\Rightarrow -(1 + \mu)R_2 I_1 + ((1 + \mu)R_2 + R_3)I_2 = 0$$


→ Mesh Analysis: AC Circuits

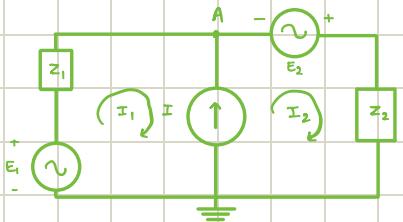Q. Write the mesh currents for the circuit given below




A. 1) KCL at A: $I_1 + I = I_2$

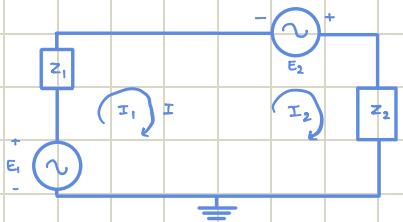2) Remove current source & write KVL for supermesh



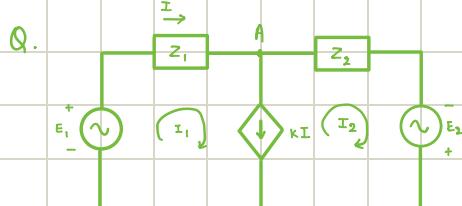
$$E_1 - I_1 Z_1 + E_2 - I_2 Z_2 = 0 \Rightarrow E_1 + E_2 = I_1 Z_1 + I_2 Z_2$$



Write the mesh currents for the circuit given

A. 1) KCL at A: $I_1 = I_2 + kI$
also $I = I_1$,
 $\text{So, } (k-1) I_1 + I_2 = 0$

2)

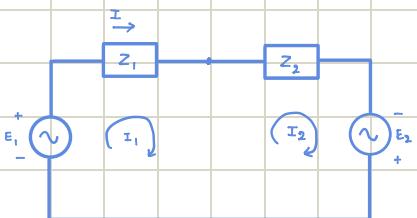


$$E_1 - I_1 Z_1 - I_2 Z_2 + E_2 = 0$$

$$Z_1 I_1 + Z_2 I_2 = E_1 + E_2$$

→ Nodal Analysis : DC Circuits

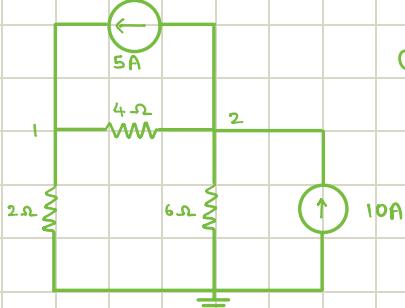Q. Calculate the node voltages for the circuit shown



A.

1) Introduce nodal voltages V_1 and V_2


2) KCL at 1: $\frac{V_1}{2} + \frac{V_1 - V_2}{4} = 5 \Rightarrow V_1 \left(\frac{1}{2} + \frac{1}{4} \right) + V_2 \left(-\frac{1}{4} \right) = 5$

KCL at 2: $\frac{V_2 - V_1}{4} + \frac{V_2}{6} = 10 - 5 \Rightarrow V_2 \left(\frac{1}{4} + \frac{1}{6} \right) + V_1 \left(-\frac{1}{4} \right) = 5$

$$V_1 = 13.33 \text{ V}$$

$$V_2 = 20 \text{ V}$$

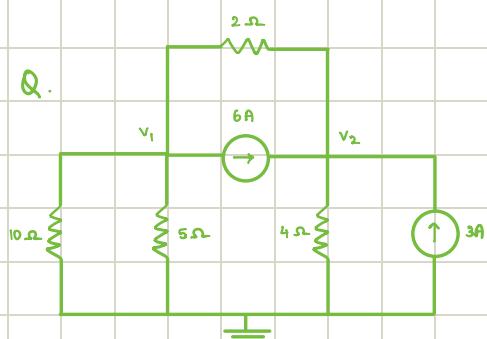Q. Find the nodal voltage equations for the circuit shown




A. Node 1: $\frac{V_1}{10} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = -6 \Rightarrow V_1 \left(\frac{1}{10} + \frac{1}{5} + \frac{1}{2} \right) + V_2 \left(-\frac{1}{2} \right) = -6$

Node 2: $\frac{V_2}{4} + \frac{V_2 - V_1}{2} = 6 + 3 \Rightarrow V_1 \left(-\frac{1}{2} \right) + V_2 \left(\frac{1}{2} + \frac{1}{4} \right) = 9$

$$V_1 = 0 \text{ V}, V_2 = 12 \text{ V}$$

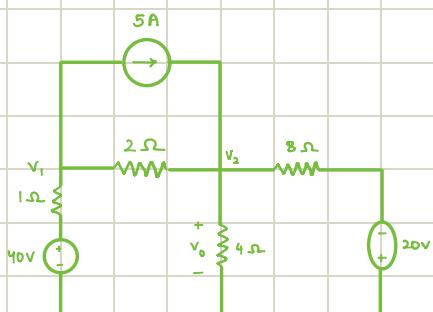Q. For the circuit shown, determine the node voltage V_0




A. Node 1, $\frac{V_1 - 40}{1} + \frac{V_1 - V_2}{2} = -5 \Rightarrow V_1 \left(1 + \frac{1}{2} \right) + V_2 \left(-\frac{1}{2} \right) = 35$

$$\left. \begin{aligned} V_1 &= 30 \text{ V} \\ V_2 &= 20 \text{ V} \end{aligned} \right\}$$


Node 2, $\frac{V_2 - V_1}{2} + \frac{V_2}{4} + \frac{V_2 + 20}{8} = 5 \Rightarrow V_1 \left(-\frac{1}{2} \right) + V_2 \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right) = 5 - \frac{20}{8}$

$$V_2 = 20 \text{ V} = V_0$$

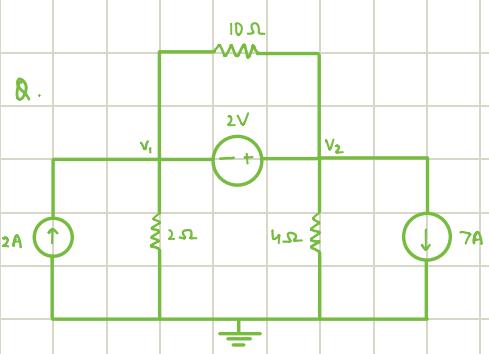

For the circuit shown find the node voltage

A. $V_2 - V_1 = 2V$

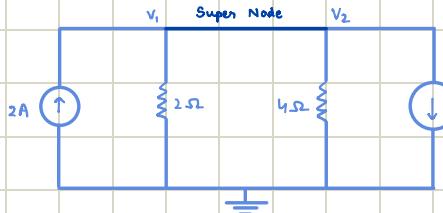


→ We eliminate floating voltage source from the circuit
→ Redraw circuit by replacing the floating voltage circuit with short circuit

KCL for super node: $\frac{V_1}{2} + \frac{V_2}{4} = 2 - 7$

$V_1 = -7.33V$

$V_2 = -5.33V$


Q.

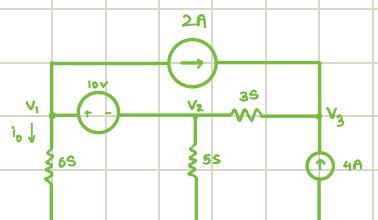

Apply nodal analysis to find the current i_0

A. $V_1 - V_2 = 10$

Now draw Super node

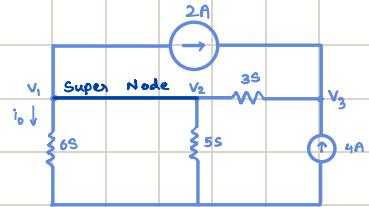


KCL for super node: $6V_1 + 5V_2 + 3(V_2 - V_3) = -2$

KCL at node 3: $3(V_3 - V_2) = 4 + 2$

$V_1 = 4.91V ; V_2 = -5.09V ; V_3 = -3.09V$

$i_0 = 6V_1 = 29.46A$

→ Nodal Analysis : AC Circuits

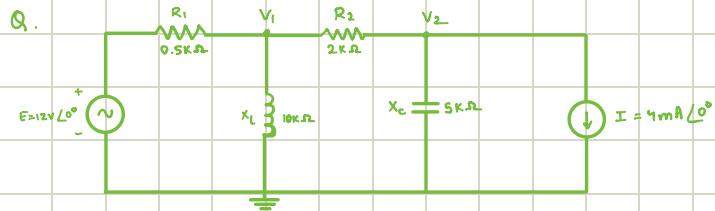

Determine Nodal Voltages

A. 1) $z_1 = R_1$; $z_2 = jX_L$; $z_3 = R_2$; $z_4 = -jX_C$

2) Node 1: $\frac{V_1 - E}{z_1} + \frac{V_1}{z_2} + \frac{V_1 - V_2}{z_3} = 0 \Rightarrow V_1 \left(\frac{1}{z_1} + \frac{1}{z_2} + \frac{1}{z_3} \right) + V_2 \left(\frac{-1}{z_3} \right) = \frac{E}{z_1}$

$$(2.5 \times 10^{-3} - 10^4 i) V_1 - 5 \times 10^{-4} V_2 = 0.024$$


$$2.502 \times 10^{-3} \angle -2.29 V_1 - 5 \times 10^{-4} V_2 = 0.024$$

Node 2: $\frac{V_2 - V_1}{z_3} + \frac{V_2}{z_4} = -I \Rightarrow V_1 \left(\frac{-1}{z_3} \right) + V_2 \left(\frac{1}{z_3} + \frac{1}{z_4} \right) = -I$

$$-5 \times 10^{-4} V_1 + (5 \times 10^{-4} + 2 \times 10^4 i) V_2 = -0.004$$


$$5 \times 10^{-4} V_1 - 5.39 \times 10^{-4} \angle 21.8 = 0.004$$
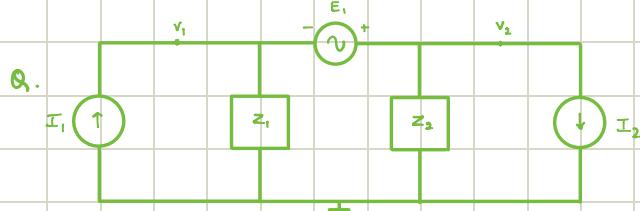
$$V_1 = \frac{E \quad B}{F \quad D} = \frac{ED - BF}{AD - BC} = 9.95 \angle 1.83^\circ$$




Find nodal voltages V_1 & V_2

A 1) $V_2 - V_1 = E_1$

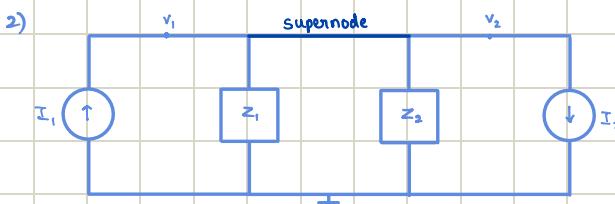

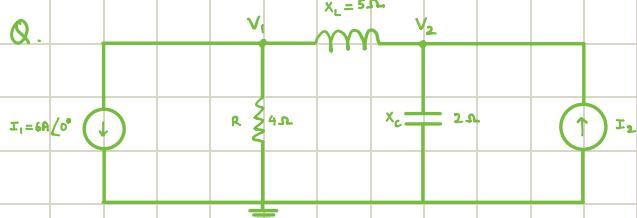KCL for supernode: $\frac{V_1}{z_1} + \frac{V_2}{z_2} = I_1 - I_2$



Determine the current through 4Ω resistor using nodal analysis

$$A. \quad z_1 = R = 4\Omega; \quad z_2 = jX_L = j5\Omega; \quad z_3 = -jX_C = -j2\Omega$$

$$\text{Node 1: } \frac{V_1}{z_1} + \frac{V_1 - V_2}{z_2} = -I_1 \Rightarrow V_1 \left(\frac{1}{z_1} + \frac{1}{z_2} \right) + V_2 \left(\frac{-1}{z_2} \right) = -I_1$$


$$0.32 \angle -38.66 V_1 + 0.2 \angle 90 V_2 = -6 \quad A \quad B \quad E$$

$$\text{Node 2: } \frac{(V_2 - V_1)}{z_2} + \frac{V_2}{z_3} = I_2 \Rightarrow V_1 \left(\frac{-1}{z_2} \right) + V_2 \left(\frac{1}{z_2} + \frac{1}{z_3} \right) = I_2$$

$$0.2 \angle 90 V_1 + 0.3 \angle 90 V_2 = 4 \quad C \quad D \quad F$$

$$V_1 = \frac{E \quad B}{F \quad D} = \frac{ED - BF}{AD - BC} = 20.8 \angle -126.87^\circ$$

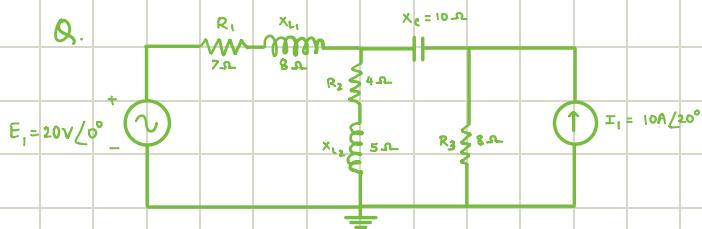
$$\begin{vmatrix} E & B \\ F & D \\ \hline A & B \\ C & D \end{vmatrix}$$



Find the nodal voltages

$$A. \quad 1) \quad z_1 = 7 + j8 \Omega; \quad z_2 = 4 + j5 \Omega; \quad z_3 = -j10 \Omega; \quad z_4 = 8 \Omega$$

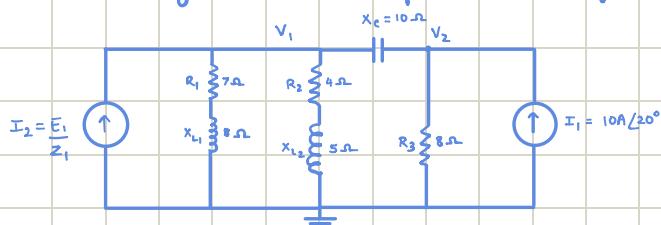2) Apply source transformation to get z_1 in parallel



$$I_2 = \frac{20}{7 + j8} = 1.88 \angle -48.81^\circ A$$

$$\text{node 1: } \frac{V_1}{z_1} + \frac{V_1}{z_2} + \frac{V_1 - V_2}{z_3} = I_2 \Rightarrow V_1 \left(\frac{1}{z_1} + \frac{1}{z_2} + \frac{1}{z_3} \right) + V_2 \left(\frac{-1}{z_3} \right) = I_2 \quad A \quad B \quad E$$

$$\text{node 2: } \frac{V_2 - V_1}{z_3} + \frac{V_2}{z_4} = I_1 \Rightarrow V_1 \left(\frac{-1}{z_3} \right) + V_2 \left(\frac{1}{z_3} + \frac{1}{z_4} \right) = I_1 \quad C \quad D \quad F$$



$$V_1 = \frac{E \quad B}{F \quad D} = 22.5 \angle 86.6^\circ$$

$$\begin{vmatrix} E & B \\ F & D \\ \hline A & B \\ C & D \end{vmatrix}$$

$$V_2 = \frac{A \quad E}{C \quad F} = 49.88 \angle -12.23^\circ$$

$$\begin{vmatrix} A & E \\ C & F \\ \hline A & B \\ C & D \end{vmatrix}$$

→ Nodal Analysis - Dependant Sources

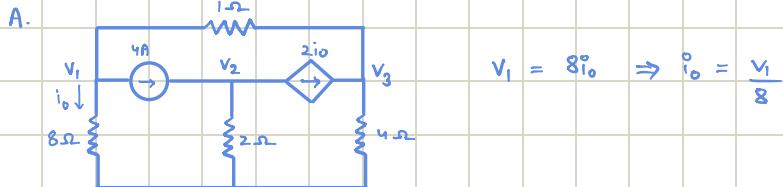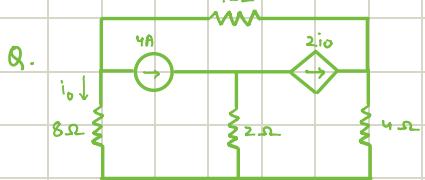

$$\text{Output of dependant current source } 2i_o = \frac{v_1}{4}$$

$$\text{node 1: } \frac{v_1}{8} + \frac{v_1 - v_3}{1} = -4 \text{ A} \Rightarrow v_1 \left(1 + \frac{1}{8}\right) + v_3 (-1) = -4$$


$$\text{node 2: } \frac{v_2}{2} = 4 - 2i_o \Rightarrow \frac{v_1}{4} + \frac{v_2}{2} = 4$$

$$\text{node 3: } \frac{v_3 - v_1}{1} - 2i_o + \frac{v_3}{4} = 0 \Rightarrow v_1 \left(-1 - \frac{1}{4}\right) + v_3 \left(1 + \frac{1}{4}\right) = 0$$

$$v_1 = -32 \text{ V}, \quad v_2 = 24 \text{ V}, \quad v_3 = -32 \text{ V}$$

$$i_o = \frac{v_1}{8} = -4 \text{ V}$$

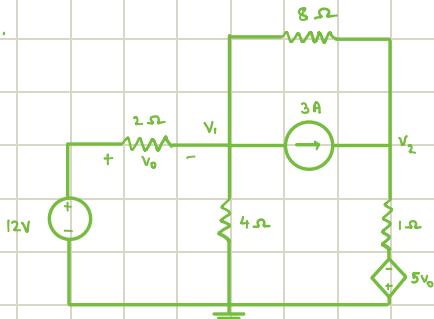Q. Determine the nodal voltages for the circuit shown



$$A \quad v_0 = 12 - v_1$$


$$\text{and } 5v_0 = 60 - 5v_1$$

$$\text{node 1: } \frac{v_1 - 12}{2} + \frac{v_1}{4} + \frac{v_1 - v_2}{8} = -3 \Rightarrow v_1 \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8}\right) + v_2 \left(-\frac{1}{8}\right) = 3$$

$$\text{node 2: } \frac{v_2 - v_1}{8} + \frac{v_2 + 60 - 5v_1}{1} = 3 \Rightarrow v_1 \left(-5 - \frac{1}{8}\right) + v_2 \left(\frac{1}{8} + 1\right) = -57$$

$$v_1 = -10.91 \text{ V}$$

$$v_2 = -100.36 \text{ V}$$

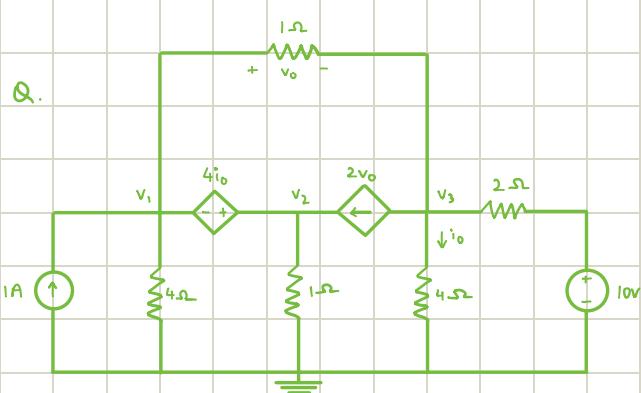


A. $i_0 = \frac{v_3}{4}$

$$v_0 = v_1 - v_3 \Rightarrow 2v_0 = 2(v_1 - v_3)$$

$$4i_0 = v_3$$
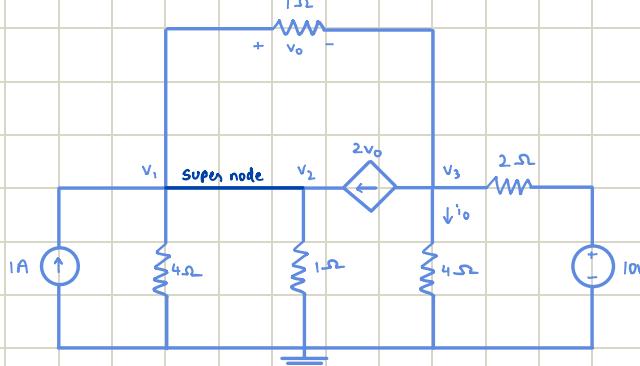
$$v_2 - v_1 = 4i_0 = v_3 \Rightarrow -v_1 + v_2 - v_3 = 0$$



KCL for supernode:


$$\frac{v_1}{4} + \frac{v_1 - v_3}{1} + \frac{v_2}{1} = 1 + 2v_0 \Rightarrow v_1 + v_1 - v_3 + v_2 - 2v_1 + 2v_3 = 1$$

$$-\frac{3}{4}v_1 + v_2 + v_3 = 1$$

KCL for node 3:

$$\frac{v_3}{4} + \frac{v_3 - 10}{2} + \frac{v_3 - v_1}{1} = -2v_0 \Rightarrow v_1 - \frac{v_3}{4} = 5$$
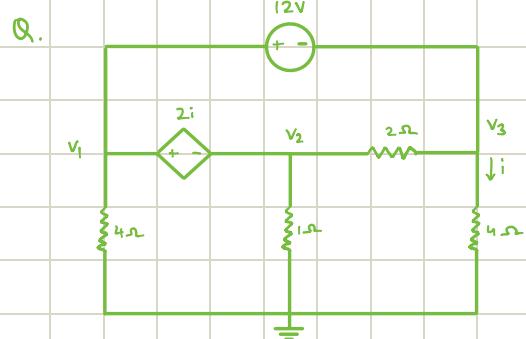
$$v_1 = 4.969V \quad v_2 = 4.848V \quad v_3 = -0.121V$$




A. $i = \frac{v_3}{4}$

$$2i = \frac{2v_3}{4} = \frac{v_3}{2}$$


$$v_1 - v_2 = 2i \Rightarrow v_1 - v_2 - \frac{v_3}{2} = 0$$

$$v_1 - v_3 = 12$$

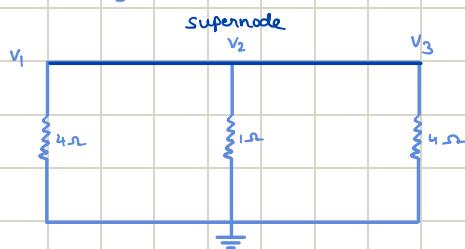

$$\frac{v_1}{4} + \frac{v_2}{1} + \frac{v_3}{4} = 0$$

$$v_1 = -3V, v_2 = 4.5V, v_3 = -15V$$

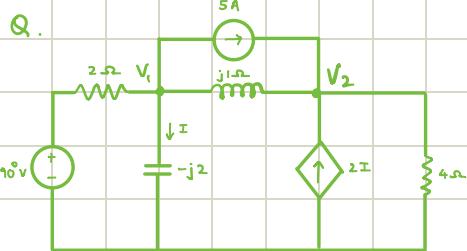

Solve for I

$$A. \quad z_1 = 2\Omega \quad z_2 = -j2\Omega \quad z_3 = j1\Omega \quad z_4 = 4\Omega$$

$$I = \frac{V_1}{z_2} \Rightarrow 2I = \frac{2V_1}{z_2}$$


$$\text{node 1: } \frac{(V_1 - E_1)}{z_1} + \frac{V_1}{z_2} + \frac{V_1 - V_2}{z_3} = -5 \Rightarrow V_1 \left(\frac{1}{z_1} + \frac{1}{z_2} + \frac{1}{z_3} \right) + V_2 \left(\frac{-1}{z_3} \right) = \frac{E_1}{z_1} - 5 \quad E$$

$$\text{node 2: } \frac{V_2 - V_1}{z_3} + \frac{V_2}{z_4} - 2I = 5 \Rightarrow V_1 \left(\frac{2}{z_2} - \frac{1}{z_3} \right) + V_2 \left(\frac{1}{z_3} + \frac{1}{z_4} \right) = 5 \quad F$$

$$V_1 = \begin{vmatrix} E & B \\ F & D \end{vmatrix} = \frac{ED - BF}{AD - BC} = 6.62 \angle -146.43$$

$$\begin{vmatrix} A & B \\ C & D \end{vmatrix}$$
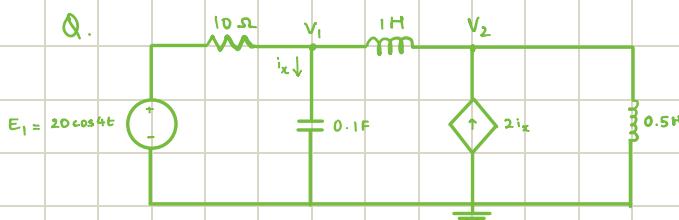
$$I = \frac{V_1}{z_2} = 3.31 \angle -56.43$$



$$A. \quad 20\cos 4t \Rightarrow \omega = 4 \text{ rad/s}$$

$$z_1 = 10\Omega \quad i_x = \frac{V_1}{z_2} \Rightarrow 2i_x = \frac{2V_1}{z_2}$$

$$z_2 = \frac{1}{j\omega C} = -j2.5\Omega$$

$$z_3 = j\omega L = j4$$

$$z_4 = j\omega L = j2$$


$$\text{node 1: } \frac{V_1 - E_1}{z_1} + \frac{V_1}{z_2} + \frac{V_1 - V_2}{z_3} = 0 \Rightarrow V_1 \left(\frac{1}{z_1} + \frac{1}{z_2} + \frac{1}{z_3} \right) + V_2 \left(\frac{-1}{z_3} \right) = \frac{E_1}{z_1} \quad E$$

$$\text{node 2: } \frac{V_2 - V_1}{z_3} + \frac{V_2}{z_4} = 2i_x \Rightarrow V_1 \left(\frac{-1}{z_3} - \frac{2}{z_2} \right) + V_2 \left(\frac{1}{z_3} + \frac{1}{z_4} \right) = 0 \quad F$$

$$V_1 = \begin{vmatrix} E & B \\ F & D \end{vmatrix} = \frac{ED - BF}{AD - BC} = 18.97 \angle 18.43$$


$$V_2 = \begin{vmatrix} A & E \\ C & F \end{vmatrix} = 13.91 \angle -161.56$$
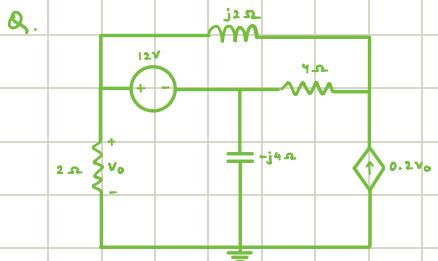
$$i_x = \frac{V_1}{z_1} = 1.89 \angle 18.43 \Rightarrow 1.89 \cos(4t + 18.43)$$



Use nodal analysis to find V_o

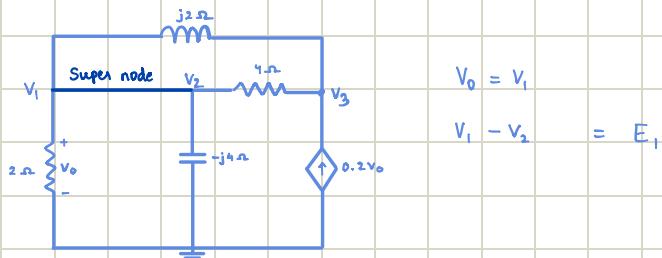A. $Z_1 = j2$ $Z_2 = 4\Omega$ $Z_3 = 2\Omega$ $Z_4 = -j4\Omega$ $E_1 = 12V$




KCL at supernode: $\frac{V_1 - V_3}{Z_1} + \frac{V_1}{Z_4} + \frac{V_2}{Z_3} + \frac{V_2 - V_3}{Z_2} = 0 \Rightarrow V_1 \left(\frac{1}{Z_1} + \frac{1}{Z_4} \right) + V_2 \left(\frac{1}{Z_3} + \frac{1}{Z_2} \right) + V_3 \left(-\frac{1}{Z_1} - \frac{1}{Z_2} \right) = 0$

Node 3: $\frac{V_3 - V_2}{Z_2} + \frac{V_3 - V_1}{Z_1} = 0.2V_o \Rightarrow V_1 \left(\frac{1}{Z_1} - 0.2 \right) + V_2 \left(-\frac{1}{Z_2} \right) + V_3 \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) = 0$


$$V_o = V_1 = \begin{vmatrix} 12 & -1 & 0 \\ 0 & B & C \\ 0 & E & F \end{vmatrix} = \frac{12(BF - CE)}{(BF - CE) + (AF - CD)} = 7.42 \angle 68.2^\circ$$
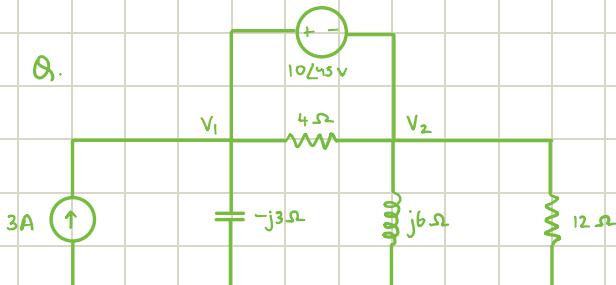
$$\begin{matrix} 1 & -1 & 0 \\ A & B & C \\ D & E & F \end{matrix}$$



A. $Z_1 = -j3\Omega$ $Z_2 = j6\Omega$ $Z_3 = 12\Omega$

$V_1 - V_2 = 10 \angle -45^\circ$

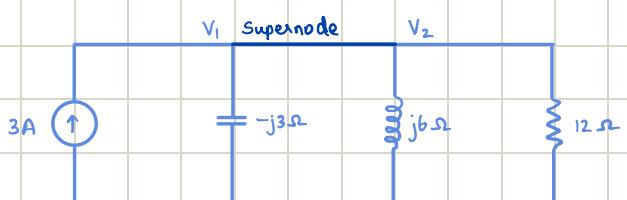

$$V_1 = \frac{10 \angle -45 - 1}{\begin{vmatrix} 1 & -1 \\ \frac{1}{Z_1} & \frac{1}{Z_2} + \frac{1}{Z_3} \end{vmatrix}} = 25.78 \angle -70.48^\circ \checkmark$$

Supernode: $\frac{V_1}{Z_1} + \frac{V_2}{Z_2} + \frac{V_2}{Z_3} = 3$

$$V_2 = \frac{1 \quad 10 \angle -45}{\begin{vmatrix} 1 & 3 \\ \frac{1}{Z_1} & 1 \end{vmatrix}} = 31.41 \angle -87.18^\circ \checkmark$$

Superposition Theorem

- The current through, or voltage across, an element in a linear bilateral network is equal to algebraic sum of the currents or voltages produced independantly by each independant source
- Applicable for bilateral linear AC networks as well

Advantages -

- Simplifies calculation
- Complex computation like calculation of determinants can be avoided


Disadvantages -

- Can't be applied to circuits with passive elements with non-linear IV characteristic
- Superposition of branch powers w different independant sources isn't allowed


→ Procedure

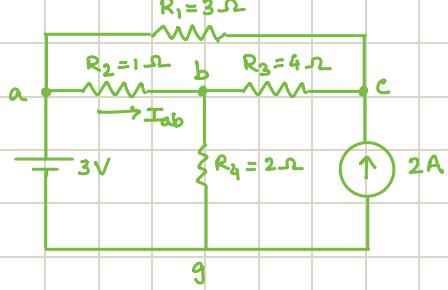- 1) Replace all but one of the sources by their internal resistances
- 2) Determine current/voltage of various branches using basic laws
- 3) Repeat it for all sources one by one
- 4) Add all the currents/voltages for each branch due to different independant sources resulting the actual current/voltage for that branch when all sources acting on the circuit simultaneously

Q. Calculate I_{ab} & V_{cg} using superposition theorem



A. 1)

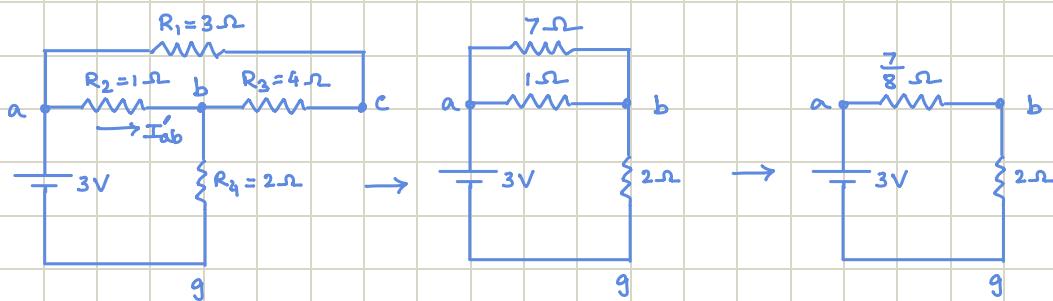

$$I = \frac{3}{2.875} = 1.043 \text{ A}$$


$$V'_{bg} = 2I = 2 \times 1.043 = 2.086 \text{ V}$$

$$I'_{ab} = \frac{3 - 2.086}{1} = 0.914 \text{ A}$$

$$I_{bc} = I'_{ab} - I = -0.129 \text{ A}$$

$$V'_{cg} = V'_{bg} + V'_{cb} = 2.086 - (4 \times -0.129) = 2.606 \text{ V}$$

2)

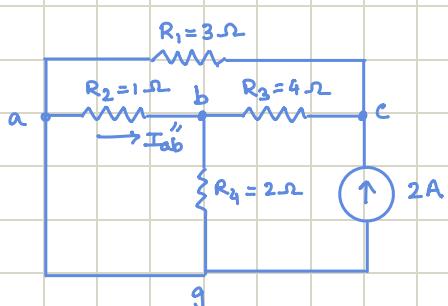


$$I = \frac{2 \times 3}{3 + (4 + (\frac{1}{1} + \frac{1}{2})^{-1}))} = 0.783 \text{ A}$$

$$I''_{ab} = -\frac{I \times 2}{1+2} = -0.522 \text{ A}$$


$$V''_{cg} = 3 \times (2 - I) = 3.652 \text{ V}$$

$$I_{ab} = I'_{ab} + I''_{ab} = 0.913 - 0.522 = 0.391 \text{ A}$$

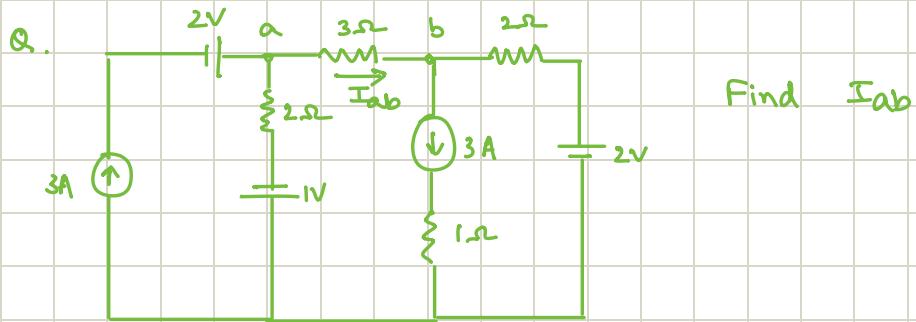
$$V_{cg} = V'_{cg} + V''_{cg} = 2.606 + 3.651 = 6.257 \text{ V}$$




Find I_{ab}

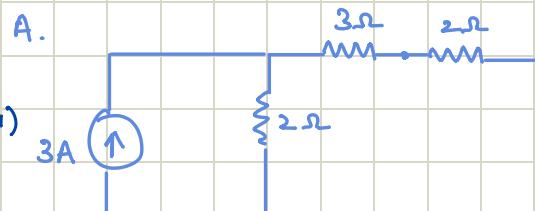
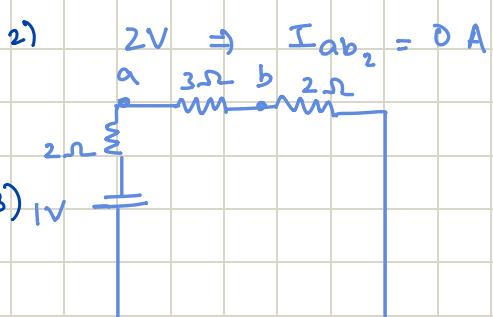
$$I_{ab_1} = \frac{3 \times 2}{7} = 0.857 \text{ A}$$


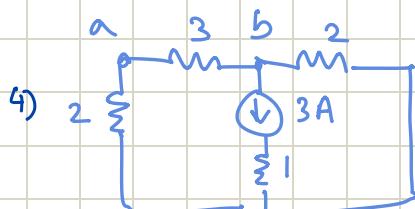
$$I_{ab_3} = -\frac{1}{7} = -0.142 \text{ A}$$





$$I_{ab_4} = \frac{3 \times 2}{5 + 2} = 0.857 \text{ A}$$




$$I_{ab_5} = -\frac{2}{7} = -0.285 \text{ A}$$
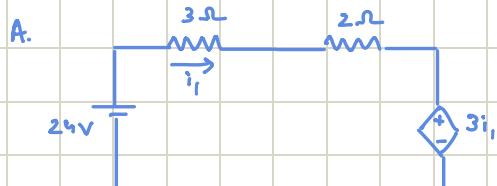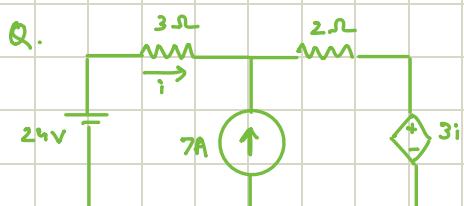
$$I_{ab} = I_{ab_1} + I_{ab_2} + I_{ab_3} + I_{ab_4} + I_{ab_5} = 1.285 \text{ A}$$



$$24 - 3i_1 - 2i_1 - 3i_1 = 0$$


$$i_1 = 3 \text{ A}$$

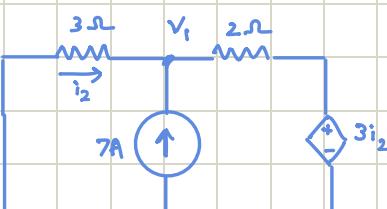


$$i_2 = -\frac{V_1}{3}$$

$$\frac{V_1}{3} + \frac{V_1 - 3(-\frac{V_1}{3})}{2} = 7 \Rightarrow V_1 = \frac{21}{4} \rightarrow i_2 = -\frac{7}{4} \text{ A}$$
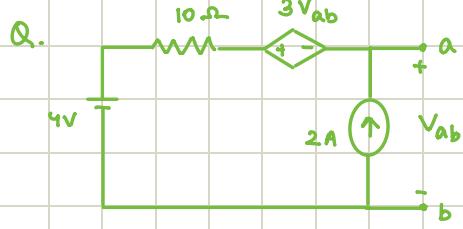
$$\text{Then, } i_1 + i_2 = 3 - \frac{7}{4} = \frac{5}{4} \text{ A}$$



Find V_{AB}

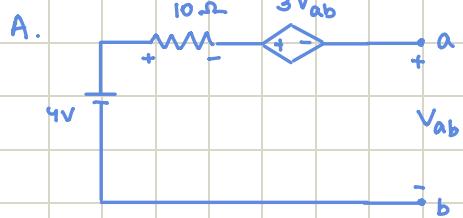

$$V_{ab_1} + 3V_{ab_1} + 10i_1 - 4 = 0$$


$$4V_{ab_1} + 10(0) = 4$$

$$V_{ab_1} = 1V$$



$$\frac{V_{ab_2} - (-3V_{ab_2})}{10} = 2$$

$$V_{ab_2} = 5V$$

$$V_{ab} = V_{ab_1} + V_{ab_2} = 6V$$

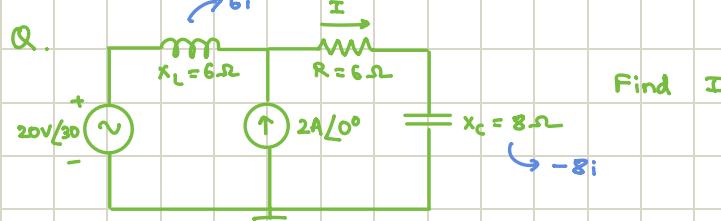


Find I

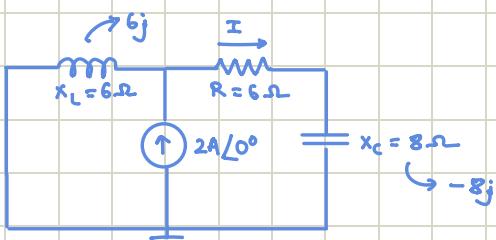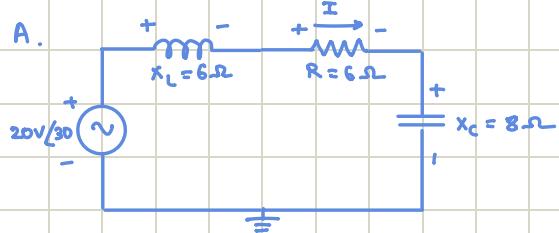

$$20V/30 = (6 - 2j)i_1 \Rightarrow i_1 = 3.16 \angle 48.43 A$$


$$i_2 = \frac{2 \times 6j}{6 - 2j} = 1.89 \angle 108.43$$

$$i = i_1 + i_2 = 4.42 \angle 70.22 A$$

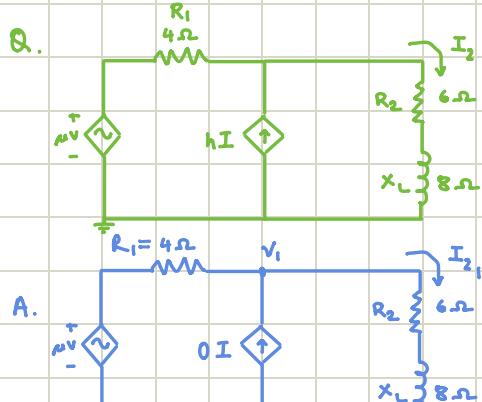


Find I_2

μ & h are constants

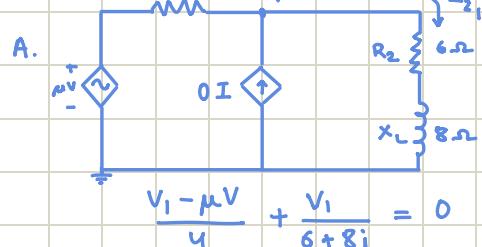

$$I_{21} = \frac{V_1}{6 + 8j} = \frac{\mu V}{10 + 8j}$$


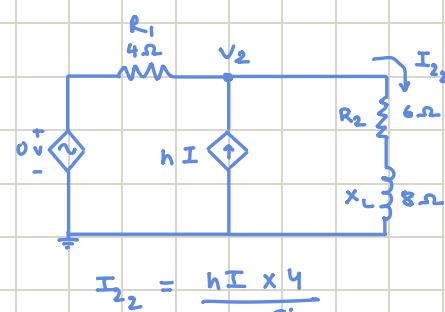
$$V_1 = \frac{\mu V}{4} \left(\frac{1}{4} + \frac{1}{6 + 8j} \right) = \frac{\mu V (6 + 8j)}{10 + 8j}$$



$$I_{22} = \frac{hI \times 4}{10 + 8j}$$

$$I_2 = I_{21} + I_{22} = \frac{\mu V + 4hI}{10 + 8j}$$


Q. Determine V_{ab}

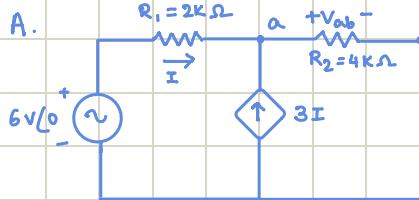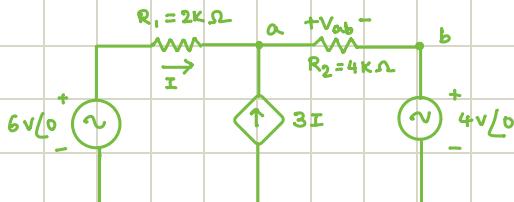

$$\text{at } a, \frac{V_a' - 6}{2000} + \frac{V_a'}{4000} = 3I \Rightarrow \frac{3V_a' - 12}{4000} = 3I \Rightarrow I = \frac{V_a' - 4}{4000}$$

$$\text{also, } I = \frac{6 - V_a'}{2000} = \frac{V_a' - 4}{4000} \Rightarrow 12 - 2V_a' = V_a' - 4 \Rightarrow V_a' = \frac{16}{3} V$$

$$V_{ab}' = V_a' = \frac{16}{3} V$$

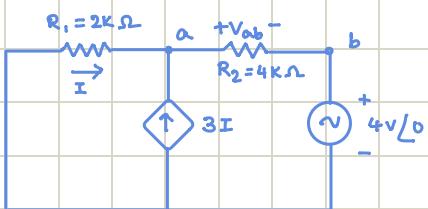

$$\text{at } a, \frac{V_a'' - 6}{2000} + \frac{V_a'' - 4}{4000} = 3I \Rightarrow I = \frac{3V_a'' - 4}{12000}$$


$$\text{also, } I = \frac{-V_a''}{2000} = \frac{3V_a'' - 4}{12000} \Rightarrow V_a'' = \frac{4}{9} V$$

$$V_{ab}'' = V_a'' - 4 = -\frac{32}{9} V$$

$$\Rightarrow V_{ab} = V_{ab}' + V_{ab}'' = \frac{16}{9} V$$

Thevenin's Theorem




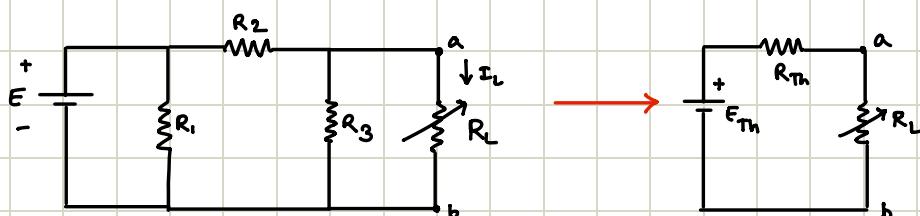
→ Same current passes through the terminals after replacing the original circuit across the terminals with the thevenin's equivalent circuit



→ Procedure

- 1) Remove that portion of the network across which Thevenin's equivalent circuit is to be found
- 2) Mark the terminals of the remaining 2-terminal network
- 3) Calculate R_{Th} by first setting all sources to zero & then finding resultant resistance b/w 2 marked terminals
- 4) Voltage sources are replaced by short circuits & current sources by open circuits
- 5) Calculate E_m by first returning all sources to original position & finding open-circuit voltage b/w marked terminals
- 6) Draw Thevenin equivalent circuit

8)

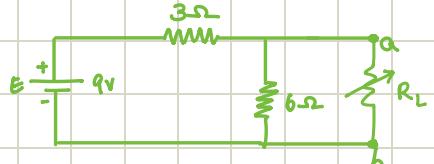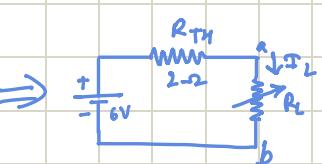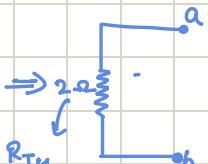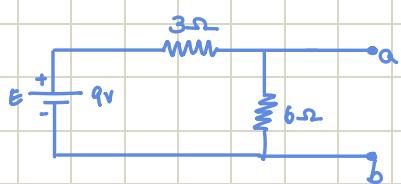
Find R_{TH} & I_L for $R_L = 100 \Omega$ 

$$I_L = \frac{E_{TH}}{R_{TH} + R_L} = \frac{6}{2 + 100}$$


$$= 0.058A$$

$$E_{TH} = E_{R_2} = \frac{9 \times 6}{3+6} = 6V$$

9)

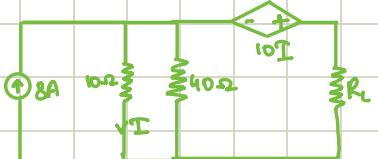Find V_{TH} accross R_L

A.

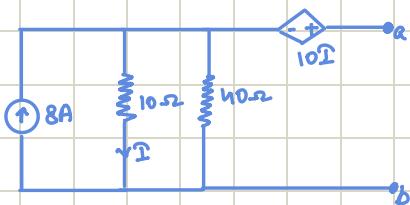


$$I = \frac{8 \times 40}{50} = 6.4A$$

$$V_{ab} - 10I - 10I = 0$$

$$\Rightarrow V_{ab} = 20 \times 6.4$$

$$= 128V$$

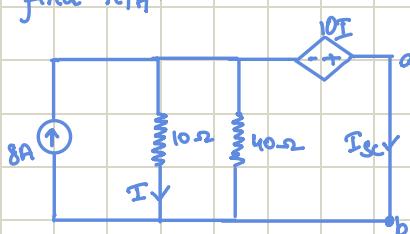To find R_{TH} :

$$WKT, R_{TH} = \frac{E_{TH}}{I_{SC}}, E_{TH} = 128V$$

All branches are parallel

$$V_{10\Omega} = 10 \times I \quad \text{---} \textcircled{1}$$


But drop voltage source is parallel to 10Ω . $\therefore V_{10\Omega} = -10I$ ---So from $\textcircled{1}$ & $\textcircled{2}$,

$$10 \times I = -10I \quad \text{or} \quad I = 0$$


Therefore the nodal voltage $V_C = 0V$

$$\text{By KCL, } I_{SC} = 8A \Rightarrow R_{TH} = \frac{128}{8} = 16\Omega$$

Q. Find Thevenin's equivalent across a-b

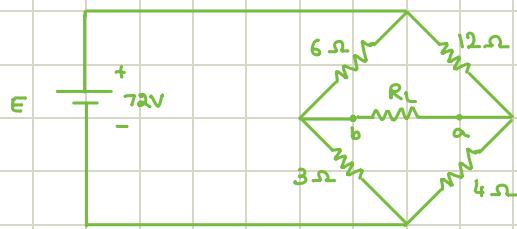


A.

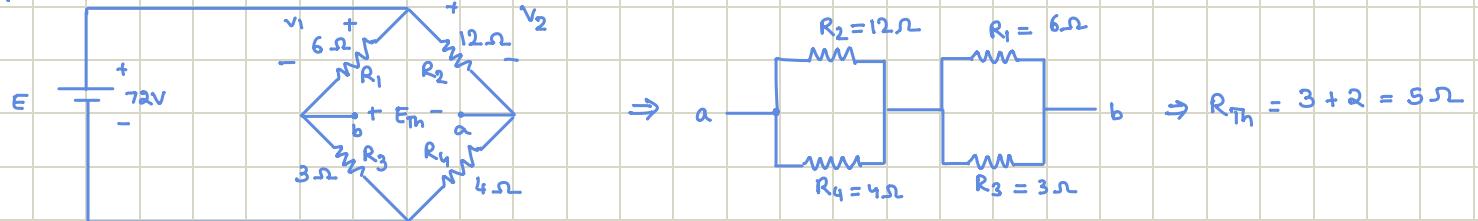


$$V_1 = \frac{E \times R_1}{R_1 + R_3} = \frac{72 \times 6}{6 + 3} = 48V$$

$$V_2 = \frac{E \times R_2}{R_2 + R_4} = \frac{72 \times 12}{12 + 4} = 54V$$

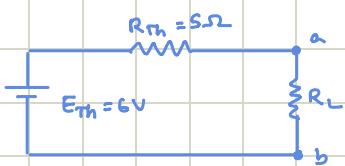KVL for mesh 1 $\Rightarrow E_{Th} + V_1 - V_2 = 0 \Rightarrow E_{Th} = 54 - 48 = 6V$





Q.

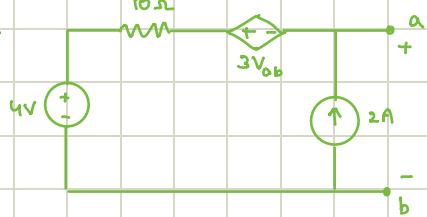


A.

$$V_{ab} = 6V$$

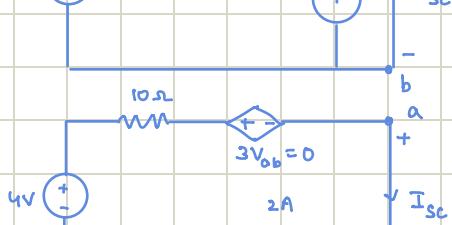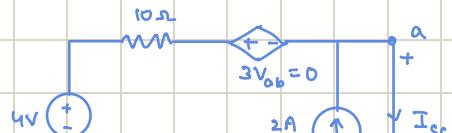

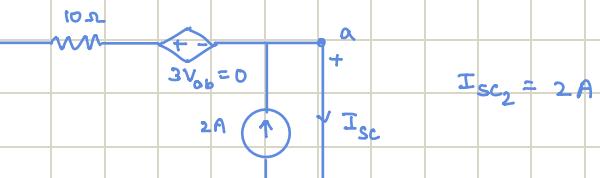
$$-4 + 10I_{Sc1} + 0 = 0 \Rightarrow I_{Sc1} = 0.4A$$



$$I_{Sc} = I_{Sc1} + I_{Sc2} = 2.4A$$

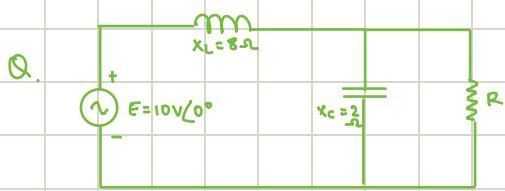
$$R_{Th} = \frac{E_{Th}}{I_{Sc}} = \frac{6}{2.4} = 2.5\Omega$$



A.

$$E_{Th} = \frac{E \times (-2j)}{8j - 2j} = 3.33V \angle -180^\circ$$
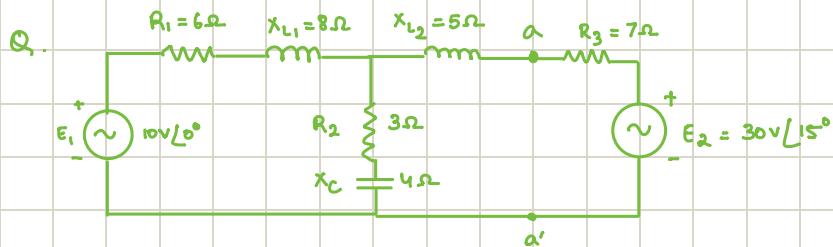
$$Z_{Th} = \left(\frac{1}{8j} - \frac{1}{2j} \right)^{-1} = 2.66 \Omega \angle -90^\circ$$



A.


$$z_1 = 6 + j8 \Omega$$



$$z_2 = 3 - j4 \Omega$$

$$z_3 = j5 \Omega$$

$$Z_{Th} = z_3 + (z_1 \parallel z_2) = j5 + \frac{(6+j8)(3-j4)}{9+j4} = 5.49 \angle 32.36^\circ \Omega$$
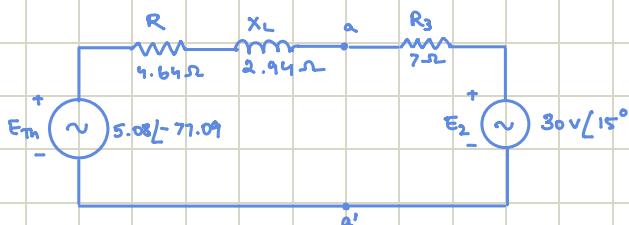
$$E_{Th} = \frac{E_1 z_2}{z_1 + z_2} = \frac{10 \times (3-j4)}{9+j4} = 5.08 \angle -77.09^\circ V$$



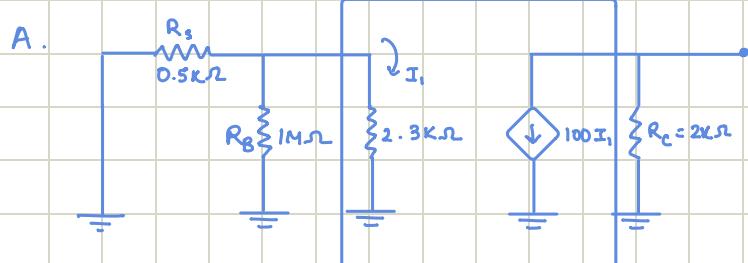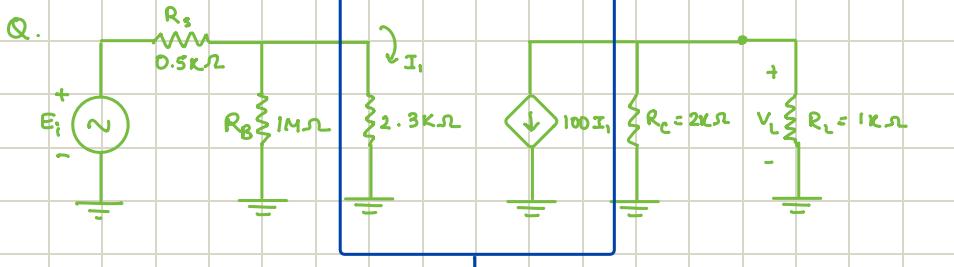


$I_1 = 0$ cuz No voltage Source

Dependant Source also is 0

$$Z_{Th} = 2\text{k}\Omega$$

For E_{Th} ,

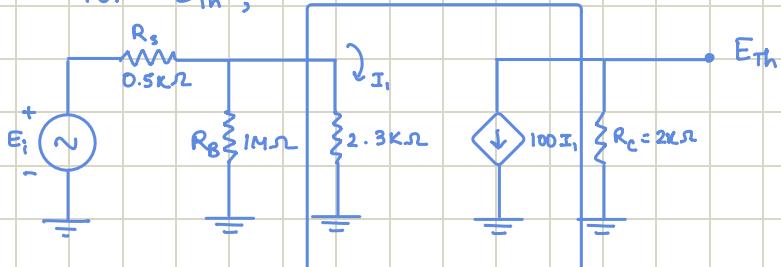

$$\text{By KCL} \Rightarrow 100I_1 + \frac{E_{Th}}{2000} = 0$$

$$I_1 = \frac{E_i}{R_s + 2300} = 0.357 \times 10^{-3} E_i$$

$$E_{Th} = -2000 \times 100 I_1 = -71.4 E_i$$


Norton's Theorem

→ Any 2-terminal linear bilateral DC network can be replaced by an equivalent circuit consisting of a current source (I_N) & a parallel resistor


(Norton's & Thevenin's are the dual of each other)

→ Procedure



- Remove portion across which norton equivalent circuit is found
- Mark the terminals of remaining '2-terminal network'
- Calculate R_N by setting all sources to zero & finding resultant resistance b/w marked 2 terminals
- Calculate I_N by setting all sources back to original & finding short circuit b/w marked terminals
- Draw Norton equivalent with portion of circuit initially removed replaced b/w terminals of equivalent circuit

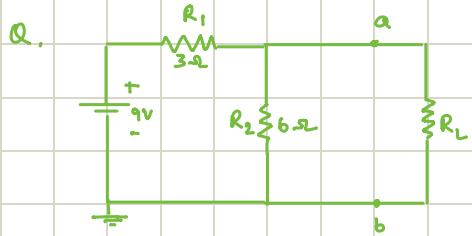

A. 1) Remove R_L b/w a & b

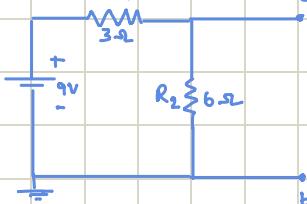


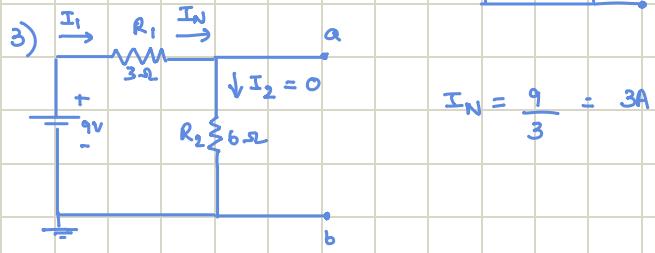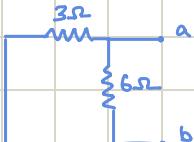
$$2) R_N \Rightarrow 3 \parallel 6 = 2\Omega$$




$$I_N = \frac{9}{3} = 3A$$

Norton's equivalent \Rightarrow

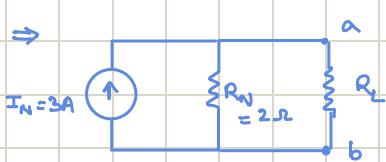


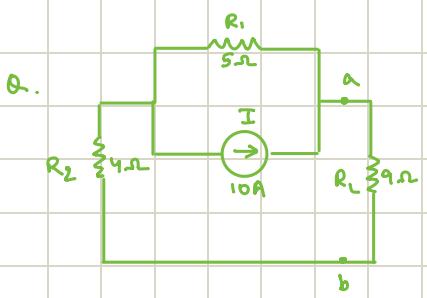


A. To find Norton's current

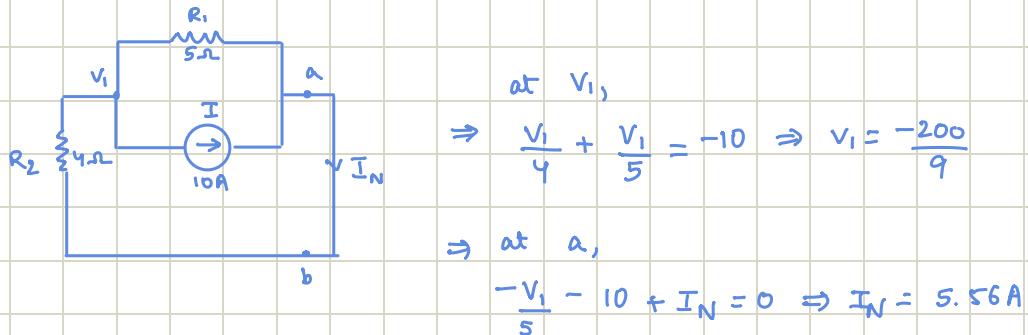


To find RN

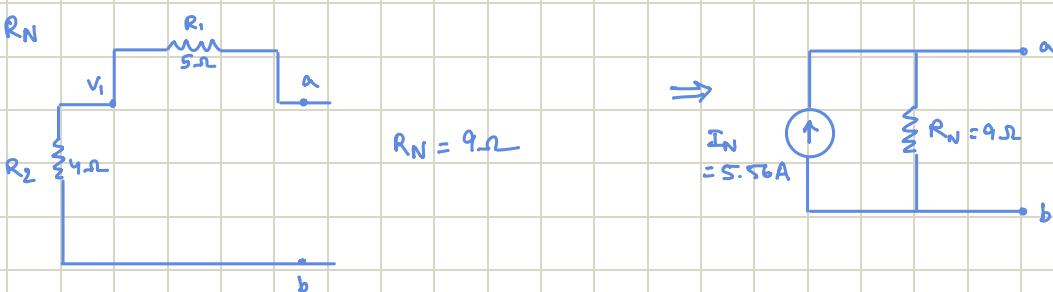


Q.

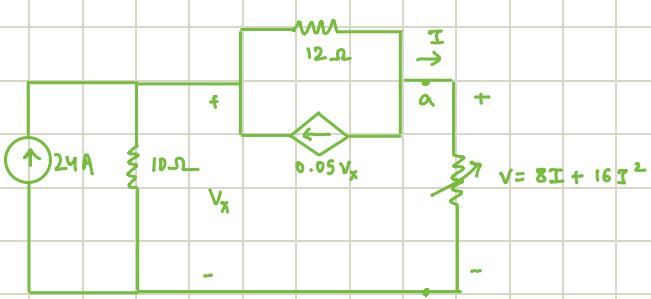

A.

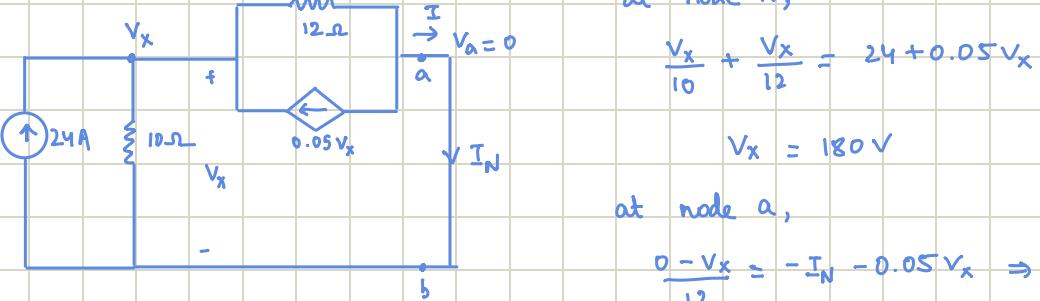

Find V_{oc} b/w a-b

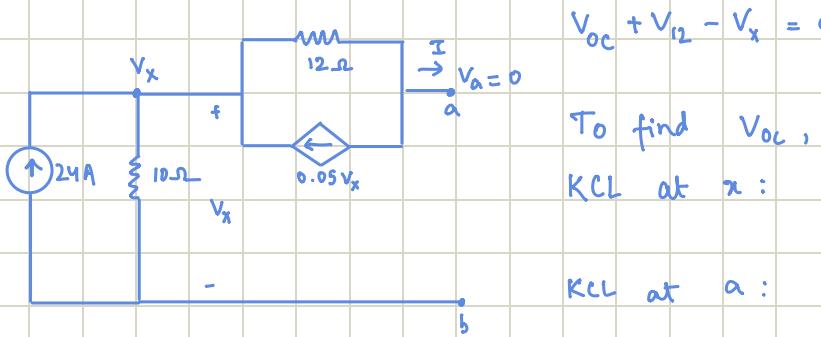



To find V_{oc} ,

$$\text{KCL at } x: -24 + \frac{V_x}{10} = 0 \Rightarrow V_x = 240V$$

$$\text{KCL at } a: \frac{V_{oc} - V_x}{12} = -0.05V_x$$

$$\Rightarrow V_{oc} = 12 \left(\frac{1}{12} - 0.05 \right) V_x$$

$$= 96V$$

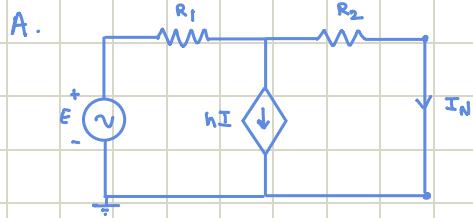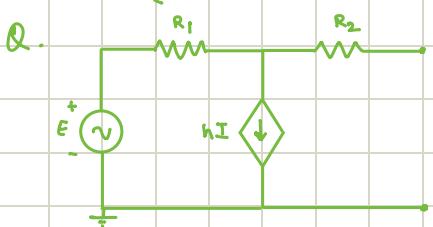

To find I_N ,

$$I = \frac{V_1 - E}{R_1}$$

$$\Rightarrow hI = h \frac{(V_1 - E)}{R_1}$$

KCL at node 1,

$$\frac{V_1 - E}{R_1} + h \frac{(V_1 - E)}{R_1} + \frac{V_1}{R_2} = 0$$

$$V_1 \left[\frac{1}{R_1} + \frac{h}{R_1} + \frac{1}{R_2} \right] = \frac{(h+1)E}{R_1}$$

$$V_1 \left[\frac{R_2 + hR_2 + R_1}{R_1 R_2} \right] = \frac{(1+h)E}{R_1}$$

$$V_1 = \frac{(1+h)E R_2}{R_2 + hR_2 + R_1}$$

$$\text{As } I_N = \frac{V_1}{R_2} = \frac{(1+h)E}{R_1 + R_2(1+h)}$$

$$\frac{V_{oc} - E}{R_1} + h \frac{(V_{oc} - E)}{R_1} = 0$$

$$V_{oc} \left[\frac{1}{R_1} + \frac{h}{R_1} \right] = \frac{1+h}{R_1} \cdot E$$


$$V_{oc} = E$$

$$Z_N = \frac{V_{oc}}{I_N} = \frac{E}{\frac{(1+h)E}{R_1 + R_2(1+h)}} = \frac{R_1 + R_2(1+h)}{1+h}$$

$$Z_N = \frac{R_1 + R_2(1+h)}{1+h}$$

Maximum Power Transfer Theorem

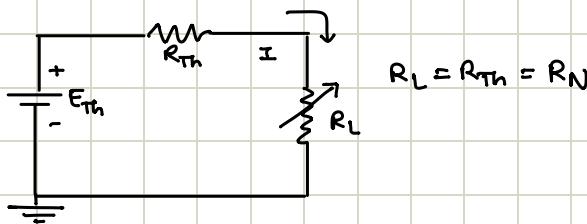→ A load will receive max power from a linear bilateral DC/AC network when its total resistive value is exactly equal to Thevenin's Resistance/Impedance of the DC/AC network as 'seen' by the load



$$\rightarrow P_L = I^2 R_L = \left(\frac{E_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$P_{\max} = \frac{E_{Th}^2}{4(R_{Th} + R_L)}$$

→ P_L is concave function of R_L

$$\frac{dP_L}{dR_L} = E_{Th}^2 \left(\frac{(R_L + R_{Th})^2 - 2R_L(R_{Th} + R_L)}{(R_L + R_{Th})^4} \right) = 0$$

$$R_L = R_{Th} \Rightarrow P_{L(\max)} = \frac{E_{Th}^2}{4R_{Th}} = \frac{I_N^2 R_{Th}}{4}$$

Condition

Max Power transferred

Q. $E_{Th} = 60V$, $R_{Th} = 9\Omega$

Analyze I_L , V_L and P_L

A. $I_L = \frac{E_{Th}}{R_{Th} + R_L} = \frac{60}{9 + R_L}$

$$V_L = \frac{R_L E_{Th}}{R_{Th} + R_L} = \frac{R_L (60)}{9 + R_L}$$

$$P_L = V_L I_L = \frac{3600 R_L}{(9 + R_L)^2}$$

DC Operating Efficiency (η)

→ Ratio of power delivered to the load to power supplied by source


$$\eta \% = \frac{P_L}{P_S} \times 100\% = \frac{I_L^2 R_L}{E_{Th} I_L} \times 100\% = \frac{R_L}{R_{Th} + R_L} \times 100\%$$

→ Under max power transfer condition ($R_L = R_{Th}$), only 50% efficiency achieved by DC Circuits


→ R_L for given efficiency & Thevenin's circuit is given by

$$R_L = \frac{\eta R_{Th}}{1 - \eta}$$

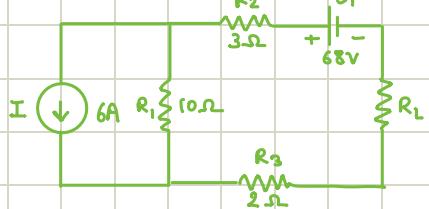
Q. For the below circuit, Find R_L that results to maximum power transfer & $P_{L\max}$?



A. $R_{Th} \Rightarrow$

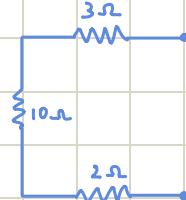

$$R_{Th} = 15\Omega = R_L$$

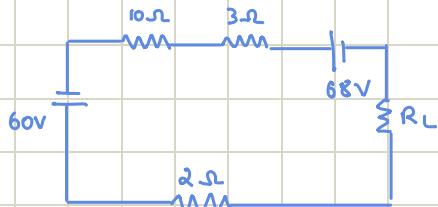

$$E_{Th} = -128V$$

$$P_{L\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(128)^2}{4 \times 15} = 273.067 W$$

Maximum Power Transfer Theorem (AC)


→ A load will receive Max power transfer when variable impedance is equal to conjugate of Thevenin's resistance

$$Z_L = Z_{Th}^*$$

$$Z_L = R_L + jX_L = R_{Th} + jX_{Th}$$

$$Z_L = Z_L \angle \theta_L = Z_{Th} \angle -\theta_{Th}$$
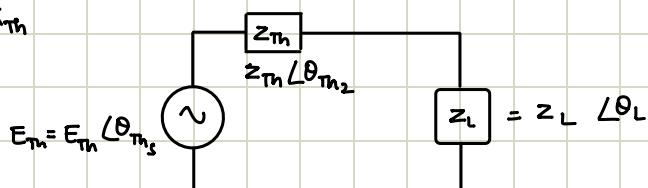
$$\rightarrow P_{L\max} = \frac{E_{Th}^2}{4R_{Th}}$$



→ Suppose only load resistance (R_L) is variable & load reactance (X_L) is fixed then the condition for maximum power is given by

$$R_L = \sqrt{R_{Th}^2 + (X_{Th} \pm X_L)^2} \Rightarrow P_{L\max} = \frac{E_{Th}^2}{4R_{avg}} \text{ where } R_{avg} = \frac{R_L + R_{Th}}{2}$$

Q. Determine optimal R_L for Max P.T when load reactance is fixed to 4Ω . What is $P_{L\max}$?

Suppose load reactance can also be varied. What is the optimal load impedance for maximum power transfer? $P_{L\max}$?


$$A. R_L = \sqrt{R_{Th}^2 + (X_{Th} \pm X_L)^2} \\ = \sqrt{4^2 + (7-4)^2} = 5\Omega$$

$$R_{avg} = \frac{R_{Th} + R_L}{2} = 4.5\Omega$$


$$P_{L\max} = \frac{E_{Th}^2}{4R_{avg}} = \frac{400}{4 \times 4.5} \approx 22W$$

$$Z_L = Z_{Th}^* = (4-7j)\Omega$$

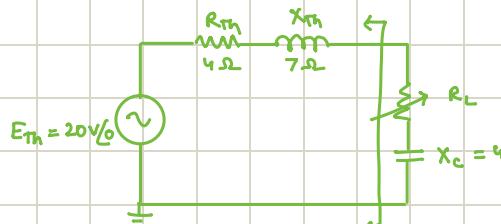
$$P_{L\max} = \frac{E_{Th}^2}{4R_{Th}} = 25W$$




Q. Find Optimal R_L .

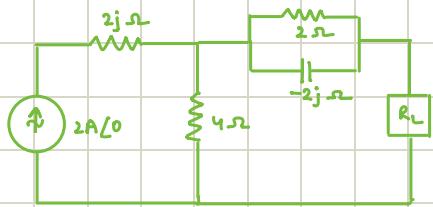
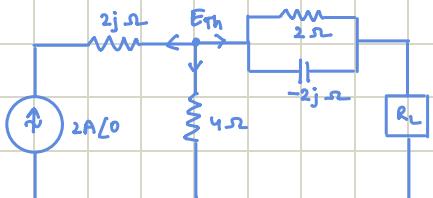
$$A. \quad R_{Th} = 4 + \left(\frac{1}{2} - \frac{1}{2j} \right)^{-1} = (5 - 1j) \Omega$$


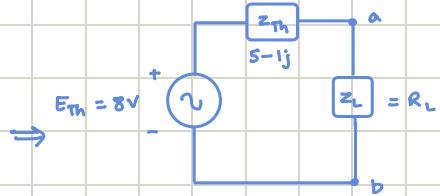
$$\frac{E_{Th}}{4} = 2 \Rightarrow E_{Th} = 8V$$




$$X_L = 0; \quad R_L = \sqrt{R_{Th}^2 + (x_L \pm x_m)^2} = \sqrt{5^2 + (0 - 1)^2} = 5.1 \Omega$$


$$R_{avg} = \frac{R_{Th} + R_L}{2} = \frac{5 + 5.1}{2} = 5.05 \Omega$$

$$P_{L\max} = \frac{|E_{Th}|^2}{4R_{avg}} = 0.627W$$


Q.

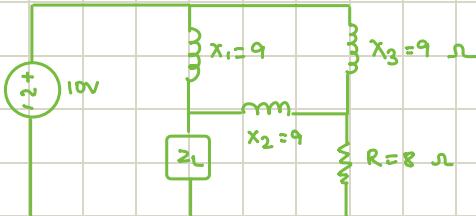

A.

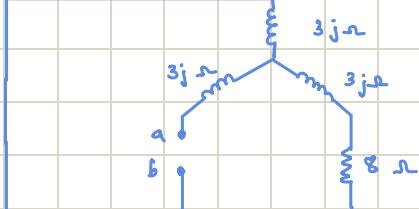
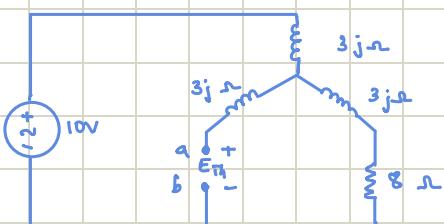
$$R_{Th} = 3j + \left(\frac{1}{3j} + \left(8 + 3j \right)^{-1} \right)^{-1} = \frac{18}{25} + \frac{273}{50}j = 0.72 + j5.46 \Omega$$



$$E_{Th} = 10[0 \times \frac{(8+3j)}{8+3j+3j}] = 8.54 \angle -16.31^\circ$$

$$P_{RL} = \frac{|E_{Th}|^2}{4R_{Th}} = 25.34 W$$

NAS UNIT - 2

Transients : RC Charging & discharging phase

→ Charging Phase

→ Voltage across the capacitor doesn't change instantaneously

i_c = current through the capacitor


$$a) t=0 \Rightarrow \text{time before switching} \Rightarrow i_c(0) = 0A$$

$$v_c(0) = 0V$$

$$b) t=0 \Rightarrow \text{time of switching} \Rightarrow i_c(0) = E/R$$

$$v_c(0) = v_c(0^-)$$
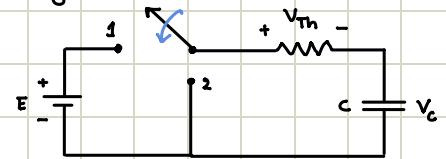
$$c) t>0 \Rightarrow v_c(t), i_c(t) = C \frac{dv_c(t)}{dt}$$




At $t=0$: C acts as short circuit

$t=\infty$: C acts as open circuit

$$\text{At } t=\infty, v_c(\infty) = E$$

$$i_c(\infty) = 0A$$

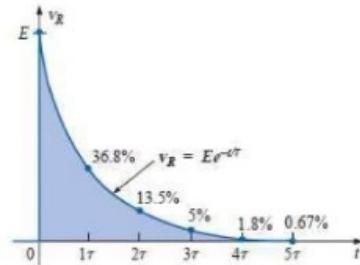

$$\begin{array}{l} R \\ \parallel \\ \text{---} \end{array} \xrightarrow{\text{a}} v_c(t) \rightarrow \text{KCL at a,} \\ i_c(t) + \frac{v_c(t) - E}{R} = 0 \end{array}$$

$$C \frac{dv_c(t)}{dt} = \frac{E - v_c(t)}{R}$$

$$\int_0^t \frac{dv_c(t)}{E - v_c(t)} = \int_0^t \frac{dt}{RC}$$

$$[-\ln(E - v_c)]_0^{v_c} = t/RC$$

$$-\ln(E - v_c) + \ln E = t/RC$$

$$\ln\left(\frac{E}{E - v_c}\right) = t/RC$$

$$\frac{E}{E - v_c} = e^{t/RC}$$


$$\frac{E - v_c}{E} = e^{-t/RC}$$

$$1 - \frac{v_c}{E} = e^{-t/RC} \Rightarrow v_c(t) = E[1 - e^{-t/RC}] \Rightarrow i_c(t) = \frac{E}{R}[1 - e^{-t/RC}]$$

$$v_c(t) = v_f + (v_i - v_f)e^{-t/RC}$$

$$\Rightarrow t = RC \ln\left(\frac{v_i - v_f}{v_c(t) - v_f}\right)$$

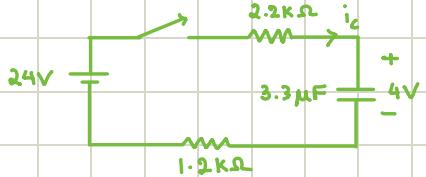Q. Find $V_c(t)$ & $i_c(t)$. Find t at which $V = 21V$



$$T = RC = (1.2 + 2.2) \times 10^3 \times 3.3 \times 10^{-6} = 11.22 \times 10^{-3} \text{ s}$$

$$i_c(0) = \frac{24 - 4}{(2.2 + 1.2) \times 10^3} = 5.88 \text{ mA}, V_c(0) = 4V$$

$$V_c(\infty) = 24V, i_c(\infty) = 0A$$

(After a long period of time)
when switch is on, capacitor behaves like open ckt

$$\begin{aligned} V_c(t) &= V_c(\infty) + (V_c(0) - V_c(\infty)) e^{-t/T} \\ &= 24 + (4 - 24) e^{-t/11.22 \times 10^{-3}} \\ &= 24 - 20 e^{\frac{-t}{11.22 \times 10^{-3}}} V \end{aligned}$$


$$i_c(t) = \frac{20 e^{\frac{-t}{11.22 \times 10^{-3}}}}{3.4 \times 10^{-3}} = 5.88 e^{\frac{-t}{11.22 \times 10^{-3}}} \text{ mA}$$

$$\text{If } V = 21V, 21 = 24 - 20e^{\frac{-t}{11.22 \times 10^{-3}}}$$

$$\ln\left(\frac{21}{24}\right) = \frac{t}{11.22 \times 10^{-3}}$$

$$\Rightarrow t = 0.021 \text{ s}$$

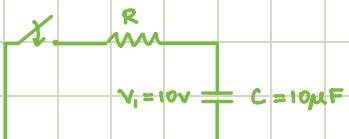Q. Capacitor was charged $V_i = 10V$. What should be value of R such that capacitor is 90% discharged at 5ms



$$T = RC = 10^{-5}R$$

$$V_c(t) = 1V @ 5 \text{ ms}$$

$$V_c(0) = V_c(0^-) = 10V$$

$$V_c(\infty) = 0V$$

$$T = \frac{t}{\ln\left(\frac{V_c(0) - V_c(\infty)}{V_c(t) - V_c(\infty)}\right)} = \frac{5 \times 10^{-3}}{\ln\left(\frac{10 - 0}{1 - 0}\right)} = 2.17 \times 10^{-3}$$

$$R = \frac{T}{C} = \frac{2.17 \times 10^{-3}}{10^{-5}} = 217 \Omega$$

- Q. a) Find mathematical expression for the transient behaviour of voltage V_C & i_C by closing switch pos 1. $V_C(0) = 0V$
- b) Find mathematical expression for the transient behaviour of voltage V_C & i_C by closing switch pos 2 at $t = 9ms$



$$A. a) E_{Th} = \frac{E R_2}{R_1 + R_2} = \frac{21 \times 30}{60 + 30} = 7V$$

$$R_{Th} = R_3 + (R_1^{-1} + R_2^{-1})^{-1} = 10 + (60^{-1} + 30^{-1})^{-1} = 30\text{ k}\Omega$$



Using thevenin's eq circuit,

$$v_c(0^-) = 0V$$

$$V_C(0) = v_c(0^-) = 0V$$

$$i_C(0) = \frac{E_{Th}}{R_{Th}} = 0.23\text{ mA}$$


$$V_C(\infty) = 7V \quad i_C(\infty) = 0A$$

$$\tau = RC = 30 \times 10^3 \times 0.2 \times 10^{-6} = 6\text{ ms}$$

$$v_c(t) = v_c(\infty) + (v_c(0) - v_c(\infty)) e^{-t/\tau} \\ = 7 + (0 - 7) e^{-t/6\text{ ms}} = 7 - 7e^{-t/6\text{ ms}}$$

$$i_C(t) = i_C(\infty) + (i_C(0) - i_C(\infty)) e^{-t/\tau} \\ = 0 + (0.23 - 0) e^{-t/6\text{ ms}} \\ = 0.23\text{ mA. } e^{-t/6\text{ ms}}$$

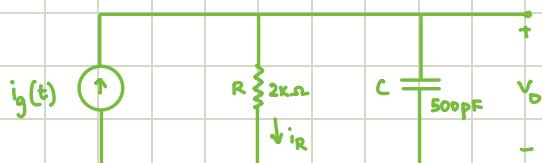- Q. After being at zero for a long time, value of $i_g(t)$ changes to 15 mA at $t=0$ (and remains the same till $t=\infty$). Find $v_o(t)$ for $t \geq 0$. Find i_R expression.



$$A. \tau = R_{Th} C = 2 \times 10^3 \times 500 \times 10^{-12} = 10^{-6} \text{ s}$$

$$v_o(0) = 0V, \quad v_o(\infty) = 2000 \times 15 \times 10^{-3} = 30V$$

$$v_o(t) = v_o(\infty) + (v_o(0) - v_o(\infty)) e^{-t/\tau} \\ = 30 + (0 - 30) e^{-t/10^{-6}} \\ = 30(1 - e^{-t/10^{-6}}) V$$

$$i_C(0) = 15\text{ mA} \quad i_R(0) = 0A$$

$$i_C + i_R = i_g = 15\text{ mA}$$

$$i_C(\infty) = 0A \Rightarrow i_R(\infty) = 15\text{ A}$$

$$i_R(t) = i_R(\infty) + (i_R(0) - i_R(\infty)) e^{-t/\tau} = 15(1 - e^{-t/10^{-6}}) A$$

$$b) \text{ at } t = 9\text{ ms}$$

$$v_i = 7 - 7e^{-1.5}$$

$$= 5.44V$$

$$v_f = 0V$$

$$\tau_2 = R_4 \times C = 10 \times 10^3 \times 0.2 \times 10^{-6} = 2\text{ ms}$$

$$v_{c_2}(t) = v_f + (v_i - v_f) e^{-t/\tau_2} \\ = -5.44 e^{-t/2\text{ ms}} V$$


$$i_i = \frac{v_i}{R_4} = \frac{-5.44}{10^4} = -0.544\text{ mA}$$

$$i_f = 0A$$

$$i_{\Sigma}(t) = i_f + (i_i - i_f) e^{-t/\tau_2} \\ = -0.544\text{ mA. } e^{-t/2\text{ ms}}$$

Q. $v_i(t)$ for $t \geq 0$

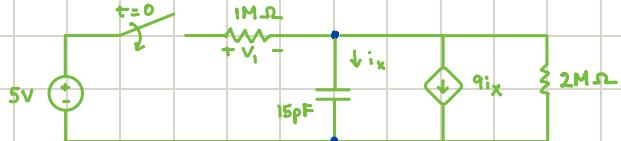(To find R_{Th} , find I_{sc} & E_{Th} across the blue terminals)



A. i) $v_i(0^-) = 0V, v_c(0^-) = 0V$


At $t=0$, $v_c(0) = v_c(0^-) = 0V$, capacitor voltage doesn't change instantaneously

By KVL, $v_i(0) + v_c(0) = 5V \Rightarrow v_i(0) + 0 = 5V \Rightarrow v_i(0) = 5V$

At $t=\infty$, $v_c(\infty) = \frac{5 \times 2}{1+2} = 3.33V$

has fully charged By KVL : $v_i(\infty) = \frac{5 \times 1}{1+2} = 1.67V$ & acts as open circuit


ii) For $t \geq 0$

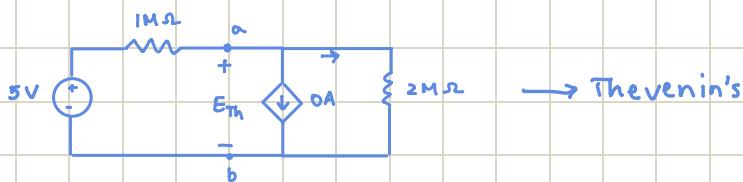

KCL at node a, $\frac{E_{Th} - 5}{1M} + 0 + \frac{E_{Th}}{2M} = 0$

$2E_{Th} - 10 + E_{Th} = 0 \Rightarrow E_{Th} = 3.33V$

To find I_{sc} :

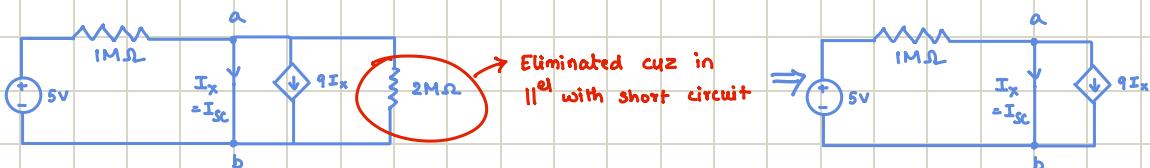


KCL at node a: $\frac{0-5}{1M} = -I_x - 9I_x \Rightarrow I_x = 0.5mA$

$$R_{Th} = \frac{E_{Th}}{I_{sc}} = \frac{3.33}{0.5 \times 10^{-3}} = 6.66M\Omega$$

iii) $\tau = R_{Th}C = 6.66M \times 15pF = 99.9\mu s \approx 100\mu s$

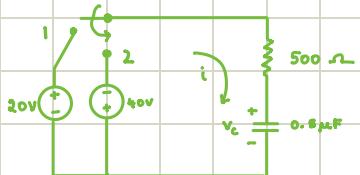iv) $v_i(t) = v_i(\infty) + (v_i(0) - v_i(\infty)) e^{-\frac{t}{\tau}}$
 $= 1.67 + 3.33 e^{-\frac{t}{100 \times 10^{-6}}} V$

Q. The switch in the circuit is closed on position 1 at $t=0$ & then moved to 2 after one time constant, at $t = \tau = 250\text{ms}$. Obtain the current for $t > 0$




A.

$$i(t) = \begin{cases} 0.04 e^{-t/250\mu\text{s}} \text{ A} & , t \leq \tau = 250\mu\text{s} \\ -0.105 e^{-t/250\mu\text{s}} \text{ A} & , t > \tau \end{cases}$$

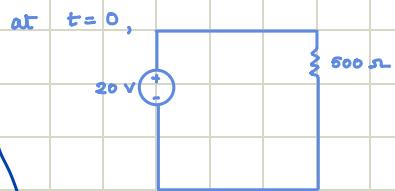i) for $t \gg 0$ & switch at position 1

$$\tau = RC = 500 \times 0.5 \times 10^{-6} = 250\mu\text{s}$$

$$i(0^-) = 0\text{A}, i(0) = \frac{20}{500} = 0.04\text{ A}$$



$$\text{at } t = \infty, i(\infty) = 0\text{A}$$


$$i(t) = i(\infty) + (i(0) - i(\infty)) e^{-t/\tau} \\ = 0.04 e^{-t/250\mu\text{s}} \text{ A}$$

$$i(\tau) = 0.04 e^{-1} = 0.014\text{ A}$$

$$V_c(0^-) = 0\text{V}, V_c(0) = V_c(0^-) = 0\text{V}$$

$$V_c(\infty) = 20\text{V} \Rightarrow V_c(t) = 20(1 - e^{-t/\tau})$$

at $t = \tau$

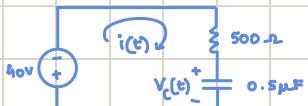

Voltage across capacitor does not change instantaneously upon switching but the current does

By KVL at $t = \tau$,

$$40 + 500 i(\tau) + V_c(\tau) = 0$$


$$\rightarrow i(\tau) = \frac{-12.64 - 40}{500} = -0.105\text{ A}$$

$$V_c(\tau) = 20(1 - e^{-1})$$

$$= 12.64\text{ V}$$

$i(\infty) = 0\text{A}$ because capacitor acts as open circuit

RL Transients - Storage Phase

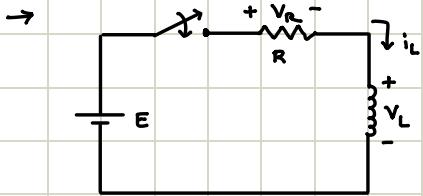

$$\text{By KVL, } E - R i_L(t) - V_L(t) = 0$$

$$E - R i_L(t) + L \frac{di_L(t)}{dt} = 0$$

$$i_L R + L \frac{di_L}{dt} = E \Rightarrow \frac{di_L}{i_L - \frac{E}{R}} = -\frac{R}{L} dt \Rightarrow \int_0^{i_L(t)} \frac{di_L}{i_L - \frac{E}{R}} = -\frac{R}{L} \int_0^t dt$$


$$\ln\left(\frac{i_L - E/R}{E/R}\right) = -\frac{Rt}{L} \Rightarrow \ln\left(\frac{i_L(t) - E/R}{-E/R}\right) = -Rt/L \Rightarrow \ln\left(\frac{-i_L(t)}{E/R} + 1\right) = -Rt/L$$

$$\frac{i_L(t)}{E/R} = 1 - e^{-\frac{Rt}{L}} \Rightarrow i_L(t) = \frac{E}{R}(1 - e^{-\frac{Rt}{L}})$$

&

$$V_L(t) = L \frac{di_L(t)}{dt} = E(1 - e^{-\frac{Rt}{L}})$$

RL Transients - Decay Phase

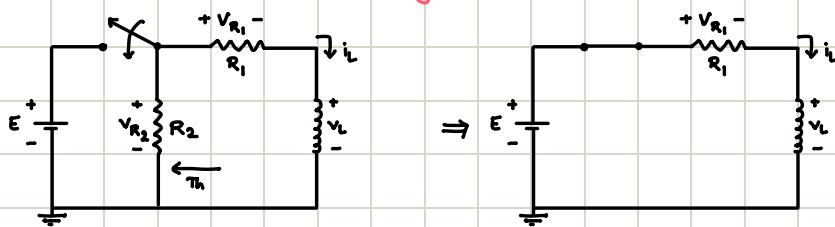

$$V_L(0^-) ; i_L(0^-) = E/R_1$$

$$I_L = i_L(0^-) = E/R_1$$

$$V_i = V_L(0^-) = -(R_1 + R_2) E$$

$$V_L(0) + i_L(0)(R_1 + R_2) = 0$$

$$V_L(0) = -(R_1 + R_2) \frac{E}{R_1}$$

$$V_L(0) + i_L(0)(R_1 + R_2) = 0$$

$$L \frac{di_L}{dt} = -i_L(0)(R_1 + R_2)$$

$$\int_0^{i_L(t)} \frac{di_L}{i_L} = -\int_0^t \frac{R_1 + R_2}{L} dt \Rightarrow \ln\left(\frac{i_L(t)}{E/R_1}\right) = -\frac{(R_1 + R_2)}{L} (dt)_0^t$$

$$\ln\left(\frac{i_L(t)}{E/R_1}\right) = -\left(\frac{R_1 + R_2}{L}\right) t$$

$$i_L(t) = \frac{E}{R_1} e^{-\left(\frac{R_1 + R_2}{L}\right)t}$$

$$\Rightarrow V_L(t) = L \frac{di_L(t)}{dt} = -L \times \frac{E}{R_1} \times \left(\frac{R_1 + R_2}{L}\right) e^{-\left(\frac{R_1 + R_2}{L}\right)t}$$

$$V_L(t) = -\left(1 + \frac{R_2}{R_1}\right) E e^{-\frac{t}{\tau}}$$

Decay Phase

$$\rightarrow i_L(t) = \frac{E}{R_1} e^{-t/\tau_d}$$

$$\rightarrow v_L(t) = -\left(1 + \frac{R_2}{R_1}\right) E e^{-t/\tau_d}$$

$$\left(\tau_d = \frac{L}{R_1 + R_2}\right)$$

Storage Phase



$$\rightarrow i_L(t) = \frac{E}{R_1} (1 - e^{-t/\tau_s})$$

$$\rightarrow v_L(t) = E (e^{-t/\tau_s})$$

$$\left(\tau_s = \frac{L}{R_1}\right)$$

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) e^{-t/\tau}$$


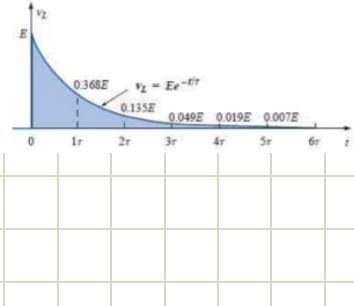
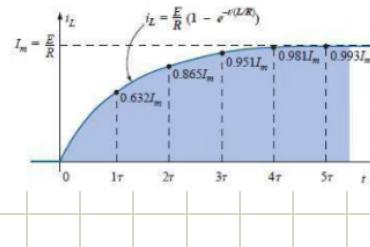
$$v_L(t) = v_L(\infty) + (v_L(0) - v_L(\infty)) e^{-t/\tau}$$



Energy

$$\rightarrow W_C = \frac{1}{2} C V^2 = \frac{1}{2} C \left(\frac{Q}{C}\right)^2 = \frac{Q^2}{2C}$$


$$\rightarrow W_L = \frac{L I_m^2}{2}$$

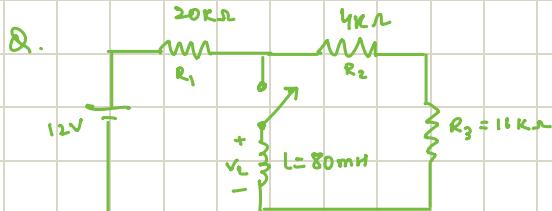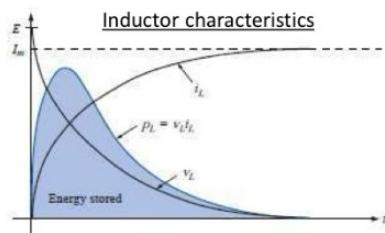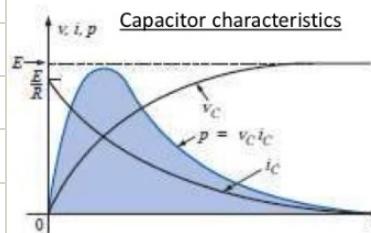

A.

$$R_{Th} = R_1 \parallel (R_2 + R_3) = 10k\Omega$$
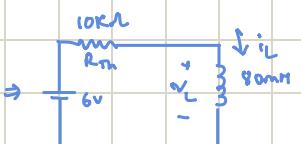
$$E_{Th} = \frac{E \times (R_2 + R_3)}{R_1 + R_2 + R_3} = 6V$$




$$I_C = i_L(0) = i_L(\infty) = 0$$

$$I_f = i_L(\infty) = \frac{E}{R_{Th}} = 0.6mA$$

$$V_i = v_L(0) = 6V$$

Q.

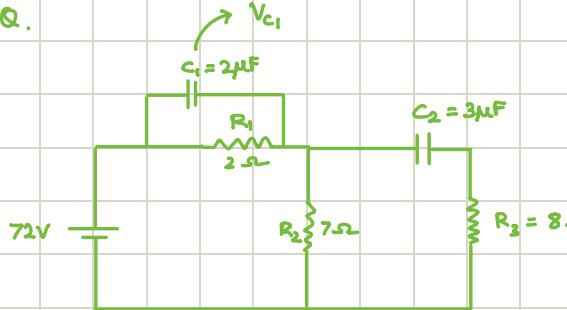

A.


$$V_{C_1}(\infty) = V_{R_1} = \frac{E \times R_1}{R_1 + R_2} = \frac{72 \times 2}{2 + 7} = 16 \text{ V}$$

$$V_{C_2}(\infty) = V_{R_2} = \frac{E \times R_2}{R_1 + R_2} = \frac{72 \times 7}{2 + 7} = 56 \text{ V}$$

$$\begin{aligned} E &= \frac{1}{2} C_1 V_{C_1}^2(\infty) + \frac{1}{2} C_2 V_{C_2}^2(\infty) \\ &= \left(\frac{1}{2} \times 2 \times 10^{-6} \times 16^2 \right) + \left(\frac{1}{2} \times 3 \times 10^{-6} \times 56^2 \right) \\ &= 4960 \times 10^{-6} \text{ J} = 4.96 \text{ mJ} \end{aligned}$$

inductor acts as short circuit at $t = \infty$ in storage phase

Q.

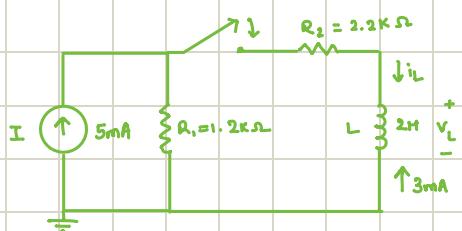

$$i_L(\infty) = \frac{E}{R_1 + R_2} = \frac{15}{2 + 3} = 3 \text{ A}$$

$$E = \frac{1}{2} L i_L^2(\infty) = \frac{1}{2} \times 6 \times 10^{-3} \times 3^2 = 27 \text{ mJ}$$

$$A. \quad I_L = i_L(0^-) = -3 \text{ mA}$$

$$I_f = i_L(\infty) = \frac{6}{R_1 + R_2} = 1.76 \text{ mA}$$

$$V_{R_1}(0) + V_{R_2}(0) + V_L(0) = 0$$

$$-1.2k I_{R_1} + 2.2k I_L(0) + V_L(0) = 0$$

$$I_{R_1}(0) - I + I_L(0) = 0$$

$$I_{R_1}(0) - 5m - 3m = 0$$

$$I_{R_1}(0) = 8 \text{ mA}$$

$$-1.2k(8m) + 2.2k(-3m) + V_L(0) = 0 \Rightarrow V_L(0) = 16.2 \text{ V}$$

$$V_L(\infty) = 0 \text{ V}$$



$$\tau = \frac{L}{R_1 + R_2} = \frac{2}{3400} = 588 \mu\text{s}$$

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) e^{-t/\tau}$$

$$= 1.76 + 4.76 e^{-\frac{t}{588 \mu\text{s}}} \text{ mA}$$

$$\begin{aligned} v_L(t) &= V_L(\infty) + (V_L(0) - V_L(\infty)) e^{-t/\tau} \\ &= 16.2 e^{-\frac{t}{588 \mu\text{s}}} \text{ V} \end{aligned}$$

Q.

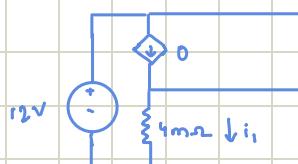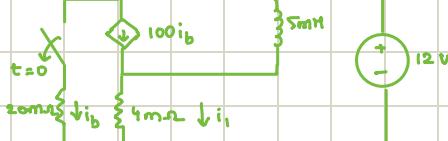

$$A. \quad -i_1(0^-) + i_L(0^-) + 100i_b(0^-)$$

$$\begin{aligned} i_L(0^-) &= i_1(0^-) - 100i_b(0^-) \\ &= \frac{12}{4m} - 100 \left(\frac{12}{20m} \right) \\ &= -57 \text{ kA} \end{aligned}$$

$$i_L(0) = i_L(0^-) = -57 \text{ kA}$$

$$i_1(\infty) = \frac{12}{4m} = 3 \text{ kA}$$

$$E_{Th} = 12 \text{ V}, \quad I_{sc} = \frac{12}{4m}$$

$$R_{Th} = \frac{12}{\frac{12}{4m}} = 4m\Omega$$

$$\tau = \frac{L}{R_{Th}} = \frac{5m}{4m} = 1.25 \mu\text{s}$$

$$\begin{aligned} i_1(t) &= i_1(\infty) + (i_1(0) - i_1(\infty)) e^{-t/\tau} \\ &= 3 - 60e^{-\frac{t}{1.25 \mu\text{s}}} \text{ kA} \end{aligned}$$

Laplace Transform

$$\rightarrow L[f(t)] = F(s) = \int_{0^-}^{\infty} f(t) e^{-st} dt$$

$$f(t) = L^{-1}[F(s)] = \frac{1}{2\pi j} \int_{-\infty - jw}^{\infty + jw} F(s) e^{st} ds \quad \text{where } s = \sigma + j\omega$$

$i(t) \xrightarrow{\text{Laplace}} I(s)$

→ Laplace transform converts differential equation from time domain into algebraic equations in complex frequency domain

→ $f(t)$ to have laplace transform must obey

$$\int_{0^-}^{\infty} |f(t)| e^{\sigma t} dt < \infty$$

$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$
t	$\frac{1}{s^2}$
e^{-at}	$\frac{1}{s+a}$
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
te^{-at}	$\frac{1}{(s+a)^2}$
$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$

$$\rightarrow L\left[\sum_i f_i(t)\right] = \sum_i L[f_i(t)] \quad (\text{Linearity})$$

$$\rightarrow \text{if } L[f(t)] = F(s), \quad L\left[\frac{df(t)}{dt}\right] = sF(s) - f(0^-) \quad (\text{Real Differentiation})$$

$$L\left[\frac{d^n f(t)}{dt^n}\right] = s^n F(s) - s^{n-1} f(0^-) - \dots - f^{(n-1)}(0^-)$$

$$\rightarrow \text{if } L[f(t)] = F(s), \quad L\left[\int_0^t f(t) dt\right] = \frac{F(s)}{s} \quad (\text{Real Integration})$$

$$L\left[t^n f(t)\right] = (-1)^n \frac{d^n F(s)}{ds^n} \quad (\text{Differentiation by } s)$$

$$F(s-a) = L[e^{at} f(t)] \quad (\text{Complex Translation})$$

$$L[f(t-a) u(t-a)] = e^{-as} F(s) \quad (\text{Shifting Theorem})$$

Partial Fraction

→ Real roots

$$F(s) = \frac{N(s)}{(s-s_0)(s-s_1)(s-s_2)}$$

where s_0, s_1, s_2 are distinct & real and degree of $N(s) < 3$

$$\text{Then, } F(s) = \frac{K_0}{s-s_0} + \frac{K_1}{s-s_1} + \frac{K_2}{s-s_2}$$

→ To solve,

$$K_i = (s-s_i) \cdot F(s) \Big|_{s=s_i}$$

→ Complex Roots

$$F(s) = \frac{N(s)}{D_1(s)(s+\sigma+j\omega)(s+\sigma-j\omega)}$$

$$F(s) = \frac{N_1(s)}{D_1(s)} + \frac{A_1}{s+\sigma+j\omega} + \frac{A_2}{s+\sigma-j\omega}$$

$$A_1 = (s+\sigma+j\omega) F(s) \Big|_{s=\sigma-j\omega}$$

$$= \alpha + j\beta \quad (\text{or}) \quad K e^{j\phi}$$

$$K = |A_1| = \sqrt{\alpha^2 + \beta^2} \quad \lambda \phi = \tan^{-1}\left(\frac{\beta}{\alpha}\right)$$

$$\begin{aligned} f_1(t) &= \mathcal{L}^{-1}\left(\frac{K e^{j\phi}}{s+\sigma+j\omega} + \frac{K e^{-j\phi}}{s+\sigma-j\omega}\right) \\ &= K \left(e^{j\phi} e^{-(\sigma+j\omega)t} + e^{-j\phi} e^{-(\sigma-j\omega)t} \right) \\ &= K e^{-\sigma t} \left(e^{-j(\omega t - \phi)} + e^{j(\omega t - \phi)} \right) \\ &= 2K e^{-\sigma t} \cos(\omega t - \phi) \end{aligned}$$

Q. $F(s) = \frac{s+3}{(s+5)(s^2+4s+5)}$

A. $F(s) = \frac{A_0}{s+5} + \frac{A_1}{s+2+j} + \frac{A_2}{s+2-j}$

$$A_0 = F(s) \Big|_{s=-5} = \frac{s+3}{s^2+4s+5} = \frac{-2}{25-20+5} = -\frac{1}{5}$$

$$A_1 = F(s) \Big|_{s=-2-j} = \frac{s+3}{(s+5)(s+2-j)} = \frac{1-j}{(3-j)(-2j)} = 0.1 + 0.2j$$

$$A_2 = A_1^* = 0.1 - 0.2j$$

$$F(s) = \frac{-1}{s(s+5)} + \frac{0.1+0.2j}{s+2+j} + \frac{0.1-0.2j}{s+2-j}$$

Inverse Laplace of $F(s) \Rightarrow \mathcal{L}^{-1}[F(s)] = -\frac{1}{5}e^{-5t} + 2K e^{-\sigma t} \cos(\omega t - \phi)$

$$K = \sqrt{0.2^2 + 0.1^2} = 0.223 \quad \phi = \tan^{-1}\left(\frac{0.2}{0.1}\right) = 63.43^\circ$$

$$f(t) = \frac{-1}{5}e^{-5t} + 0.446 e^{-2t} \cos(t - 63.43^\circ)$$

$$Q. \frac{s+3}{(s+5)(s^2+4s+5)}$$

$$A. \frac{A}{s+5} + \frac{Bs+C}{s^2+4s+5} = \frac{A(s^2+4s+5) + (Bs+C)(s+5)}{(s+5)(s^2+4s+5)}$$

$$\begin{aligned} A+B &= 0 \\ 4A+5B+C &= 1 \\ 5A+5C &= 3 \end{aligned}$$

$$\left. \begin{aligned} A &= -0.2 \\ B &= 0.2 \\ C &= 0.8 \end{aligned} \right\}$$

$$\Rightarrow \frac{-0.2}{s+5} + \frac{0.2s+0.8}{(s+2)^2+1^2}$$

$$\begin{aligned} L^{-1}[F(s)] &= -0.2e^{-5t} + L^{-1}\left[\frac{0.2(s+2)}{(s+2)^2+1^2} + \frac{0.4}{(s+2)^2+1^2}\right] \\ &= -0.2e^{-5t} + 0.2e^{-2t} \cdot \cos t + 0.4e^{-2t} \sin t \\ &= -0.2e^{-5t} + 0.2e^{-2t} (\cos t + 2 \sin t) \end{aligned}$$

$$Q. Y(s) = \frac{3s^2-28}{(s-4)(s^2+4)}$$

$$A. Y(s) = \frac{A}{s-4} + \frac{Bs+C}{s^2+4} = \frac{A(s^2+4) + (Bs+C)(s-4)}{(s-4)(s^2+4)}$$

$$\left. \begin{aligned} A+B &= 3 \\ -4B+C &= 0 \\ 4A-4C &= -28 \end{aligned} \right\} \begin{aligned} A &= 1 \\ B &= 2 \\ C &= 8 \end{aligned}$$

$$Y(s) = \frac{1}{s-4} + \frac{2s+8}{s^2+4}$$

$$\begin{aligned} L^{-1}[Y(s)] &= e^{4t} + 2\cos 2t + 4\sin 2t \\ &= e^{4t} + 2(\cos 2t + 2\sin 2t) \end{aligned}$$

(OR)

$$Y(s) = \frac{A_0}{s-4} + \frac{A_1}{s+2j} + \frac{A_2}{s-2j}$$

$$A_0 = Y(s)|_{s=4} = \frac{3s^2-28}{s^2+4} = \frac{20}{20} = 1$$

$$A_1 = Y(s)|_{s=-2j} = \frac{3s^2-28}{(s-4)(s-2j)} = \frac{-12-28}{(-2j-4)(-4j)} = 1+2j$$

$$A_2 = 1-2j$$

$$K = \sqrt{12+2^2} = \sqrt{5} = 2.236 \quad \omega = 2, \gamma = 0$$

$$\phi = \tan^{-1}\left(\frac{1}{2}\right) = 63.43^\circ$$

$$\begin{aligned} f(t) &= e^{4t} + 2K \cos(2t - \phi) \\ &= e^{4t} + 4.472 \cos(2t - 63.43^\circ) \end{aligned}$$

$$Q. \quad F(s) = \frac{16}{(s-2)(s^2-7s+12)} + \frac{6s-38}{s^2-7s+12}$$

$$A. \quad F(s) = \frac{16 + (6s-38)(s-2)}{(s-2)(s^2-7s+12)} = \frac{16 + 6s^2 - 12s - 38s + 76}{(s-2)(s-3)(s-4)} = \frac{6s^2 - 50s + 92}{(s-2)(s-3)(s-4)}$$

$$\begin{aligned} F(s) &= \frac{A}{s-2} + \frac{B}{s-3} + \frac{C}{s-4} \\ &= \frac{A(s-3)(s-4)}{(s-2)(s-3)(s-4)} + \frac{B(s-2)(s-4)}{(s-2)(s-3)(s-4)} + \frac{C(s-2)(s-3)}{(s-2)(s-3)(s-4)} \\ &= \frac{A(s^2-7s+12)}{(s-2)(s-3)(s-4)} + \frac{B(s^2-6s+8)}{(s-2)(s-3)(s-4)} + \frac{C(s^2-5s+6)}{(s-2)(s-3)(s-4)} \end{aligned}$$

$$\begin{array}{l} s^2 \Rightarrow A + B + C = 6 \\ s \Rightarrow -7A - 6B - 5C = -50 \\ 1 \Rightarrow 12A + 8B + 6C = 92 \end{array} \quad \left. \begin{array}{l} A = 8 \\ B = 4 \\ C = -6 \end{array} \right\}$$

$$F(s) = \frac{8}{s-2} + \frac{4}{s-3} - \frac{6}{s-4}$$

$$\mathcal{L}^{-1}[F(s)] = f(t) = 8e^{2t} + 4e^{3t} - 6e^{4t}$$

Multiple roots

$$\rightarrow F(s) = \frac{N(s)}{(s-s_0)^n D_1(s)}$$

$$= \frac{K_0}{(s-s_0)^n} + \frac{K_1}{(s-s_0)^{n-1}} + \dots + \frac{K_{n-1}}{s-s_0} + \frac{N_1(s)}{D_1(s)}$$

$\underbrace{\qquad\qquad\qquad}_{F_1(s)}$

(Deals only with real roots in syllabus)

$$K_0 = (s-s_0)^n \cdot F(s) \Big|_{s=s_0} \Rightarrow \text{This leads to } \frac{0}{0}$$

So,

$$\begin{aligned} F_1(s) &= (s-s_0)^n F(s) \\ &= K_0 + K_1 (s-s_0) + \dots + K_{n-1} (s-s_0)^{n-1} + \frac{N_1(s)}{D_1(s)} (s-s_0)^n \end{aligned}$$

$$\frac{dF_1(s)}{ds} = K_1 + 2K_2 (s-s_0) + \dots + K_{n-1} (n-1)(s-s_0)^{n-2}$$

$$(s-s_0)^j K_j = \frac{d^j F_1(s)}{ds^j} \Big|_{s=s_0}, \quad K_2 (s-s_0)^2 = \frac{1}{2} \frac{d^2 F_1(s)}{ds^2} \Big|_{s=s_0}$$

$$(s-s_0)^j K_j = \frac{1}{j!} \frac{d^j F_1(s)}{ds^j} \Big|_{s=s_0} \quad j = 0, 1, 2, \dots, n-1$$

Q. $\frac{s-2}{s(s+1)^3}$

A. $\frac{A}{s} + \frac{K_0}{(s+1)^3} + \frac{K_1}{(s+1)^2} + \frac{K_2}{(s+1)}$

$$F_1 = \frac{K_0}{(s+1)^3} + \frac{K_1}{(s+1)^2} + \frac{K_2}{(s+1)}$$

$$A = s F(s) \Big|_{s=0} = \frac{-2}{1} = -2$$

$$K_0 = (s-1)^3 F(s) \Big|_{s=-1} = \frac{s-2}{s} = 3$$

$$K_1 = \frac{1}{1!} \frac{d}{ds} (F_1(s)) \Big|_{s=-1} = \frac{2}{s^2} \Big|_{s=-1} = 2$$

$$K_2 = \frac{1}{2!} \frac{d^2}{ds^2} (F_1(s)) \Big|_{s=-1} = \frac{-2}{2s^3} \Big|_{s=-1} = 1$$

$$F(s) = \frac{-2}{s} + \frac{3}{(s+1)^3} + \frac{2}{(s+1)^2} + \frac{2}{s+1}$$

$$f(t) = -2u(t) + (3t^2 + 2t + 2)e^{-t} u(t)$$

$$Q. \quad F(s) = \frac{2s^2}{(s-6)^3} \quad . \quad f(t) = ?$$

$$A. \quad F(s) = \frac{k_1}{(s-6)^3} + \frac{k_2}{(s-6)^2} + \frac{k_3}{(s-6)}$$

$$(s-6)^3 F(s) = k_1 + k_2(s-6) + k_3(s-6)^2$$

$$2s^2 \Big|_{s=6} = k_1 = 72$$

$$\lambda \left. \frac{d}{ds} ((s-6)^3 F(s)) \right|_{s=6} = k_2 = 4s = 24$$

$$\left. \frac{d^2}{ds^2} ((s-6)^3 F(s)) \right|_{s=6} = k_3 = 4$$

$$F(s) = \frac{72}{(s-6)^3} + \frac{24}{(s-6)^2} + \frac{4}{s-6}$$

$$= (72t^2 + 24t + 4) e^{6t} u(t)$$

Initial & Final Value Theorems

→ Initial Value Theorem

→ Relates initial value of $f(t)$ at $t = 0^+$ to limiting value of $sF(s)$ as s approaches ∞

$$\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(s)$$

($f(t)$ must be continuous (or) step discontinuity at $t = 0$)


→ If $f(t)$ is continuous at $t = 0$

$$f(0^-) = f(0^+)$$


We know, $L[f'(t)] = \int_0^\infty f'(t) e^{-st} dt = sF(s) - f(0^-)$

$$\lim_{s \rightarrow \infty} L[f'(t)] = \lim_{s \rightarrow \infty} sF(s) - f(0^-) = 0 \Rightarrow \lim_{s \rightarrow \infty} sF(s) = f(0^-) = f(0^+)$$


→ If $f(t)$ is discontinuous at $t = 0$

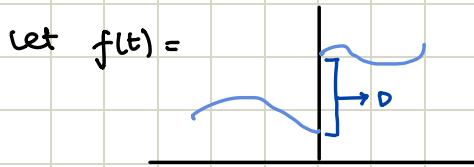

Then $f_1(t) =$

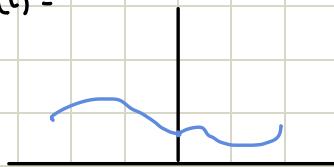

and $D u(t) =$

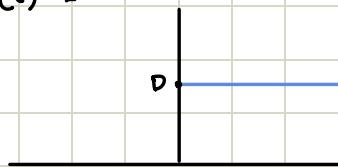

$$f(t) = f_1(t) + D u(t)$$

$$\text{where } D = f(0^+) - f(0^-)$$

$$\text{Then, } f'(t) = f'_1(t) + D \delta(t)$$

Since $f_1(t)$ is continuous at $t = 0$

$$\lim_{s \rightarrow \infty} sF_1(s) = f_1(0^-) = f(0^-)$$

Laplace on B.s

$$L[f'(t)] = L[f'_1(t)] + L[D \delta(t)]$$

$$sF(s) - f(0^-) = sF_1(s) - f_1(0^-) + D$$

$$sF(s) = sF_1(s) + D$$

$$\lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} sF_1(s) + f(0^+) - f(0^-)$$

$$\lim_{s \rightarrow \infty} sF(s) = f(0^+)$$

→ Final Value Theorem

→ Theorem states that

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$$

(Poles of denominator of $F(s)$ must not be in right half of complex frequency plane)

$$\rightarrow \int_{0^-}^{\infty} f'(t) e^{-st} dt = sF(s) - f(0^-)$$

Taking limit as $s \rightarrow 0$

$$\int_{0^-}^{\infty} f'(t) dt = \lim_{s \rightarrow 0} sF(s) - f(0^-)$$

$$f(\infty) - f(0^-) = \lim_{s \rightarrow 0} sF(s) - f(0^-)$$

$$f(\infty) = \lim_{s \rightarrow \infty} sF(s)$$

Q. Find initial value of $f(t)$ if $F(s) = \frac{2(s+1)}{s^2+2s+5}$

A. $f(0^+) = \lim_{s \rightarrow \infty} sF(s)$

$$= \lim_{s \rightarrow \infty} \frac{2s(s+1)}{s^2+2s+5} = \lim_{s \rightarrow \infty} \frac{s^2}{s^2} \left(\frac{2\left(1 + \frac{1}{s}\right)}{1 + \frac{2}{s} + \frac{5}{s^2}} \right) = \frac{2(1+0)}{1+0+0} = 2$$

Verification,

$$f(t) = \mathcal{L}^{-1}\{F(s)\} = \mathcal{L}^{-1}\left\{ \frac{2(s+1)}{s^2+2s+5} \right\} = \mathcal{L}^{-1}\left\{ \frac{2(s+1)}{(s+1)^2+2^2} \right\}$$

$$= 2e^{-t} \cos t$$

$$f(0^+) = 2$$

Q. Find final value of $f(t)$ if $F(s) = \frac{5s+3}{s(s+1)}$

$$A. f(\infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \frac{5s+3}{s+1} = 3$$

$$\text{Verification, } f(t) = \mathcal{L}^{-1}\{F(s)\} = \mathcal{L}^{-1}\left\{\frac{5s+3}{s(s+1)}\right\} = \mathcal{L}^{-1}\left\{\frac{A}{s} + \frac{B}{s+1}\right\} = \mathcal{L}^{-1}\left\{\frac{3}{s} + \frac{2}{s+1}\right\}$$

$$f(t) = 3u(t) + 2e^{-t} \Rightarrow f(\infty) = 3$$

→ Failures of initial / final value theorem

→ Initial value theorem fails when function $f(t)$ is discontinuous

$$f(t) = \delta(t) + 3e^{-t} \text{ then } f(0^+) = 3$$

$$F(s) = 1 + \frac{3}{s+1} \text{ then } \lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} s + \frac{3s}{s+1} = \lim_{s \rightarrow \infty} s + \frac{3}{1+\frac{1}{s}} = \infty$$

→ Final value theorem fails when roots of denominator (poles) are on right half of s-plane

$$f(t) = 2e^t \text{ then } f(\infty) = \infty$$

$$F(s) = \frac{2}{s-1} \text{ then } \lim_{s \rightarrow 0} sF(s) = \frac{2s}{s-1} = 0$$

The Transformed Circuit

→ The V-I relationships of network elements in time domain may be represented in complex frequency domain

$$v(t) \rightarrow L[v(t)] = V(s)$$

$$i(t) \rightarrow L[i(t)] = I(s)$$

$$\text{So, } v(t) = R i(t)$$



$$v(t) = L \frac{di(t)}{dt}$$

$$\rightarrow V(s) = R I(s)$$

$$\rightarrow V(s) = sL I(s) - L i(0^-)$$

$$i(t) = \frac{1}{L} \int_{0^-}^t v(\tau) d\tau + i(0^-)$$
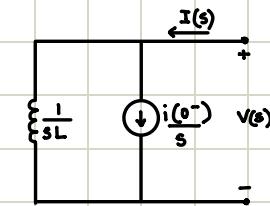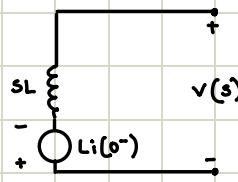
$$\rightarrow I(s) = \frac{1}{sL} V(s) + \frac{i(0^-)}{s}$$






$$v(t) = \frac{1}{C} \int_{0^-}^t i(\tau) d\tau + v(0^-)$$

$$\rightarrow V(s) = \frac{I(s)}{sC} + \frac{v(0^-)}{s}$$

$$i(t) = C \frac{dv}{dt}$$
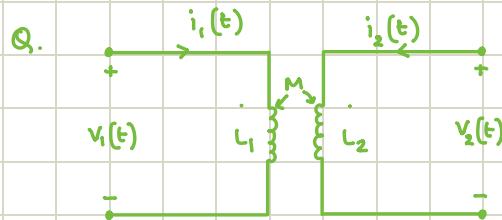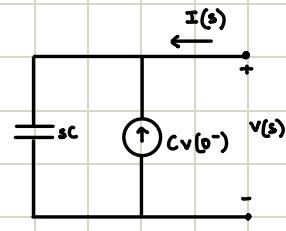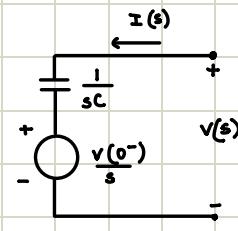
$$\rightarrow I(s) = sC V(s) - C v(0^-)$$




Consider the following transformer & transform it

$$A. \quad v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \& \quad v_2(t) = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$


$$\text{Transformed equations} \Rightarrow V_1(s) = sL_1 I_1(s) - L_1 i_1(0^-) + sM I_2(s) - M i_2(0^-)$$

$$V_2(s) = sL_2 I_2(s) - L_2 i_2(0^-) + sM I_1(s) - M i_1(0^-)$$

Transformed circuit

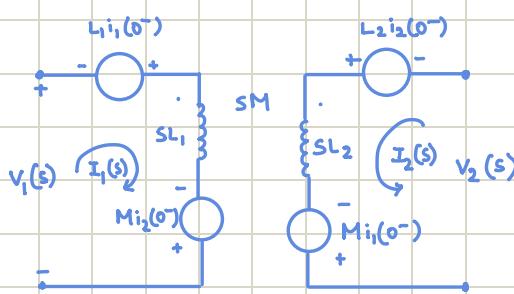

Q. Find $v_o(t)$ given $v_o(0^-) = 5V$

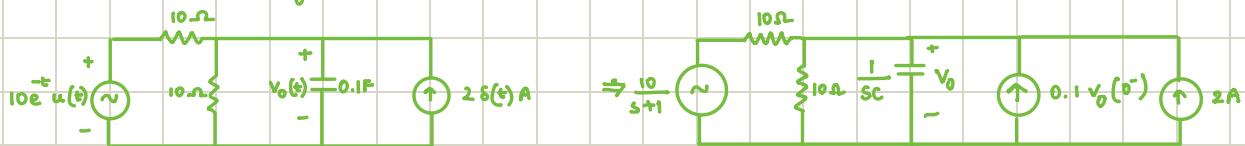

A. Applying KCL,

$$\frac{v_o(t)}{10} + \frac{v_o(t) - 10e^{-t} u(t)}{10} + 0.1 \frac{dv_o(t)}{dt} = 2\delta(t)$$

$$\text{Transforming, } \frac{V_o(s)}{10} + \frac{V_o(s)}{10} - \frac{1}{s+1} + 0.1(sV_o(s) - v_o(0^-)) = 2$$

$$V_o(s) \left(\frac{1}{10} + \frac{1}{10} + \frac{s}{10} \right) = 2 + \frac{1}{s+1} + 0.5$$

$$V_o(s) \left(\frac{s+2}{10} \right) = \frac{2.5(s+1) + 1}{s+1}$$

$$V_o(s) = \frac{2.5(s+1) + 10}{(s+1)(s+2)} = \frac{2.5s + 3.5}{(s+1)(s+2)} = \frac{A}{s+1} + \frac{B}{s+2}$$

$$As + 2A + Bs + B = 2.5s + 3.5$$

$$\begin{aligned} A + B &= 2.5 \\ 2A + B &= 3.5 \end{aligned} \quad \begin{cases} A = 10 \\ B = 15 \end{cases}$$

$$V_o(s) = \frac{10}{s+1} + \frac{15}{s+2}$$

$$v_o(t) = 10e^{-t} + 15e^{-2t}$$

Q. Find $i(t)$ for $t \geq 0$. Assume initial capacitor voltage of 1V

A. By KVL,

$$-v_c(0^-) + L \frac{di(t)}{dt} + Ri(t) = 0 \Rightarrow -1 + \frac{di(t)}{dt} + 2i(t) = 0$$

Applying transform,



$$sI(s) - i(0^-) + 2I(s) = \frac{1}{s}$$

$$sI(s) + 2I(s) = \frac{1}{s} \Rightarrow I(s) = \frac{1}{s(s+2)} = \frac{A}{s} + \frac{B}{s+2}$$


$$As + 2A + Bs = 1 \Rightarrow A = \frac{1}{2}, B = -\frac{1}{2}$$

$$I(s) = \frac{1}{2s} - \frac{1}{2(s+2)}$$

$$i(t) = 0.5u(t) - 0.5e^{-2t}$$

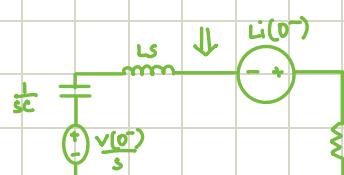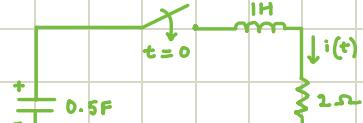

Q.

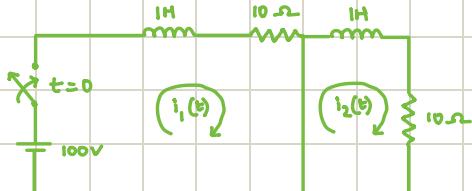

Find the mesh currents in the circuit. The switch is open for a long time before closing at $t=0$

$$A. \quad i_1(0^-) = i_2(0^-) = 0A$$

$$1 \frac{di_1(t)}{dt} + 10i_1(t) = 100 \quad \text{and} \quad \frac{di_2(t)}{dt} + 10i_2(t) = 0$$

Applying Transform,

$$sI_1(s) - i_1(0^-) + 10I_1(s) = \frac{100}{s}$$

$$I_1(s) = \frac{100}{s(s+10)} = \frac{10}{s} - \frac{10}{s+10}$$


$$i_1(t) = 10u(t) - 10e^{-10t}$$

$$sI_2(s) + i_2(0^-) + 10I_2(s) = 0$$

$$I_2(s) = 0$$

$$i_2(t) = 0$$

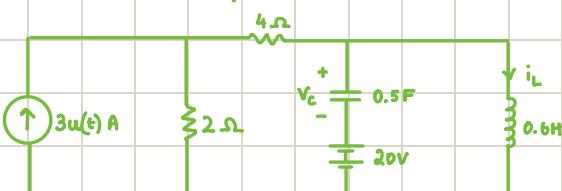Q. Find $v_c(t)$ for $t \geq 0$. The current source is activated at $t=0$



$$A. \quad v_c(0^-) = 20V \quad \& \quad i_L(0^-) = 0A$$

At $t=0$, we can apply Thevenin's Theorem

And by source transformation

By KCL,

$$\frac{v_1(t) - 6u(t)}{6} + 0.5 \frac{dv_1(t)}{dt} + \frac{1}{0.6} \int_{-\infty}^t v_1(\tau) d\tau = 0$$

$$\frac{v_1(t) - u(t)}{6} + 0.5 \frac{d(v_1(t) - 20)}{dt} + \frac{5}{3} \int_{-\infty}^t v_1(\tau) d\tau = 0$$

$$\frac{v_1(t) - u(t)}{6} + \frac{1}{2} \frac{d v_1(t)}{dt} - 0 + \frac{5}{3} \int_{-\infty}^t v_1(\tau) d\tau = 0$$

$$\text{Applying Transform, } \frac{v_1(s)}{6} - \frac{1}{s} + \frac{1}{2} (sv_1(s) - v_1(0^-)) + \frac{5}{3} \frac{v_1(s)}{s} + i_L(0^-) = 0$$

$$v_1(s) \left(\frac{1}{6} - \frac{1}{s} + \frac{5}{3s} \right) = \frac{1}{s} \Rightarrow v_1(s) = \frac{2}{s^2 + \frac{s}{3} + \frac{10}{3}}$$

$$v_1(s) = \frac{2}{(s + \frac{1}{6})^2 + (\frac{\sqrt{119}}{6})^2} = \frac{2}{(s + 0.167)^2 + (1.82)^2}$$


$$\mathcal{L}^{-1}[v_1(s)] = v_1(t) = 2e^{-0.167t} \sin(1.82t)$$

$$v_c(t) = v_1(t) - 20u(t) = 2e^{-0.167t} \sin(1.82t) - 20u(t)$$

Table for Constructing Transformed Circuits



Resistor $v(t) = R i(t)$	 $V(s) = R I(s)$	 $\gamma(s) = \frac{1}{R}$ $I(s) = \frac{V(s)}{R}$
Inductor $v(t) = L \frac{di(t)}{dt}$	 $V(s) = sL I(s) - L i(0^-)$ $v(s) = sL I(s) - L i(0^-)$	 $I(s) = \frac{V(s)}{sL} + \frac{i(0^-)}{s}$
Capacitor $i(t) = C \frac{dv}{dt}$	 $V(s) = \frac{I(s)}{sC} + \frac{v(0^-)}{s}$	 $I(s) = sC V(s) - C v(0^-)$

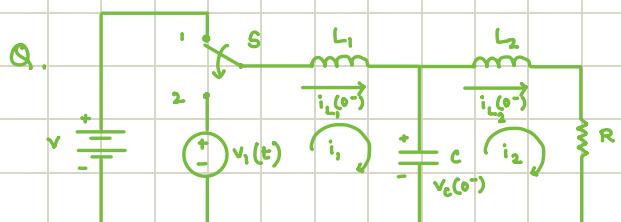

Assuming switch is thrown from posⁿ 1 to 2 at $t=0$, write mesh equations

A. mesh 1,

$$v_1(t) - L_1 \frac{di_1(t)}{dt} - \frac{1}{C} \int_{-\infty}^t (i_1(\tau) - i_2(\tau)) d\tau = 0$$

$$v_1(s) - L_1 \left(s I_1(s) - i_1(0^-) \right) - \frac{1}{C} \left(\frac{I_1(s)}{s} - \frac{I_2(s)}{s} \right) + \frac{v_c(0^-)}{s} = 0$$


$$\left(s L_1 + \frac{1}{Cs} \right) I_1(s) - \frac{I_2(s)}{sC} = v_1(s) + L_1 i_1(0^-) - \frac{v_c(0^-)}{s}$$

mesh 2,


$$L_2 \frac{di_2(t)}{dt} + R i_2(t) + \frac{1}{C} \int_{-\infty}^t (i_2(\tau) - i_1(\tau)) d\tau$$

$$L_2 \left(s I_2(s) - i_2(0^-) \right) + R I_2(s) + \frac{1}{C} \left(\frac{I_2}{s} - \frac{I_1}{s} \right) - \frac{v_c(0^-)}{s} = 0$$
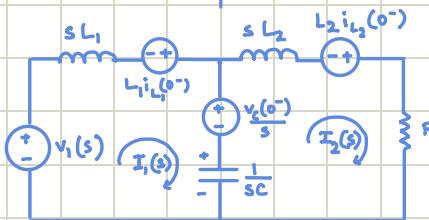
$$- \frac{I_1(s)}{sC} + \left(s L_2 + \frac{1}{Cs} + R \right) I_2(s) = L_2 i_2(0^-) + \frac{v_c(0^-)}{s}$$



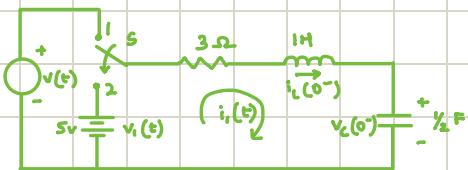Q. Assuming switch is thrown from posⁿ 1 to 2 at $t=0$, write $i(t)$ for $t \geq 0$.
 Here, $i_L(0^-) = 2A$ & $v_C(0^-) = 2V$



A.

$$KVL, 5 - 3i_1(t) - 1 \frac{di_1(t)}{dt} - \frac{1}{1/2} \int_{-\infty}^t i_1(t) dt = 0$$

$$\text{Transform, } \frac{5}{s} - 3I_1(s) - sI_1(s) + i_1(0^-) - 2 \frac{I_1(s)}{s} - \frac{v_c(0^-)}{s} = 0$$

$$I_1(s) \left(s + 3 + \frac{2}{s} \right) = \frac{5}{s} - \frac{2}{s} + 2 = \frac{3}{s} + 2$$

$$I_1(s) = \frac{\frac{3+2s}{s}}{s(s+3+\frac{2}{s})} = \frac{3+2s}{s^2+3s+2}$$


Q. Assume switch opened at $t=0$, write nodal voltages for $t \geq 0$

$$L = \frac{1}{2} H$$

$$C = 1 F$$

$$G = 1 \text{ mho}$$

$$V = 1 V$$

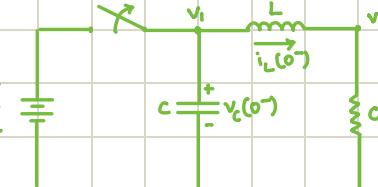

$$\text{A. Node 1, } C \frac{dV_1(t)}{dt} + \frac{1}{L} \int_{-\infty}^t (V_1(t) - V_2(t)) dt = 0$$

$$i_L(0^-) = 1A$$

$$v_C(0^-) = 1V$$

$$\text{Laplace, } C \left(sV_1(s) - v_C(0^-) \right) + \frac{1}{L} \left(\frac{V_1(s)}{s} - \frac{V_2(s)}{s} \right) + \frac{i_L(0^-)}{s} = 0$$

$$V_1(s) \left(\frac{2}{s} + s \right) - 2 \frac{V_2(s)}{s} = 1 - \frac{1}{s} \Rightarrow (2+s^2) V_1(s) - 2 V_2(s) = s - 1$$

$$\text{Node 2, } \frac{1}{L} \int_{-\infty}^t (V_2(t) - V_1(t)) dt + GV_2(s) = 0$$

$$\text{Laplace, } 2 \left(\frac{V_2(s)}{s} - \frac{V_1(s)}{s} \right) - \frac{i_L(0^-)}{s} + V_2(s) = 0$$

$$V_2(s) \left(\frac{2}{s} + 1 \right) - 2 \frac{V_1(s)}{s} = \frac{1}{s} \Rightarrow -2 V_1(s) + (2+s) V_2(s) = 1$$

$$\text{By Cramer's Rule, } V_1(s) = \begin{vmatrix} s-1 & -2 \\ 1 & s+2 \end{vmatrix} = \frac{s+1}{(s+1)^2+1}$$


$$V_2(s) = \begin{vmatrix} s^2+2 & s-1 \\ -2 & 1 \end{vmatrix} = \frac{(s+1)+1}{(s+1)^2+1}$$

$$V_1(t) = e^{-t} \cos t$$

$$V_2(t) = e^{-t} (\cos t + \sin t)$$

Thevenin's Theorem

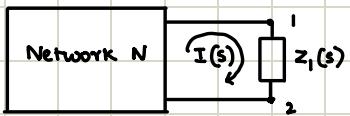→ From the standpoint of determining the current $I(s)$ through an element of impedance $Z_1(s)$, The rest of the network N can be replaced by an equivalent impedance $Z_2(s)$ in series with an equivalent voltage source $V_e(s)$




(elements in Z_1 must not be magnetically coupled to any element N)

By compensation theorem, replace $Z_1(s)$ by Voltage Source




and by superposition principle, $I(s) = I_1(s) + I_2(s)$

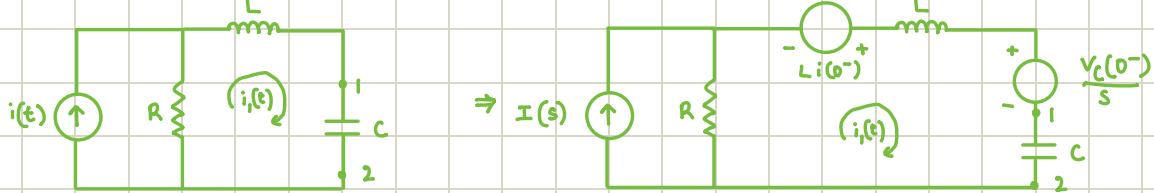
Q. Find current through capacitor using Thevenin's theorem



A. Removing Capacitor, find $Z_e(s)$

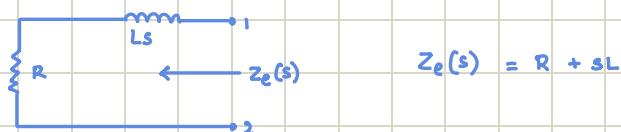


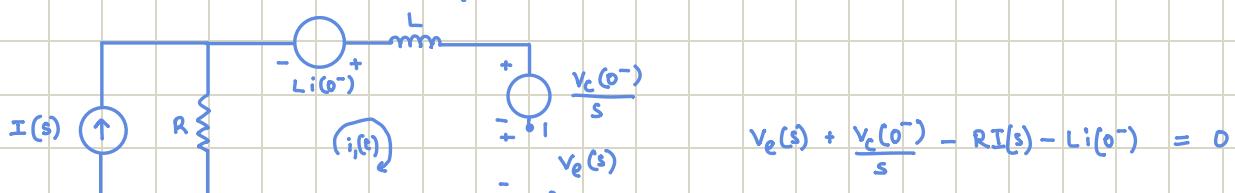Find Thevenin's voltage across Terminals 1 & 2



$$I_1(s) = \frac{V_e(s)}{Z_e(s) + Z(s)} = \frac{RI(s) + LI(0^-) - \frac{V_c(0^-)}{s}}{R + sL + \frac{1}{sC}}$$

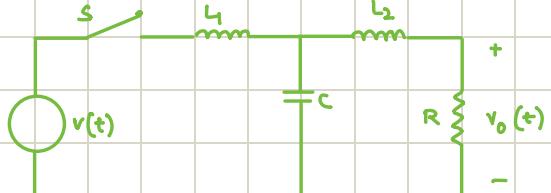Q. Find $v_o(t)$ by Thevenin's Theorem. Assume all initial values to be zero at by the time switch closes at $t=0$




A. Thevenin's Impedance $Z_e(s) = L_2 s + (L_1 s \parallel \frac{1}{sC})$

$$\text{Thevenin's Voltage } V_e(s) = \frac{V(s) \left(\frac{1}{sC} \right)}{L_2 s + \frac{1}{sC}}$$

$$\begin{aligned} \text{By voltage division, } V_o(s) &= \frac{V_e(s) R}{R + Z_e(s)} = \frac{R V(s) \left(\frac{1}{sC} \right)}{\left(L_2 s + \frac{1}{sC} \right) \left(R + L_2 s + \frac{L_1 s \times \frac{1}{sC}}{L_2 s + \frac{1}{sC}} \right)} \\ &= \frac{R V(s) \times \frac{1}{sC}}{\left((R + L_2 s) \left(L_2 s + \frac{1}{sC} \right) \right) + \frac{L_1}{C}} \end{aligned}$$

$$v_o(t) = \mathcal{L}^{-1} \{ V_o(s) \}$$

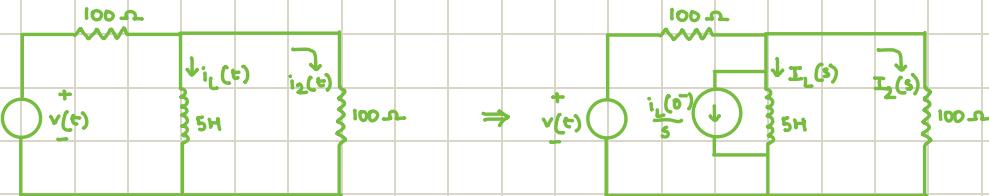Q. Find $i_2(t)$ given $v(t) = 2u(t)$ & $i_L(0^-) = 2A$



A. Thevenin's impedance, $Z_e(s) = \frac{100(5s)}{5s + 100}$

$$\text{Thevenin's voltage, } V_e'(s) = V(s) \times \frac{5s}{5s + 100} = \frac{10}{5s + 100}$$


$$V_e''(s) = -i_L(0^-) \times \frac{5s(100)}{5s + 100} = -\frac{1000}{5s + 100}$$

$$V_e(s) = V_e'(s) + V_e''(s) = -\frac{990}{5s + 100}$$

$$I_2(s) = \frac{V_e(s)}{100 + Z_e(s)} = \frac{-990}{(5s + 100)(100 + \frac{500s}{5s + 100})} = \frac{-990}{500s + 10000 + 500s} = \frac{-99}{100s + 1000} = \frac{-0.99}{s + 10}$$

$$i_2(t) = \mathcal{L}^{-1}[I_2(s)] = \mathcal{L}^{-1}\left[\frac{-0.99}{s + 10}\right] = -0.99 e^{-10t}$$

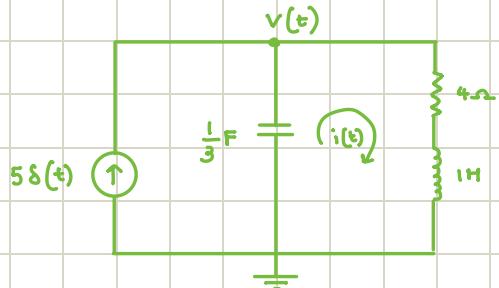Q. Find $i(t)$ using Thevenin's theorem assuming initial values as zeroes



A. Thevenin's Impedance $Z_e(s) = 4 \parallel \frac{3}{s} = \frac{4 \times 3}{s(4 + \frac{3}{s})} = \frac{12}{4s + 3} \Omega$

$$\text{Thevenin's Voltage } V_e(s) = \frac{5}{s} \times \frac{3/s}{4 + \frac{3}{s}} = \frac{15}{4s^2 + 3s}$$

Voltage across capacitor

$$I(s) = \frac{V_e(s)}{Z_e(s) + s} = \frac{\frac{15}{(4s+3)s}}{\frac{12}{4s+3} + s} = \frac{15}{(12 + 4s + 3s)s(4s+3)} = \frac{15}{s(4s^2 + 3s + 12)} = \frac{15/4}{s(s^2 + \frac{3s}{4} + 3)}$$

$$i(t) = 1.25u(t) - e^{-0.375t} (1.25 \cos 1.69t + 0.277 \sin 1.69t)$$

Solve it yourself!